

Op-amp simple comparators




Op-amp in *switching mode* \Rightarrow *comparators* with op-amp.

The **voltage comparator** compares two input voltages and signalizes to the output what input voltage is greater.

- voltages comparison: by the sign of their difference
- according to the sign of the difference, the comparator outputs one or another of the two possible output voltages
- for op-amp comparators one can consider only one input, namely the difference between v^+ and v^- , meaning v_D

$$V_O \in \{V_{OL}, V_{OH}\} \quad \begin{array}{l} v_D > 0, \text{ that is } v^+ > v^-, \quad v_O = V_{OH} \\ v_D < 0, \text{ that is } v^+ < v^-, \quad v_O = V_{OL} \end{array}$$

Op-amp model in switching regime

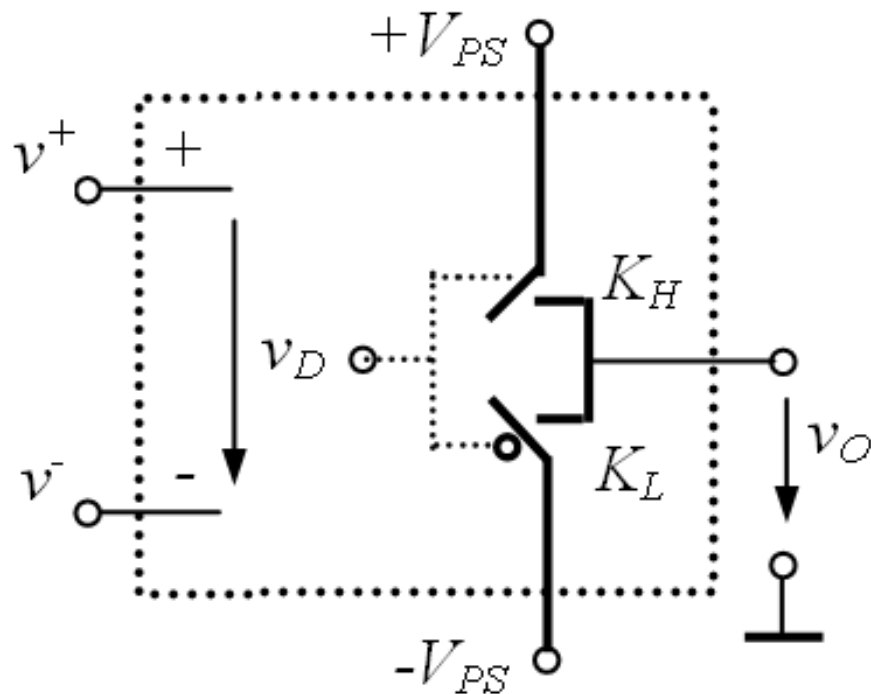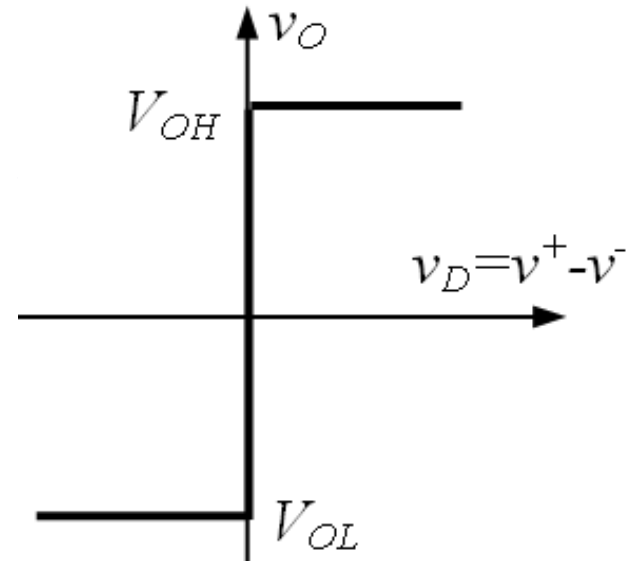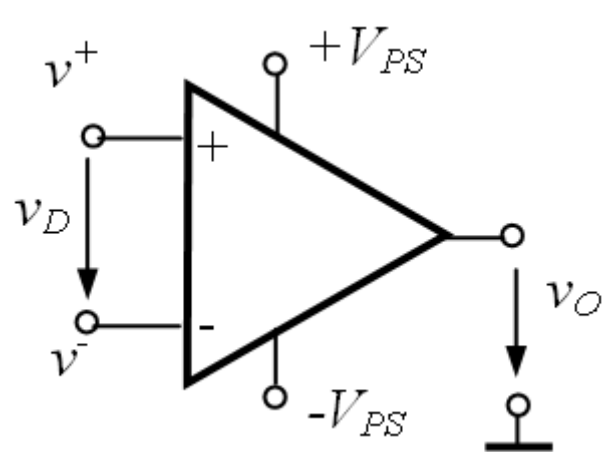

v_D	K_H	K_L	v_O
> 0	on	off	$V_{OH} = +V_{PS}$
< 0	off	on	$V_{OL} = -V_{PS}$

**Appropriate for
rail-to-rail op-amp**

Two types of voltage comparators:

➤ **simple comparators**, without any feedback, **one threshold** voltage.

➤ **hysteresis comparators**, with positive feedback, **two threshold** voltages

□ **threshold voltage V_{Th}** : that particular value of the input voltage v_I for which the output switches, v_D - crosses through zero.

Simple Comparators

- no feedback, only one threshold voltage

Threshold voltage V_{Th} : that particular value of the input voltage v_I for which the output switches from one state in the other state ($v_D = 0$).

To find V_{Th} :


- find the expression of v_D
- use the condition $v_D = 0$ and replace v_I with V_{Th}
- obtain V_{Th}

Simple comparators with $V_{Th} = 0V$

- one grounded input
- v_I is applied to the other input


Comparators with $V_{Th} = 0V$

- **noninverting**

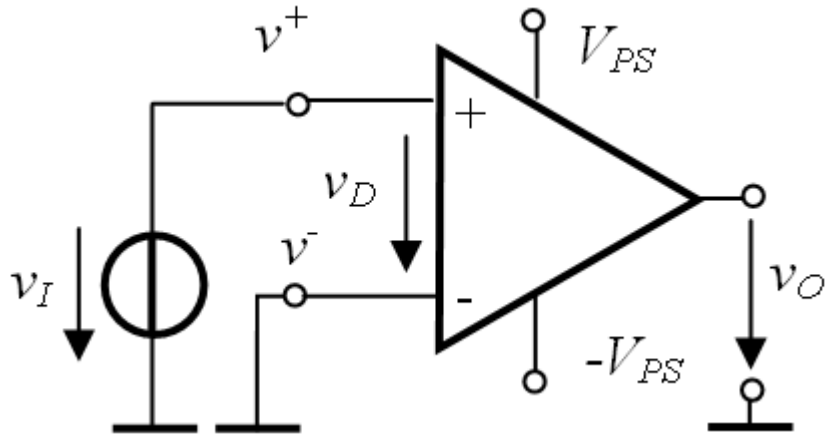

$$v_O = \begin{cases} V_{OH} & \text{if } v_D > 0, \text{ this is } v_I > 0 \\ V_{OL} & \text{if } v_D < 0, \text{ this is } v_I < 0 \end{cases}$$

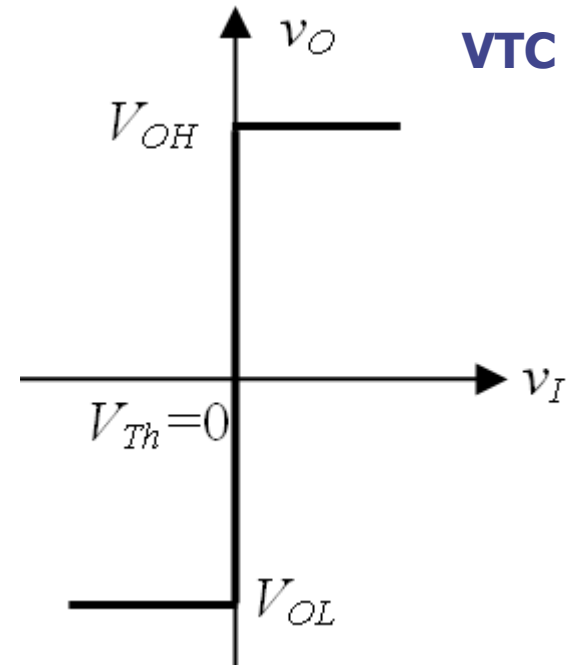How does the output voltage look like if the input voltage is a sine wave with 3 V amplitude and the supply is $\pm V_{PS} = \pm 12$ V?



$$v_D = v^+ - v^-$$


$$v^+ = v_I; \quad v^- = 0$$

$$v_D = v_I$$

$$v_D = 0; \quad V_{Th} = 0$$

Comparators with $V_{Th} = 0V$ – *cont.*


- **inverting**

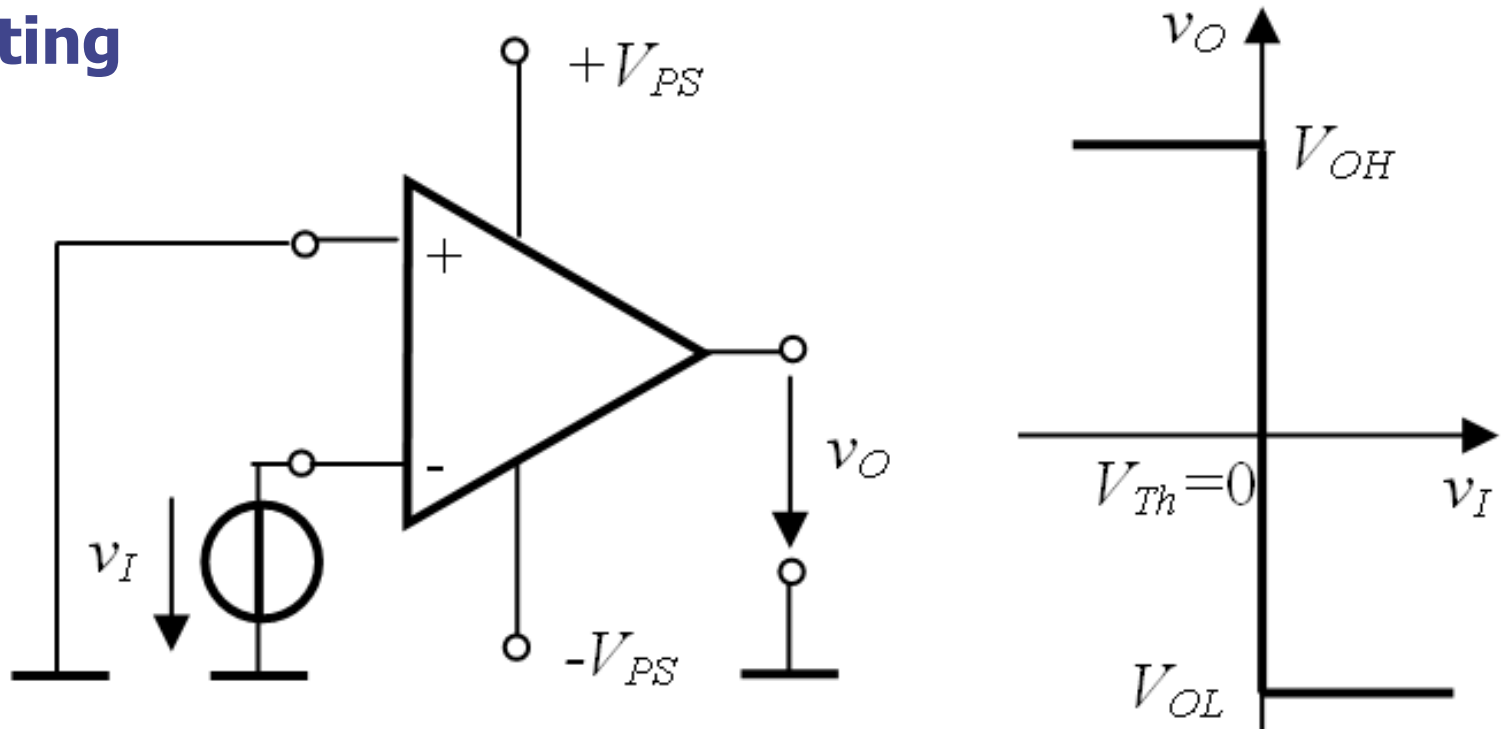


How does the output voltage look like if the input voltage is a sine wave with 3V amplitude and the supply is $\pm V_{PS} = \pm 12V$?

Comparators with $V_{Th} \neq 0$

noninverting



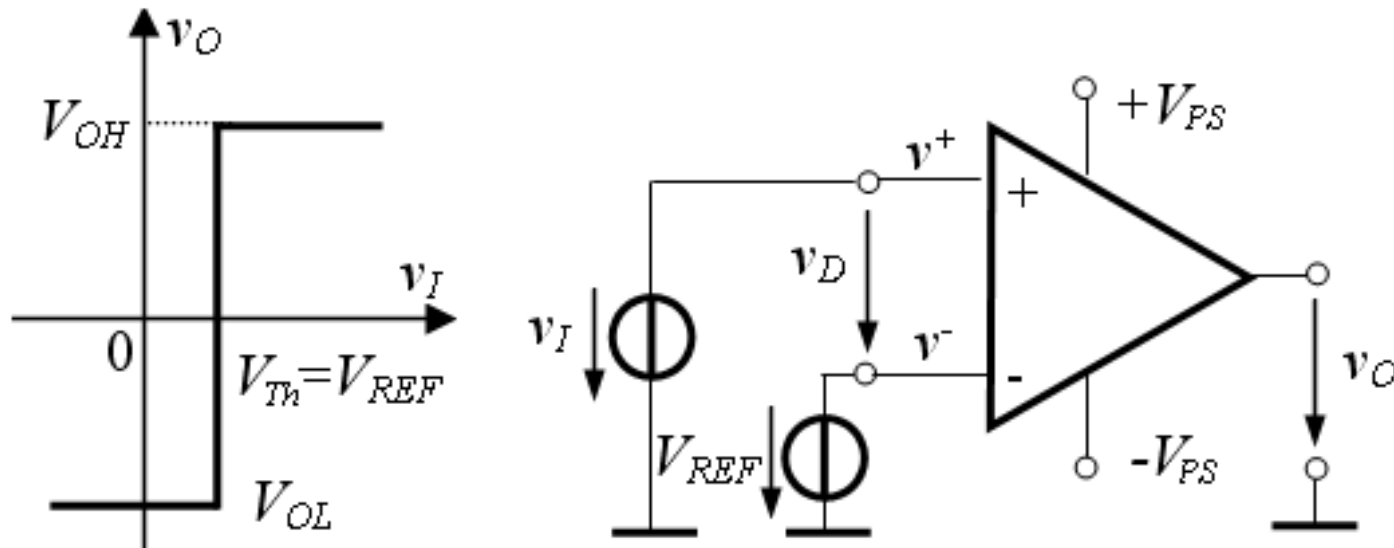


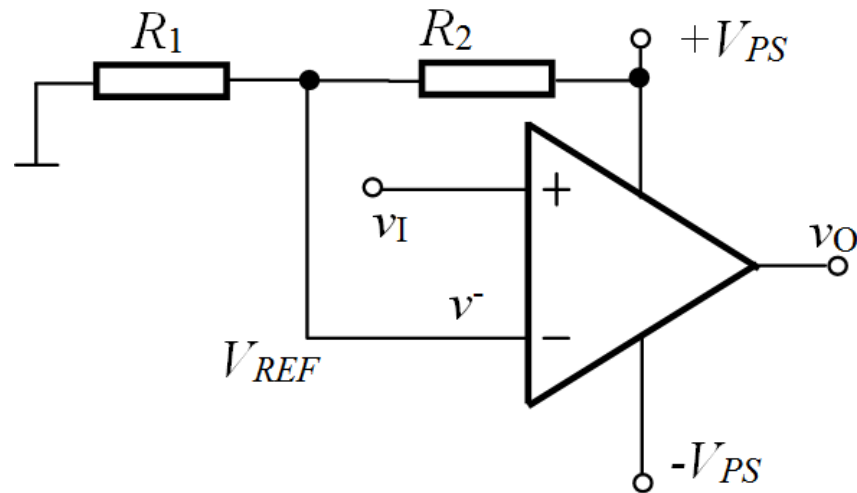How can V_{REF} be obtained from the available dc sources?



$$V_{REF} = \frac{R_1}{R_1 + R_2} V_{PS}$$

• Example

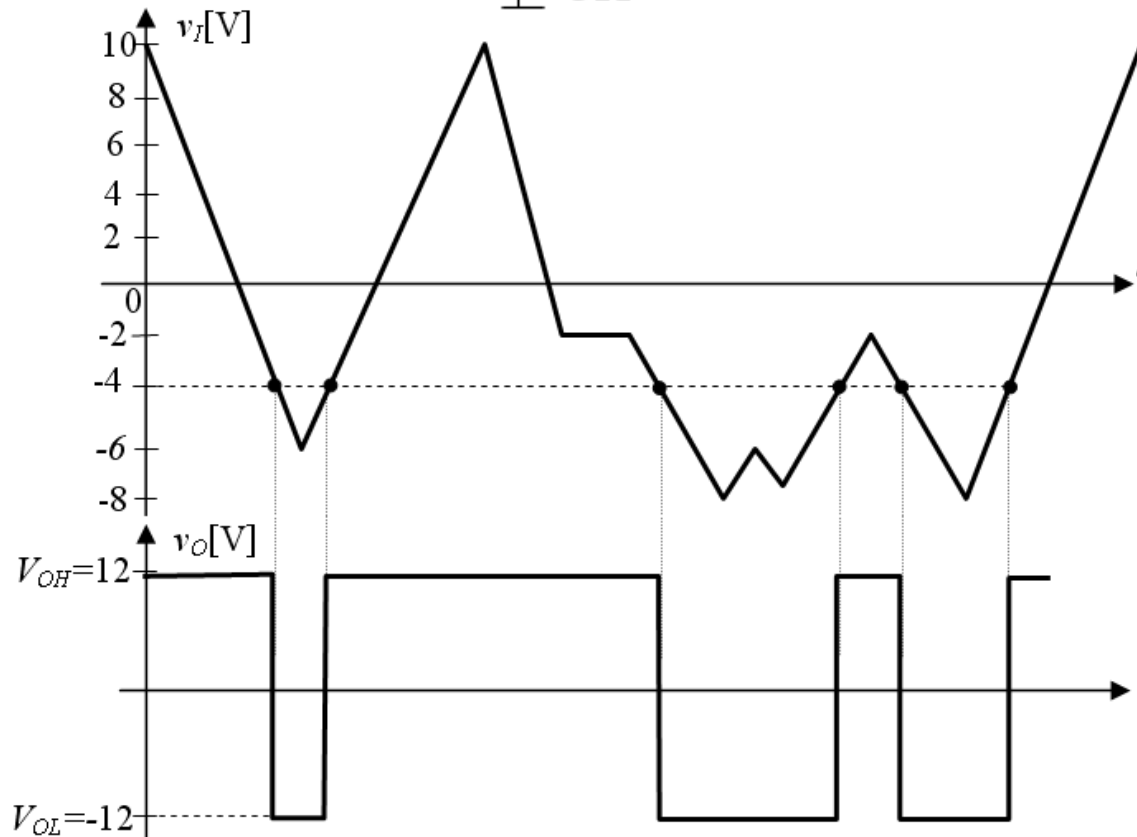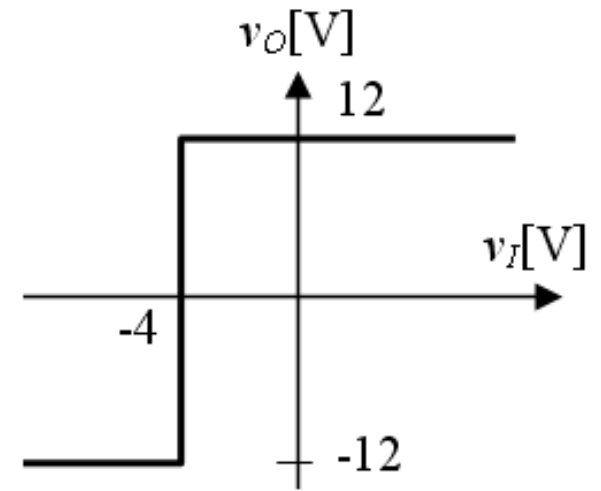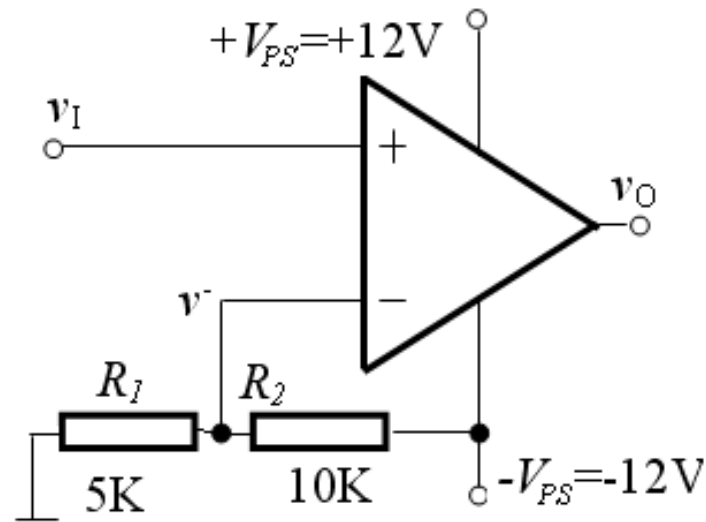

Redesign:

✓ inverting




✓ $V_{Th} = +6\text{V}$

? VTC

? $v_O(t)$

Comparators with $V_{Th} \neq 0$

inverting

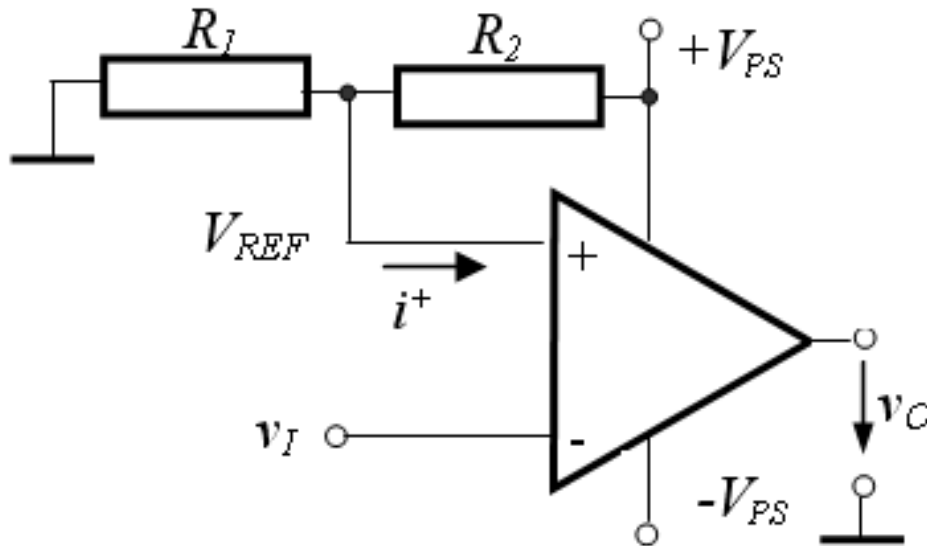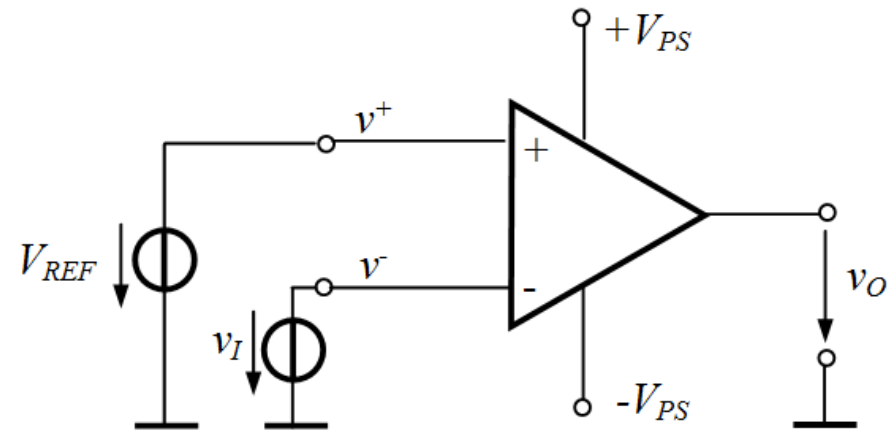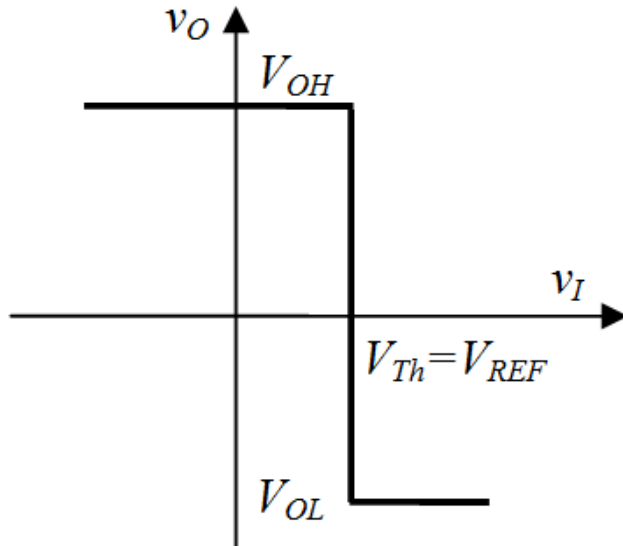

$i^+ \ll$ current through R_1, R_2 divider ($i^+ \cong 0$)

$$V_{REF} = \frac{R_1}{R_1 + R_2} V_{PS}$$

Op-amps specially intended for comparators

- general-purpose op-amp comparators
- **special class** of op-amp intended for comparators like:
LM306, LM 311 ,LM 399, LM 393, LM 339 :
 - **high** differential **voltages**
 - **very fast** response (very high slew rate)
 - usual comparators has **open collector** output (they necessitate an external resistor connected from the output towards a positive potential)
 - can have an extra **ground terminal** beside the usual supply terminals


Applications of simple comparators

- **Light sensor**
- **Interface between analog and logic circuits**
- **Obtaining rectangular signal from sinusoidal (triangular) signal**
- **Optical indicator for voltage level**
- **Pulse width modulation**
- **Signalizing and control circuit**
- **Analog to digital converter**
- **.....**

Light Sensor Circuit



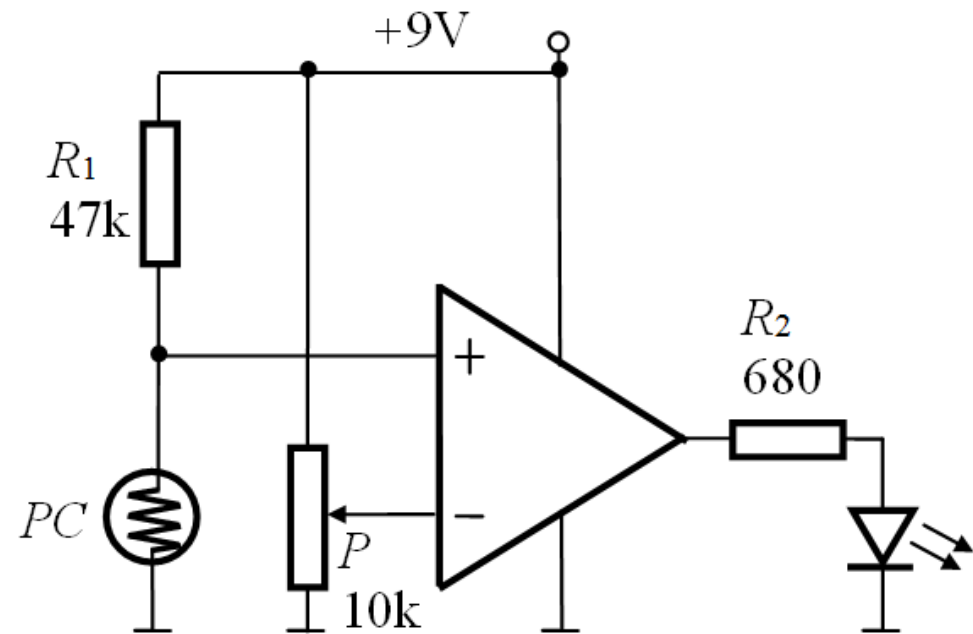PC: CdS
Photoconductive
Photocells
PDV-P8001




LDR - Light Dependent Resistor

Dark resistance (big): $R_D > 200 \text{ k}\Omega$

Illuminated resistance (small): $R_I \in (3; 11) \text{ k}\Omega$

When the light falling on the photocell (PC) is blocked, its resistance will increase and the voltage across PC will rise. When the voltage rises above 1/2 of the supply voltage the output of the comparator will turn ON and the LED will be lit.

Optical Indicator for Voltage Level

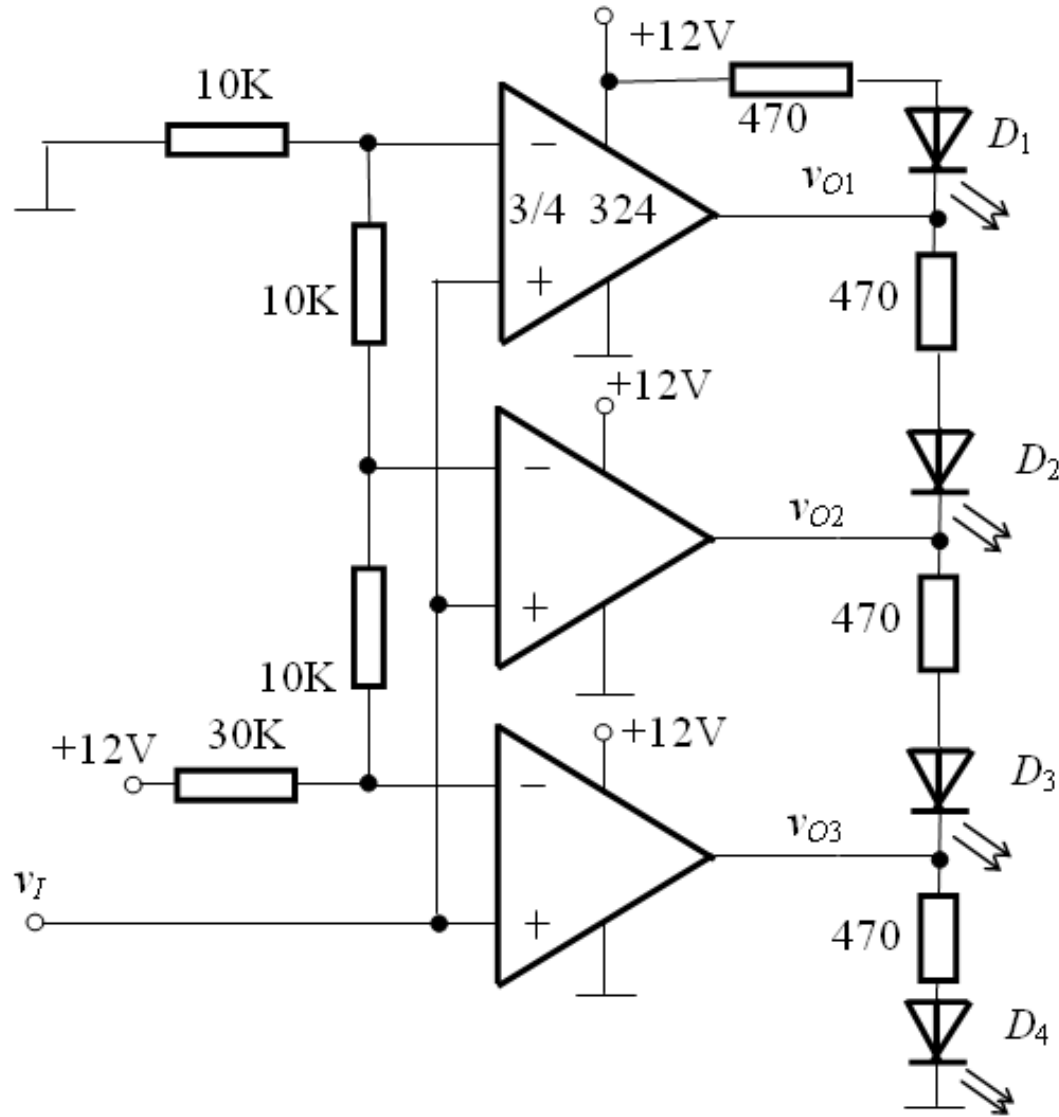

v_I	v_{O1}	v_{O2}	v_{O3}	
12V	12V	12V	12V	D_4 -on
6V	12V	12V	0V	D_3 -on
4V	12V	0V	0V	D_2 -on
2V	0V	0V	0V	D_1 -on
0V	0V	0V	0V	D_1 -on


Design a bar graph optical indicator for the voltage level using 5 LEDs

LED Bar Graph Dual Column Vu-meter display Decibel level 2x12

Bar graph LED indicating the audio level under 2X12 levels (stereo)

It contains 12 LEDs per side (7 green, 2 orange, 3 red).

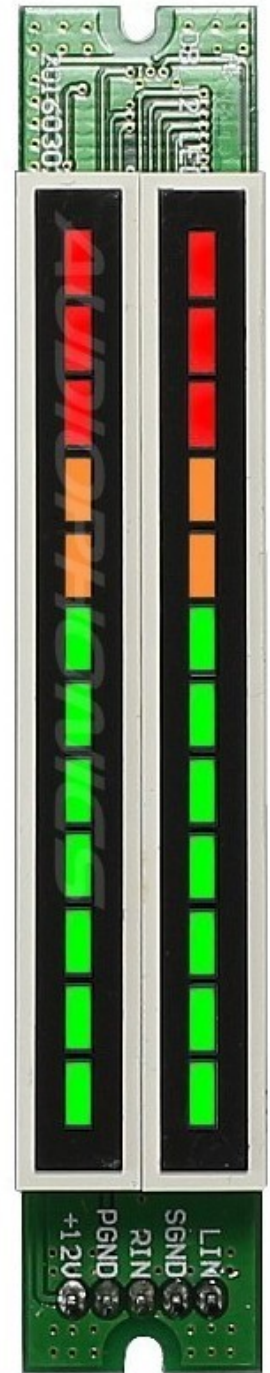The display speed and peak level can be adjusted individually by the button on the rear panel.



Analog to Logic Circuits Interfacing

High speed
voltage
comparator

