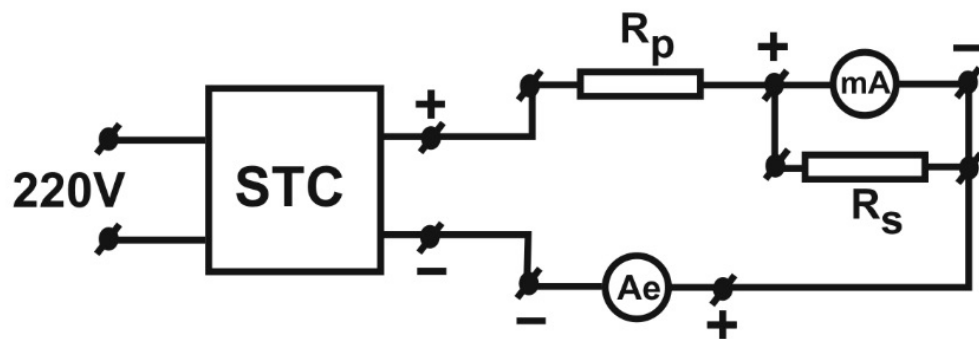



## Measurements and Actuators

## Extension of Domain

## 1. Two terminal connections

[illegible]

## 2. Four terminal connections

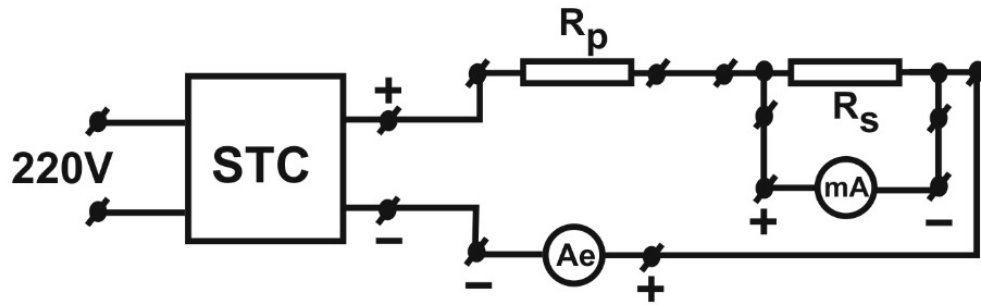[illegible]

**Formulas used for calculations:**

$$R_a = 10\Omega$$

$$I \text{ \& } I_e = [div] * \_\_\_ \rightarrow \text{for } I_{SN} = \_\_\_\_\_\_;$$

$$I \text{ \& } I_e = [div] * \_\_\_ \rightarrow \text{for } I_{SN} = \_\_\_\_\_\_;$$

$$I \text{ \& } I_e = [div] * \_\_\_ \rightarrow \text{for } I_{SN} = \_\_\_\_\_\_;$$

$$\varepsilon_a = I - I_e [mA];$$

$$\varepsilon_r = \frac{I - I_e}{I_e} * 100 [\%];$$

$$n' = n - \frac{\varepsilon_a}{I_a};$$

$$n'' = n - \frac{\varepsilon_a}{I_e};$$


$$R_c = \frac{3}{2} * \frac{n - n'}{(n-1)*(n'-2)} * R_a - \text{for ammeter circuit with simple shunts.}$$

$$R_c = \frac{1}{2} * \frac{n'' - n}{n-1} * R_a - \text{for ammeter circuit with double terminals.}$$

**Graphics to be traced for both tables on a single sheet:**

$$f(I) = \varepsilon_a;$$

$$f(I) = \varepsilon_r;$$

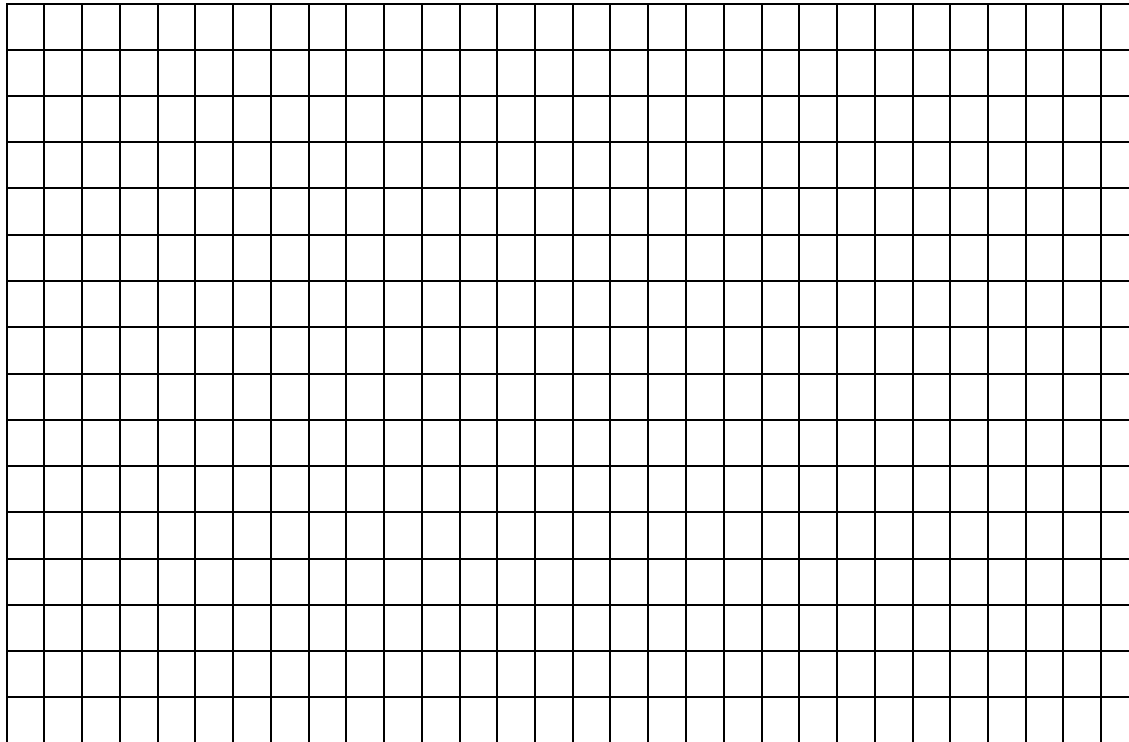

## Upstream AC experimental circuit with different loads

NR.	Meter	Range $X_N$	Max. defl. $\alpha_{max}$	Instr. Constant $C = \frac{X_N}{\alpha_{max}}$	Accuracy Class c	Max. abs. error $\varepsilon_{max} = \frac{cX_N}{100}$
	type	[X]	[div.]	[X/div]	[%]	[X]
1						
2						
3						

Range			$R_a$	$R_v$	$R_{wi}$	$R_{wu}$	$R_{aw}$	$R_{vw}$
ammeter	voltmeter	wattmeter	$\Omega$	$k\Omega$	$\Omega$	$k\Omega$		

**Formulas to be used for calculations:**

$$R_{aw} = R_a + R_{wi}$$

$$R_{vw} = R_v \parallel R_{wu} = \left( \frac{1}{R_v} + \frac{1}{R_{wu}} \right)^{-1}$$


Downstream Connection	Upstream Connection
$\Delta P_{aw} = R_{aw} * I^2$	$\Delta P_{aw} = \frac{U^2}{R_{vw}}$
$Z = \frac{\sqrt{U^2 - R_{aw}(2P - R_{aw}I^2)}}{I}$	$Z = \frac{U}{\sqrt{I^2 - \frac{1}{R_{vw}}(2P - \frac{U^2}{R_{vw}})}}$
$\cos\varphi_Z = \frac{P - R_{aw}I^2}{I\sqrt{U^2 - R_{aw}(2P - R_{aw}I^2)}}$	$\cos\varphi_Z = \frac{P - \frac{U^2}{R_{vw}}}{U\sqrt{I^2 - \frac{1}{R_{vw}}(2P - \frac{U^2}{R_{vw}})}}$

$$R_Z = Z\cos\varphi_Z$$


$$X_Z = Z\sin\varphi_Z$$

$$P_Z = P - R_{aw}I^2$$

### Upstream AC experimental circuit

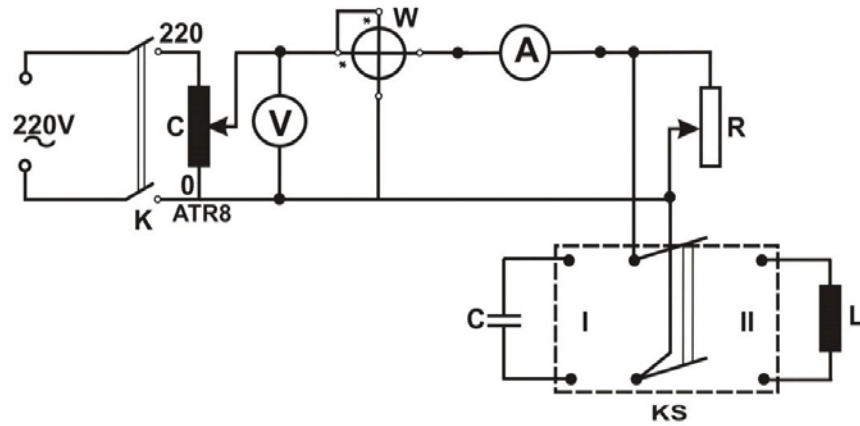
[illegible]

### Downstream AC experimental circuit

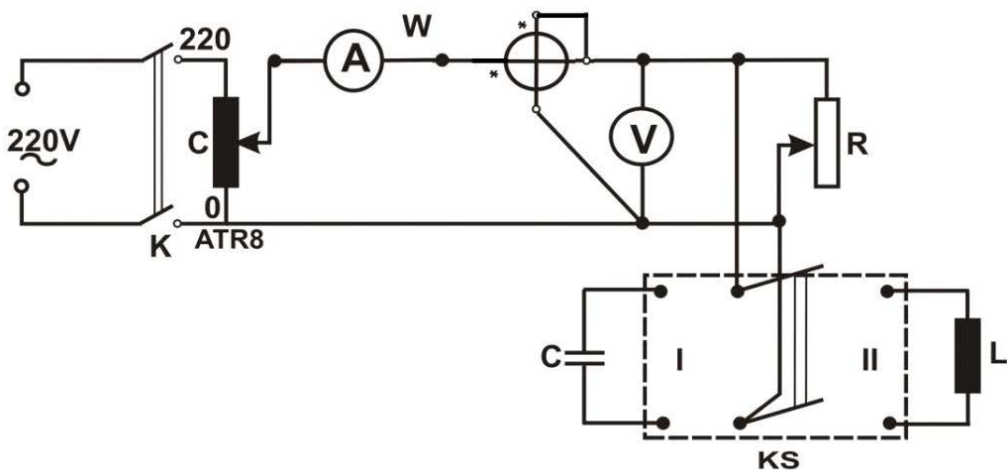[illegible]

ANALOG AND DIGITAL MEASUREMENT DEVICES

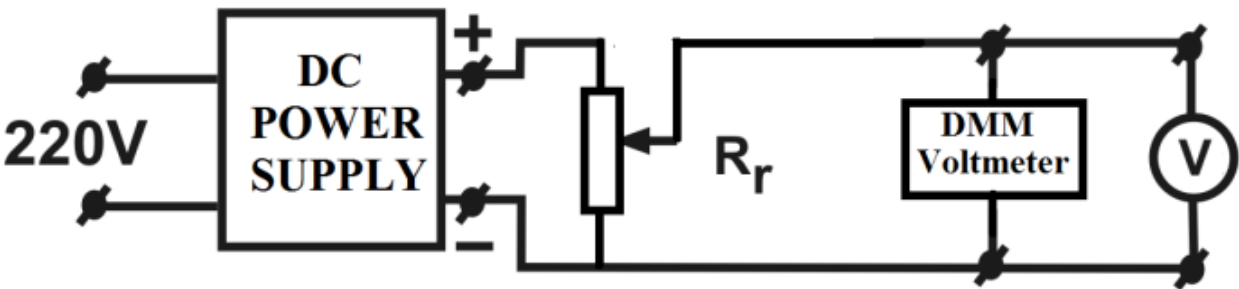1. Experimental circuit for digital DC voltmeter




DMM/Digital Voltmeter	Analog voltmeter	$DMM U_i$	$Analog U_i$		$DMM e_{max}$	$Analog e_{max}$	$DMM e_r[\%]$	$Analog e_r[\%]$	$DMM U_m$
			[V]				$\frac{e_{max}}{U_i} 100$	$\frac{e_{max}}{U_i} 100$	$U_i \pm e_{max}$
Range $U_N$ / Resolution	Range/ $U_N$ Resolution	[V]	[div]	[V]	[V]	[V]	[%]	[%]	[V]

$$Analog U_i = [div] * \frac{Range}{Resolution} = [div] * \text{———}$$

$$DMM: e_{max} = 0.012\% * U_i + 5 * digits, \text{ where } 1 \text{ digit} = \text{values from first column}$$

$$Analog: c = \frac{Range}{Resolution} = \text{———}; U_N = \text{———} V, e_{max} = \frac{c * U_N}{100}$$
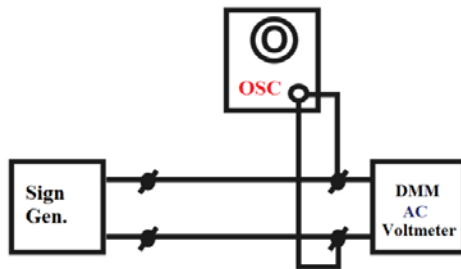
## 2. The measurement of periodical signals:



Waveform	Effective value (U)	Mean value ( $U_{mean}$ )	Crest factor. ( $k_c$ )	Form factor ( $k_f$ )	Distortion factor ( $k_d$ )
	$\frac{U_m}{\sqrt{2}}$	$\frac{2 \cdot U_m}{\pi}$	$\sqrt{2}$	$\frac{\pi}{2\sqrt{2}} = 1.11$	0
	$\frac{U_m}{\sqrt{3}}$	$\frac{U_m}{2}$	$\sqrt{3}$	$\frac{2}{\sqrt{3}} = 1.156$	0.12
	$U_m$	$U_m$	1	1	0.435
	$\frac{U_m}{\sqrt{3}}$	$\frac{U_m}{2}$	$\sqrt{3}$	$\frac{2}{\sqrt{3}}$	0.626


Pick three different values of Amplitudes (1-10V) on the Signal Generator and note them here:

\_\_\_\_\_ V; \_\_\_\_\_ V; \_\_\_\_\_ V.

Waveform	Pick coeff ( $k_v$ ) (table)	Shape coeff ( $k_f$ ) (table)	Indicated value ( $U_i$ )	Mean value $U_{mean} = \frac{U_i}{k_f \sin}$	RMS value $U = \frac{k_f}{k_f \sin} * U_i$	Max. value $U_m = \frac{k_f * k_c}{k_f \sin} * U_i$	Osc. Pk to pk ( $U_{v-p}$ )
			[ V ]	[ V ]	[ V ]	[ V ]	[ V ]



## Wheatstone Bridge

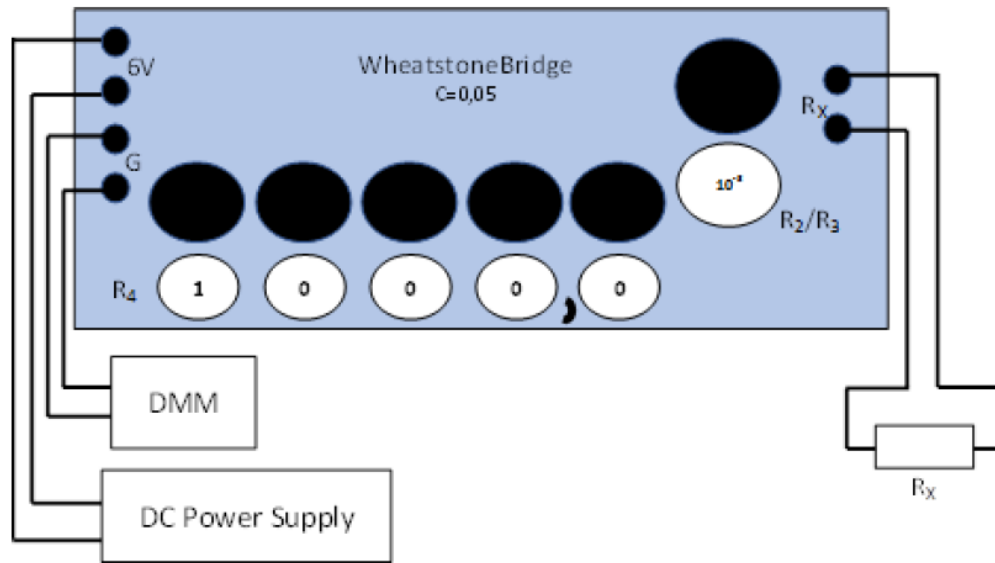

Measured resistance	The ND (null detector) $\alpha$ deviation after the adjustment of:					
	$R_2/R_3$	The first decade (the most significant)	The second decade	The third Decade	The fourth decade	The fifth Decade
	[mV]	$\alpha_1$ [mV]	$\alpha_2$ [mV]	$\alpha_3$ [mV]	$\alpha_4$ [mV]	$\alpha_5$ [mV]
$R_1$						
$R_2$						
$R_3$						
$R_4$						
$R_5$						
$R_6$						

Meas R esist. $R_{xN}$	Measured values						Computed values						
	$R_2/R_3$ (1)	$R_{4e}$ (2)	$\alpha_l$ left	$R_{4l}$ left	$\alpha_r$ right	$R_{4r}$ right	$R_{4i}$	$R_{mas}$ (1) *(2)	$e_{rc}$	$e_{rd}$	$e_{rRx}$	$e_a$	$R_x$
	[ $\Omega/\Omega$ ]	[ $\Omega$ ]	[div]	[ $\Omega$ ]	[div]	[ $\Omega$ ]	[ $\Omega$ ]	[ $\Omega$ ]	[%]	[%]	[%]	[%]	[ $\Omega$ ]
$R_1$										0			
$R_2$										0			
$R_3$										0			
$R_4$										0			
$R_5$										0			
$R_6$										0			

Meas. resist. $R_{xN}$	$R_2/R_3$	$\alpha_l(\alpha_j)$ [mV]	$R_{4l}(R_{4j})$	$\alpha_r(\alpha_j + 1)$ [mV]	$R_{4r}(R_{4j} + 1)$	$S_l$	$S_r$	S
$R_1$								
$R_2$								
$R_3$								
$R_4$								
$R_5$								
$R_6$								

$$e_{rRx} = e_{rc} + e_{rd}$$

$$e_a = \frac{e_{rRx} R_{mas}}{100}$$

$$R_X = R_{mas} \pm e_a$$

$$S_r = \frac{\alpha_r}{\frac{R_{4r} - R_{4e}}{R_{4e}}};$$

$$S_l = \frac{\alpha_l}{\frac{R_{4e} - R_{4l}}{R_{4e}}};$$

$$S = \frac{\alpha_r - \alpha_l}{\frac{R_{4r} - R_{4l}}{R_{4e}}}$$