

Electrotechnics

ET

Course 9

Year I-ISA English

Associate Professor Dr Eng Ec Claudia PĂCURAR

Claudia.Pacurar@ethm.utcluj.ro

= Course 9 =

ELECTRICAL CIRCUITS IN HARMONIC REGIME

Linear Electric Circuits in Permanent Sinusoidal Regime

Phasors Diagrams. Applications

Complex Equivalent Impedances. Applications

Phasors Diagrams

❑ **There exist two types of phasors diagrams:**



■ **Phasors Diagrams at Scale:**

- **are drawn respecting the effective values and the phase shift angles of the voltages and currents;**


■ **Phasors Diagrams of Principle:**

- **are drawn respecting the phase shifts introduced by resistors (0°), inductors (90°), capacitors (-90°) and adding voltages (in series) and currents (in parallel) according to the parallelogram rule;**



❑ Ideal resistor:

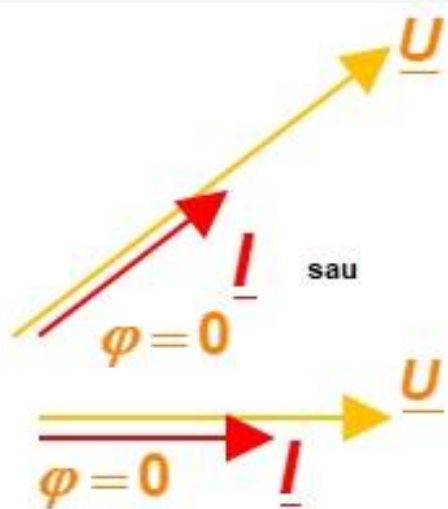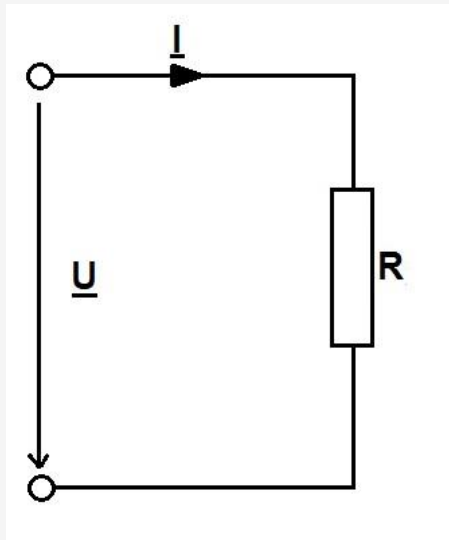

❑ Ideal inductor:

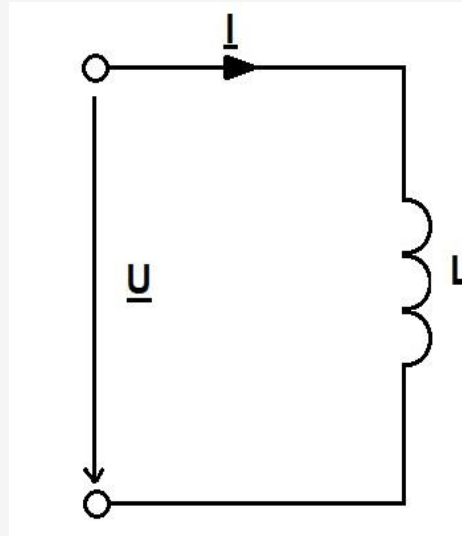

❑ Ideal capacitor:

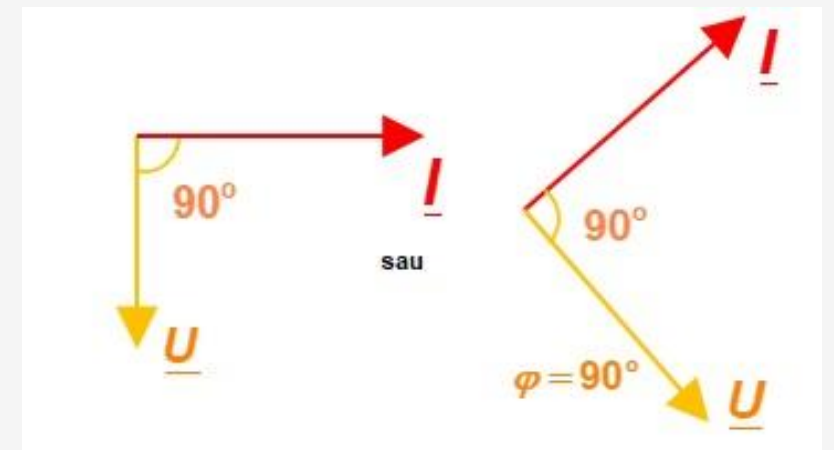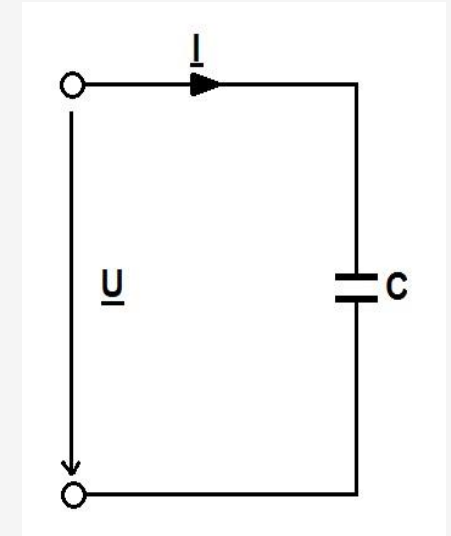




Applications

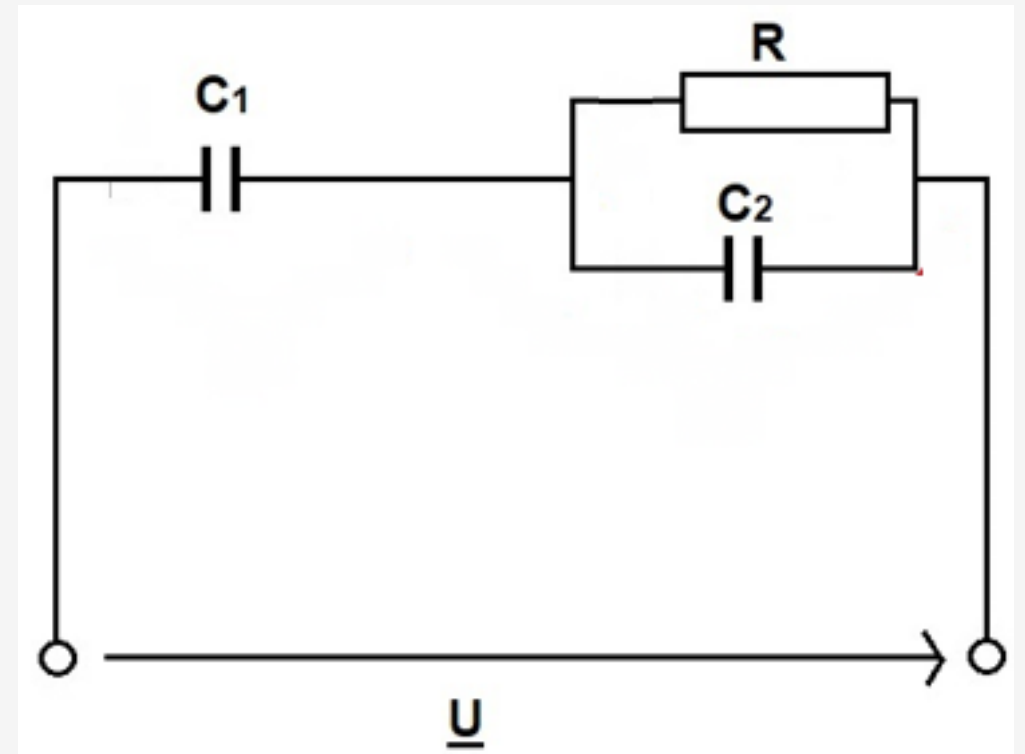Problem 1




Draw the phasors diagram of principle for to the circuit from the figure:



Solution:




Solution:

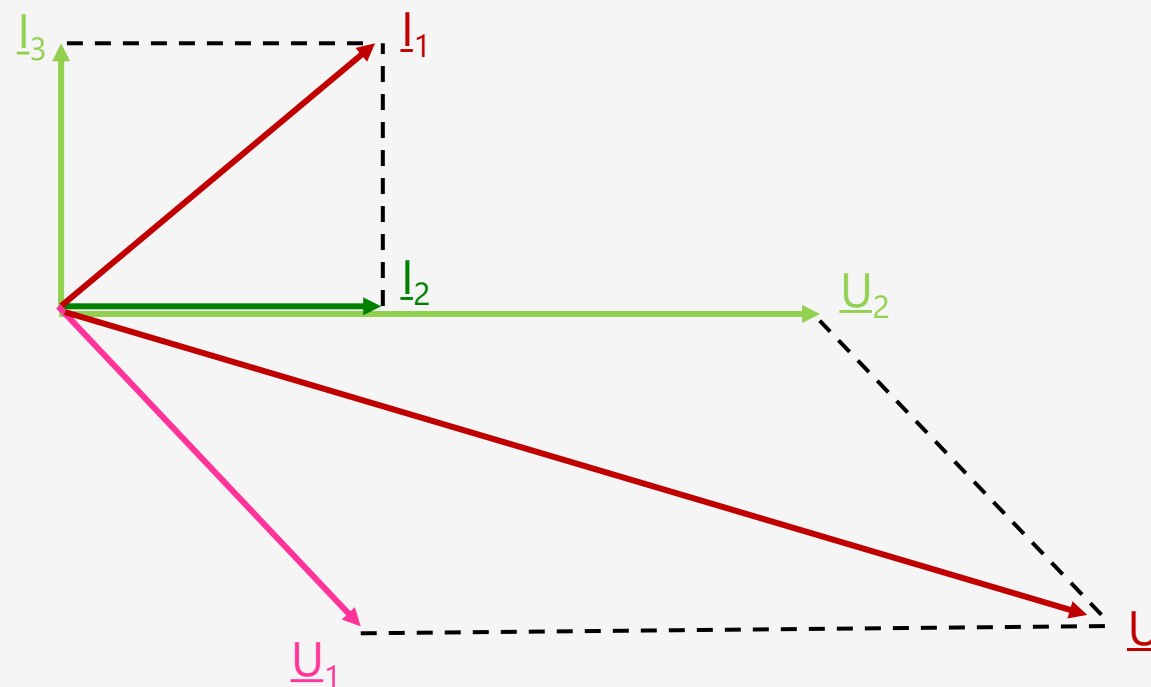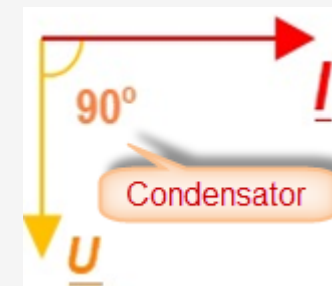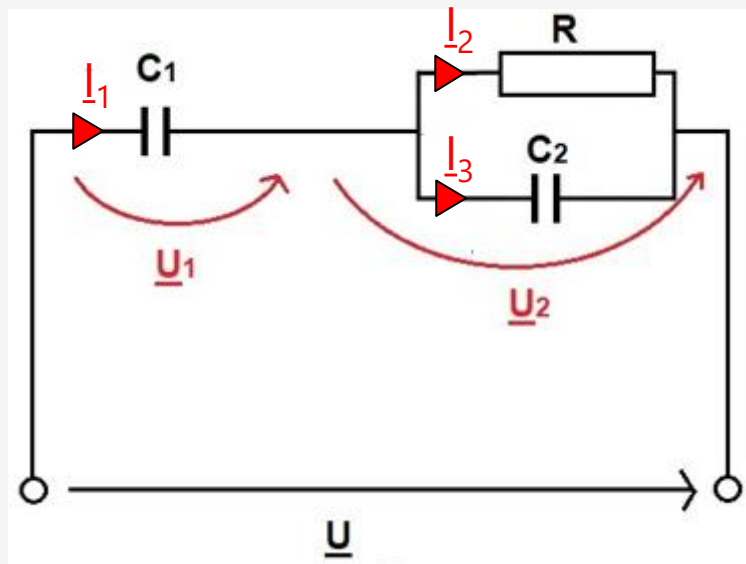

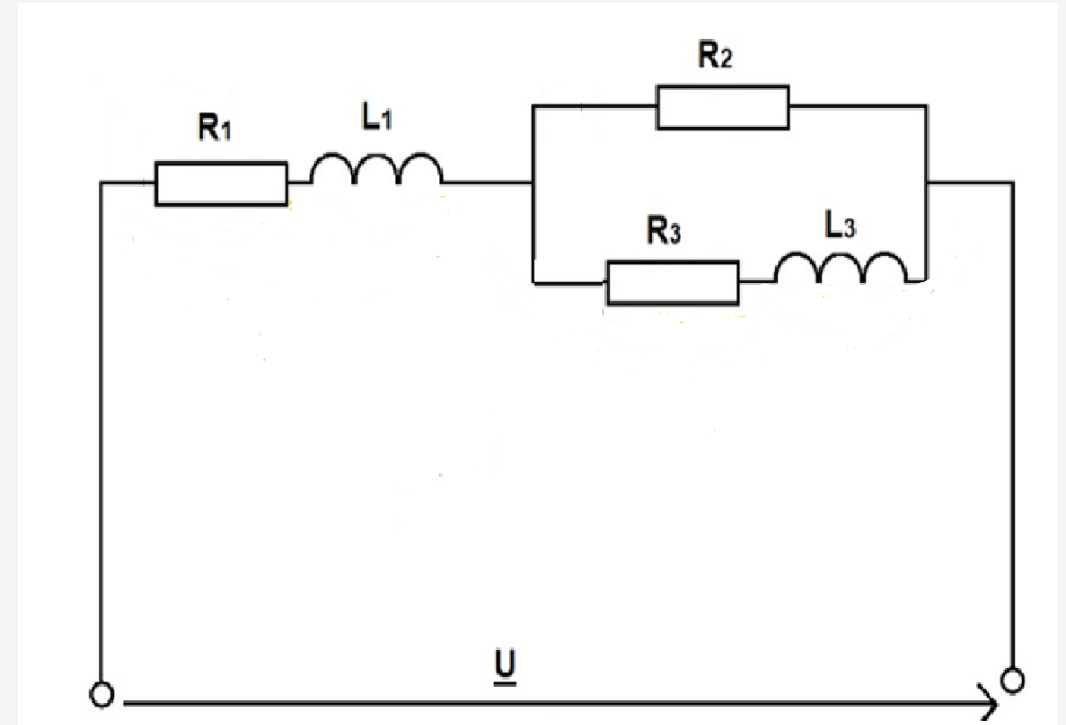Problem 2




Draw the phasors diagram of principle for the circuit from the figure:



Solution:




Solution:

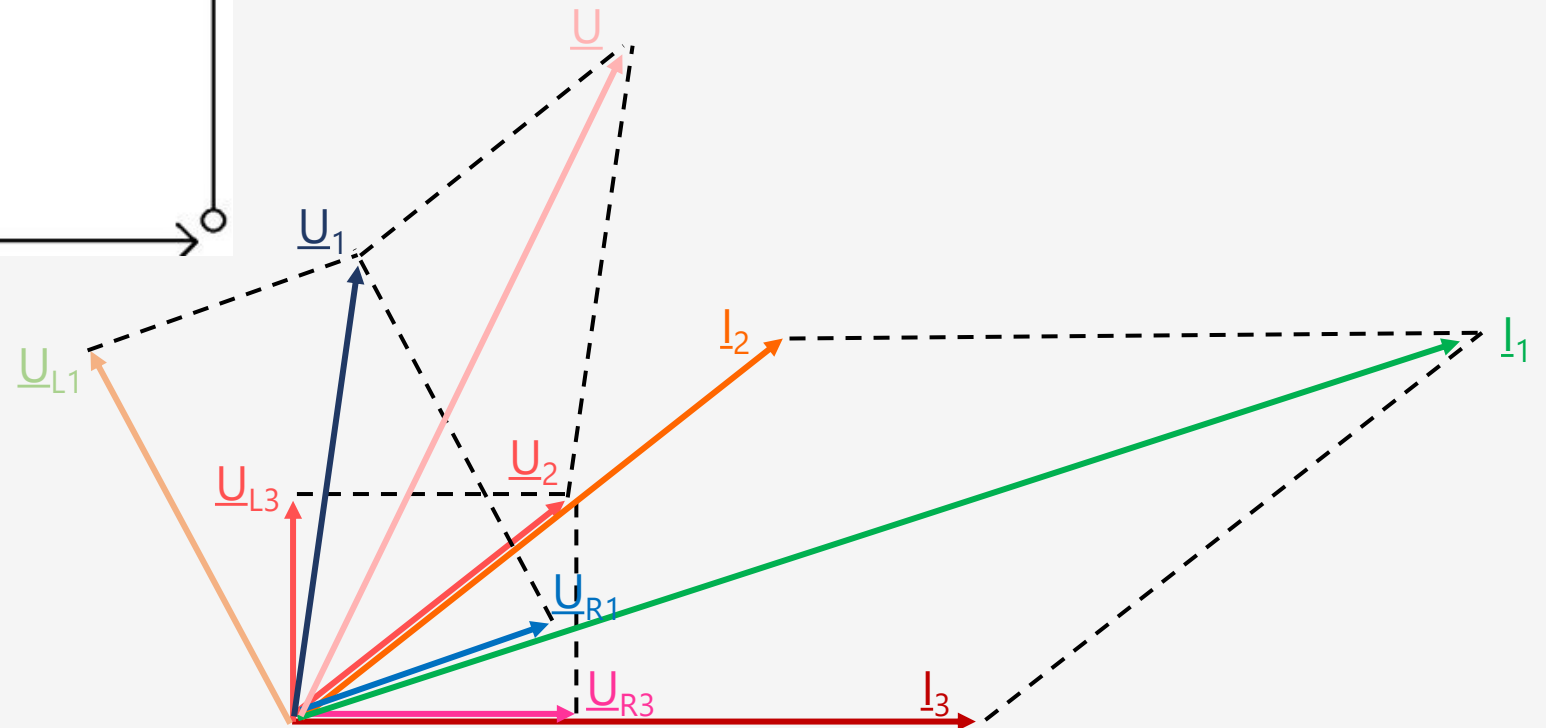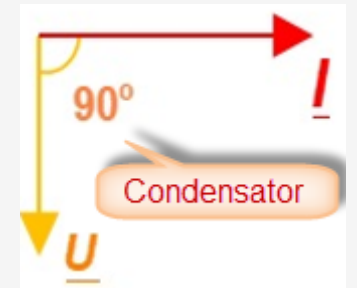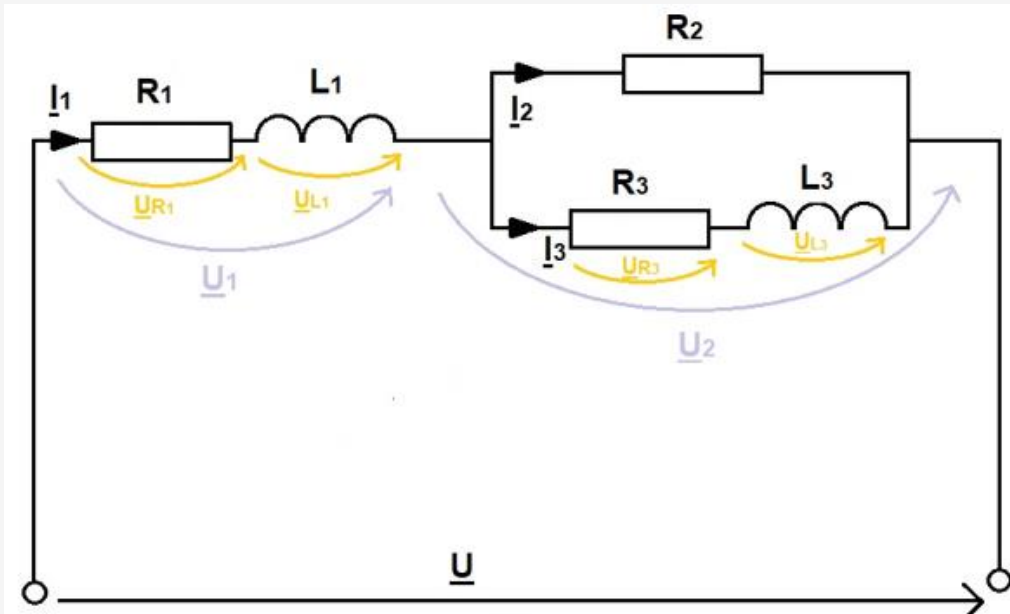


Homework

Draw the phasors diagrams of principle for the circuits from the figures:


a)

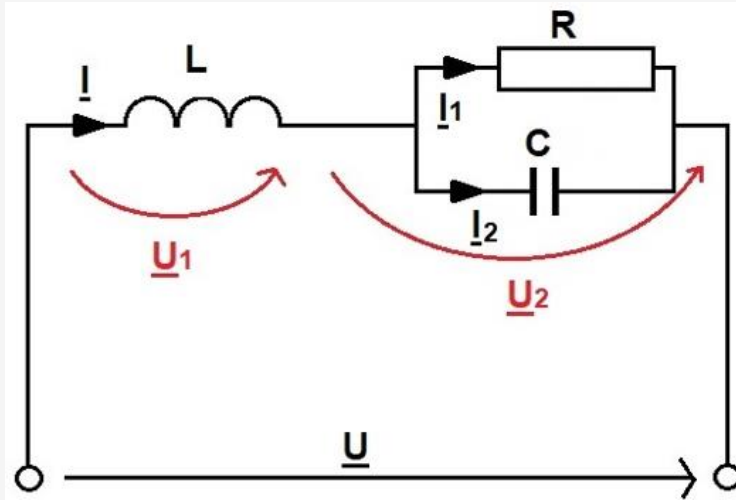

b)

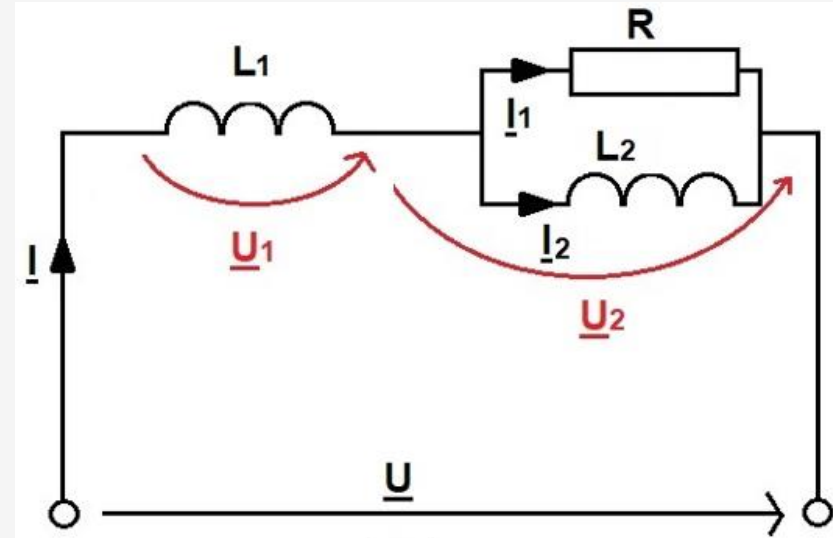


c)

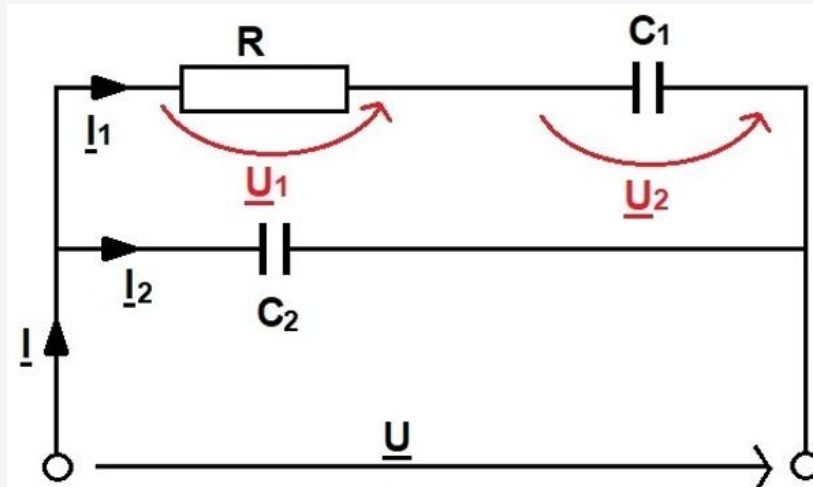

Complex Equivalent Impedances

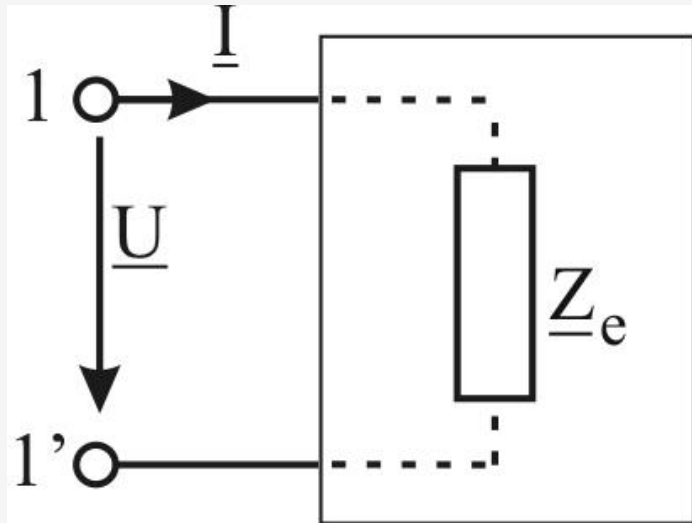Equivalent Impedance for Connections without Inductive Coupling



- Equivalent Complex Impedance:

$$\underline{Z}_e = \frac{\underline{U}}{\underline{I}} = Z_e e^{j\varphi_e} = R_e + jX_e$$

- Equivalent Complex Admittance:

$$\underline{Y}_e = \frac{1}{\underline{Z}_e} = \frac{\underline{I}}{\underline{U}} = Y_e e^{-j\varphi_e} = G_e - jB_e$$

1. Passive Branches without Inductive Coupling

A) Series Circuits (Connections)

$$\underline{U} = \underline{U}_1 + \underline{U}_2 + \dots + \underline{U}_n$$


$$\underline{U} = \underline{Z}_1 \underline{I} + \underline{Z}_2 \underline{I} + \dots + \underline{Z}_n \underline{I} = \underline{I} \sum_{k=1}^n \underline{Z}_k$$

$$\Rightarrow \underline{Z}_e = \frac{\underline{U}}{\underline{I}} = \sum_{k=1}^n \underline{Z}_k \Rightarrow \underline{Z}_e = R_e + jX_e$$


$$\Rightarrow R_e = \sum_{k=1}^n R_k > 0$$

$$\Rightarrow X_e = \sum_{k=1}^n X_k >< 0$$
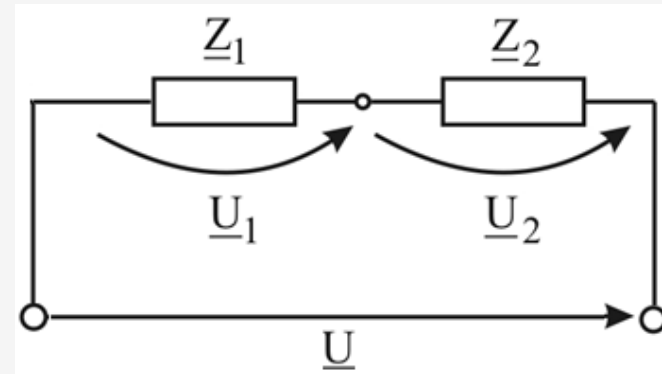
$$\Rightarrow \sum_{k=1}^n \underline{Z}_k = \sum_{k=1}^n R_k + j \sum_{k=1}^n X_k \quad n=2$$


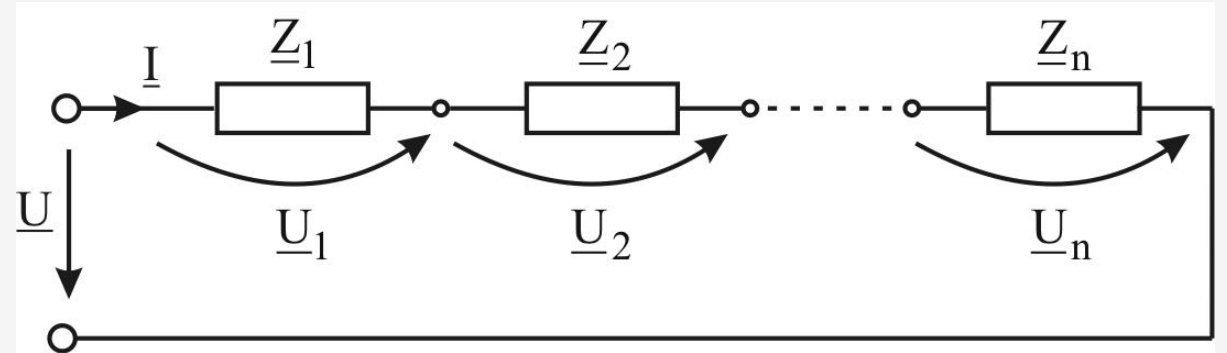
$$\Rightarrow \underline{Z}_e = \underline{Z}_1 + \underline{Z}_2$$




Voltage Divider

$$\underline{I} = \frac{\underline{U}_k}{\underline{Z}_k} = \frac{\underline{U}}{\underline{Z}_e} = \frac{\underline{U}}{\sum_{k=1}^n \underline{Z}_k}$$



$$\underline{U}_k = \frac{\underline{Z}_k}{\sum_{k=1}^n \underline{Z}_k} \underline{U}$$


$n = 2$

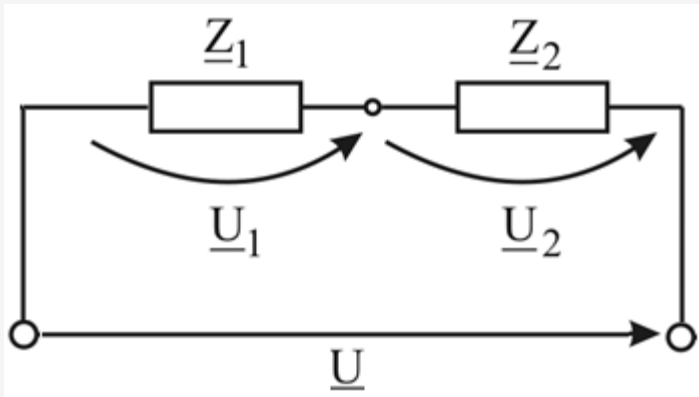

$$\underline{U}_1 = \frac{\underline{Z}_1}{\underline{Z}_1 + \underline{Z}_2} \underline{U} = \frac{\underline{Y}_2}{\underline{Y}_1 + \underline{Y}_2} \underline{U}$$

$$\underline{U}_2 = \frac{\underline{Z}_2}{\underline{Z}_1 + \underline{Z}_2} \underline{U} = \frac{\underline{Y}_1}{\underline{Y}_1 + \underline{Y}_2} \underline{U}$$

b) Parallel Circuits (Connections)

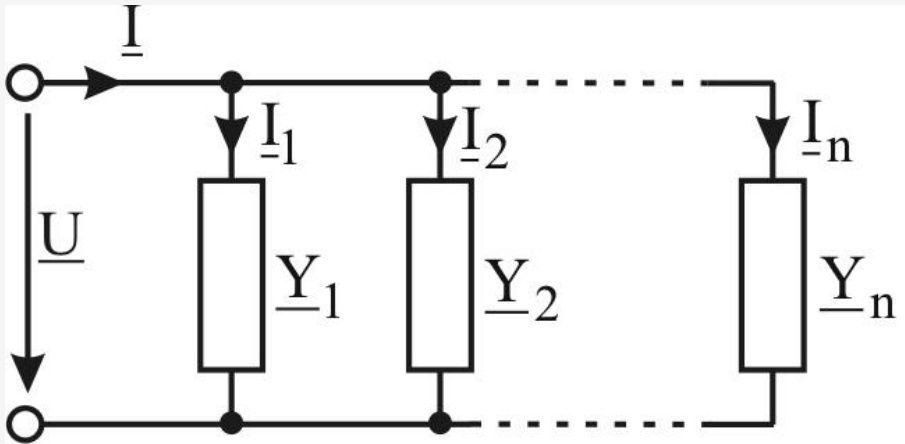

$$\underline{I} = \underline{I}_1 + \underline{I}_2 + \dots + \underline{I}_n$$

$$\underline{I} = \underline{Y}_1 \underline{U} + \underline{Y}_2 \underline{U} + \dots + \underline{Y}_n \underline{U}$$

$$\underline{I} = \underline{U}(\underline{Y}_1 + \underline{Y}_2 + \dots + \underline{Y}_n) = \underline{U} \sum_{k=1}^n \underline{Y}_k$$


$$\Rightarrow \underline{Y}_e = \frac{\underline{I}}{\underline{U}} = \sum_{k=1}^n \underline{Y}_k$$

$$\Rightarrow \underline{Y}_e = G_e - jB_e$$

$$\Rightarrow G_e = \sum_{k=1}^n G_k > 0$$

$$\Rightarrow B_e = \sum_{k=1}^n B_k >< 0$$

$n = 2$

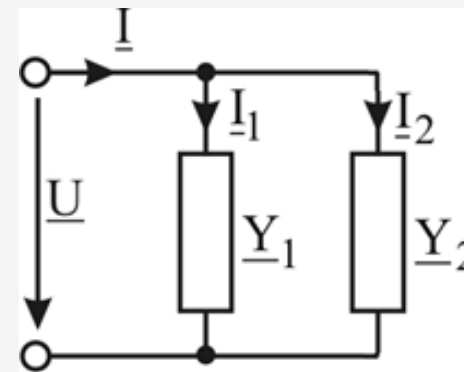

$$\Rightarrow \underline{Z}_e = \frac{\underline{Z}_1 \cdot \underline{Z}_2}{\underline{Z}_1 + \underline{Z}_2}$$


Current Divider

$$\underline{U} = \frac{\underline{I}_k}{\underline{Y}_k} = \frac{\underline{I}}{\underline{Y}_e} = \frac{\underline{I}}{\sum_{k=1}^n \underline{Y}_k}$$



$$\underline{I}_k = \frac{\underline{Y}_k}{\sum_{k=1}^n \underline{Y}_k} \underline{I}$$


$n = 2$

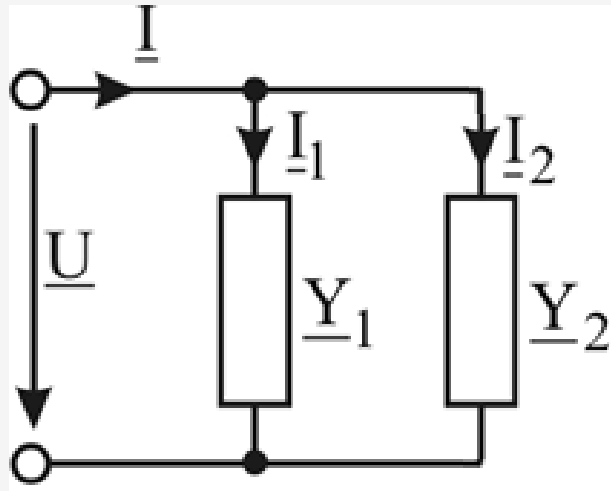

$$\underline{I}_1 = \frac{\underline{Y}_1}{\underline{Y}_1 + \underline{Y}_2} \underline{I} = \frac{\underline{Z}_2}{\underline{Z}_1 + \underline{Z}_2} \underline{I}$$

$$\underline{I}_2 = \frac{\underline{Y}_2}{\underline{Y}_1 + \underline{Y}_2} \underline{I} = \frac{\underline{Z}_1}{\underline{Z}_1 + \underline{Z}_2} \underline{I}$$

C) Mixt Connection

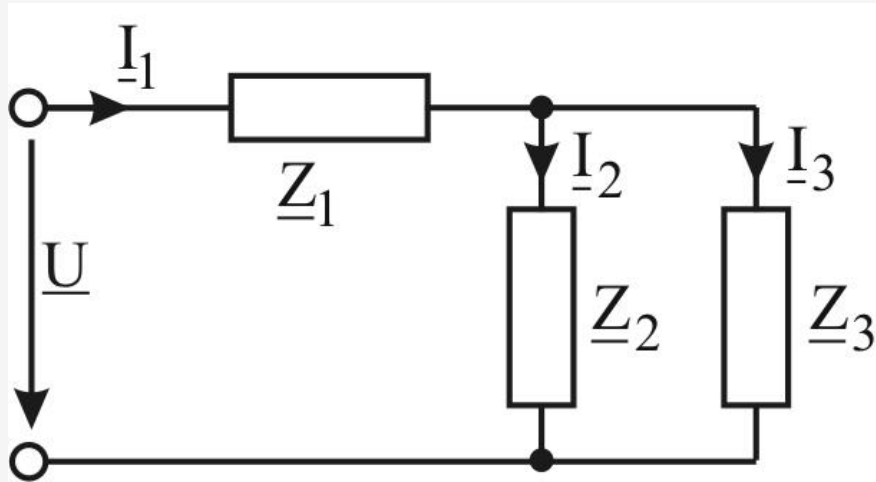


$$\underline{Z}_{2,3} = \frac{1}{\frac{1}{\underline{Z}_2} + \frac{1}{\underline{Z}_3}} = \frac{\underline{Z}_2 \underline{Z}_3}{\underline{Z}_2 + \underline{Z}_3}$$

$$\underline{Z}_e = \underline{Z}_1 + \underline{Z}_{2,3} = \underline{Z}_1 + \frac{\underline{Z}_2 \underline{Z}_3}{\underline{Z}_2 + \underline{Z}_3} = \frac{\underline{Z}_1 \underline{Z}_2 + \underline{Z}_2 \underline{Z}_3 + \underline{Z}_1 \underline{Z}_3}{\underline{Z}_2 + \underline{Z}_3}$$

2. Passive Branches with Inductive Couplings

A) Series Connection

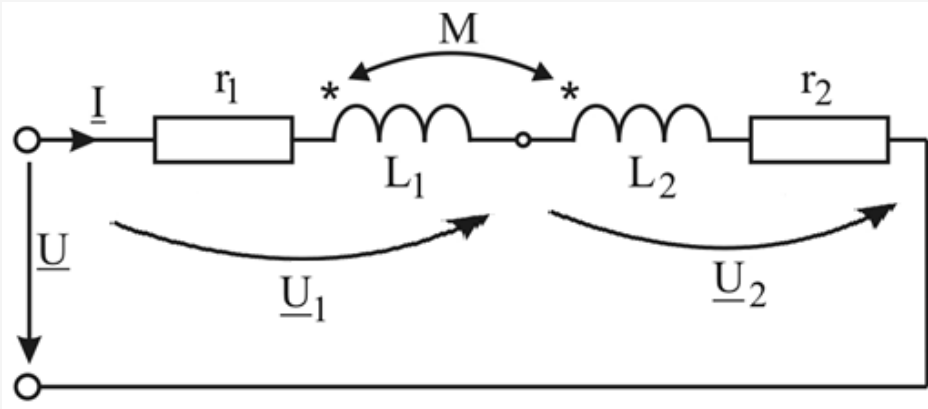

■ coupling coefficient is:

$$k = \frac{|M|}{\sqrt{L_1 L_2}} \leq 1$$

■ Applying Ohm's Law: $\underline{U}_1 = r_1 \underline{I} + j\omega L_1 \underline{I} + j\omega M \underline{I}$
 $\underline{U}_2 = r_2 \underline{I} + j\omega L_2 \underline{I} + j\omega M \underline{I}$ $\Rightarrow \underline{U} = \underline{I}[(r_1 + r_2) + j\omega(L_1 + L_2 + 2M)]$

\Rightarrow Equivalent impedance: $\underline{Z}_e = (r_1 + r_2) + j\omega(L_1 + L_2 + 2M)$

$$\underline{Z}_e = R_e + jX_e \quad R_e = r_1 + r_2 \quad L_e = L_1 + L_2 + 2M$$

■ if $M < 0$: $\Rightarrow L'_e = L_1 + L_2 - 2M$

- Equivalent inductivity is always a positive parameter

The elimination rule (desfacere) of the magnetic coupling between 2 inductors

❖ Additional Coupling

- the marked terminals are asymmetric to the common point




❖ Differential Coupling

- the marked terminals are symmetric to the common point



b) Parallel connection

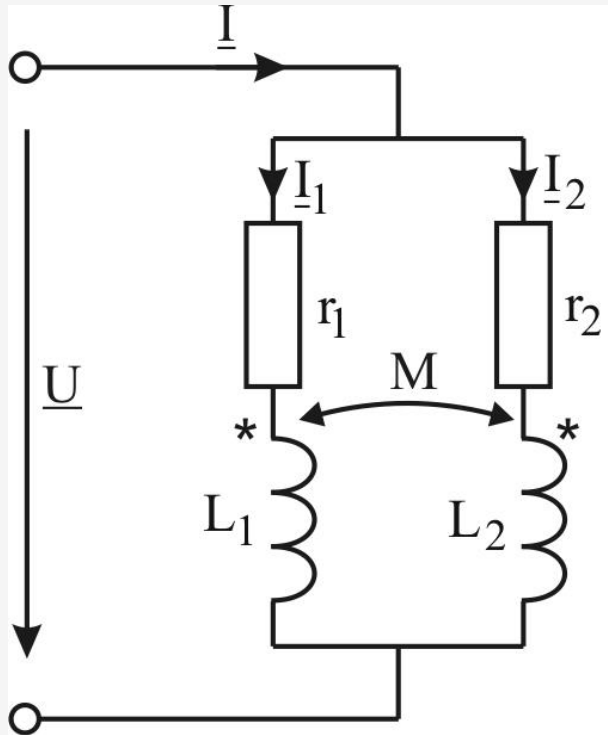

$$\underline{U} = (r_1 + j\omega L_1)\underline{I}_1 + j\omega M\underline{I}_2 = \underline{Z}_1\underline{I}_1 + \underline{Z}_M\underline{I}_2$$

$$\underline{U} = (r_2 + j\omega L_2)\underline{I}_2 + j\omega M\underline{I}_1 = \underline{Z}_M\underline{I}_1 + \underline{Z}_2\underline{I}_2$$

$$\underline{Z}_1 = r_1 + j\omega L_1$$

$$\underline{Z}_2 = r_2 + j\omega L_2$$


$$\underline{Z}_M = j\omega M$$

$$\underline{Z}_e = \frac{\underline{U}}{\underline{I}} = \frac{\underline{U}}{\underline{I}_1 + \underline{I}_2} \Rightarrow \underline{Z}_e = \frac{\underline{Z}_1\underline{Z}_2 - \underline{Z}_M^2}{\underline{Z}_1 + \underline{Z}_2 \mp 2\underline{Z}_M}$$

The elimination rule (desfacere) of the magnetic coupling between 2 inductors


❖ Additional Coupling

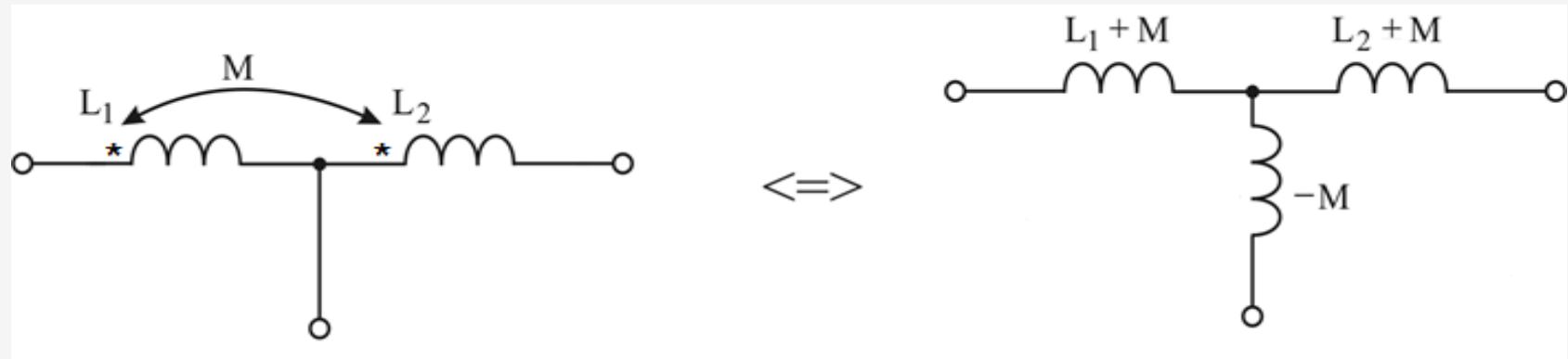- the marked terminals are asymmetric to the common point



❖ Differential Coupling

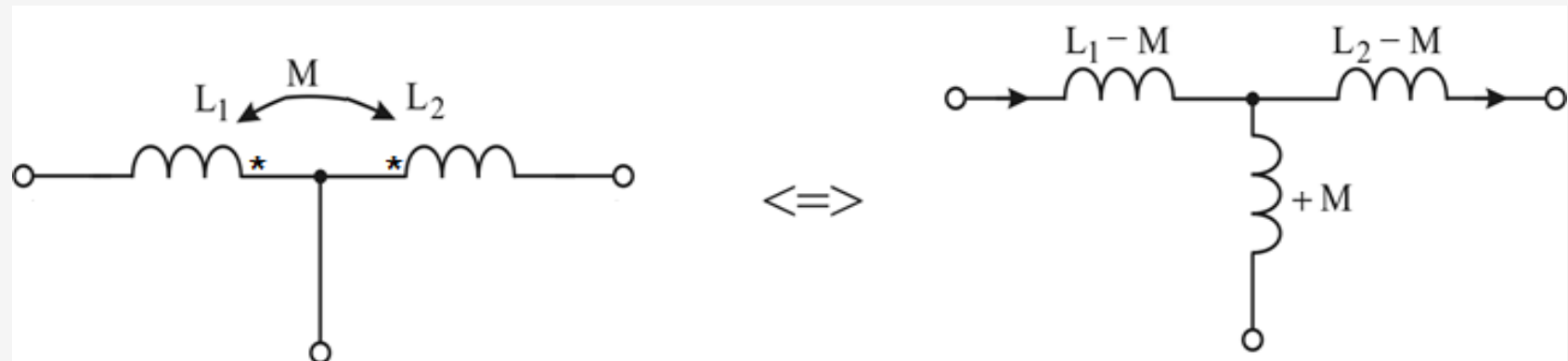- the marked terminals are symmetric to the common point





Applications

Problem 3

Find the currents, voltages and powers and draw the phasors diagram for the circuit, knowing that:


$$u(t) = 220\sqrt{2} \sin(\omega \cdot t + 0^\circ) [V];$$

$$f = 50 [\text{Hz}];$$

$$R = 60 [\Omega];$$

$$L = 0.2 [\text{H}];$$

$$C = 60 [\mu\text{F}].$$

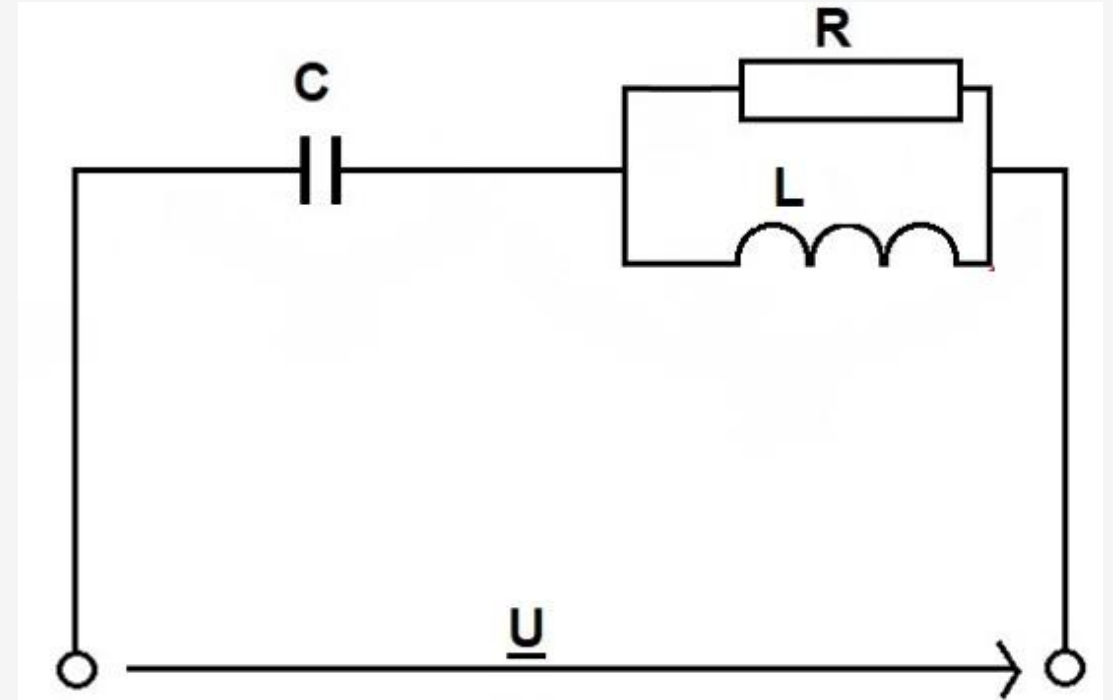

Solution:



Solution:

- the supply voltage is:

$$u(t) = 220\sqrt{2} \sin(\omega \cdot t + 0^\circ) [V]$$

- we write it in simplified complex:


$$\left. \begin{array}{l} U = \frac{220\sqrt{2}}{\sqrt{2}} = 220 \\ \gamma_u = 0^\circ \end{array} \right\} \Rightarrow \underline{U} = U \cdot e^{j\gamma_u} = U \angle \gamma_u$$

$$\Rightarrow \underline{U} = 220 \cdot e^{j \cdot 0^\circ} = 220 \cdot (\cos 0^\circ + j \cdot \sin 0^\circ) \Rightarrow \boxed{\underline{U} = 220, [V]}$$

- pulsation :

$$\omega = 2 \cdot \pi \cdot f \Rightarrow \omega = 2 \cdot \pi \cdot 50 = 2 \cdot 3,14 \cdot 50$$
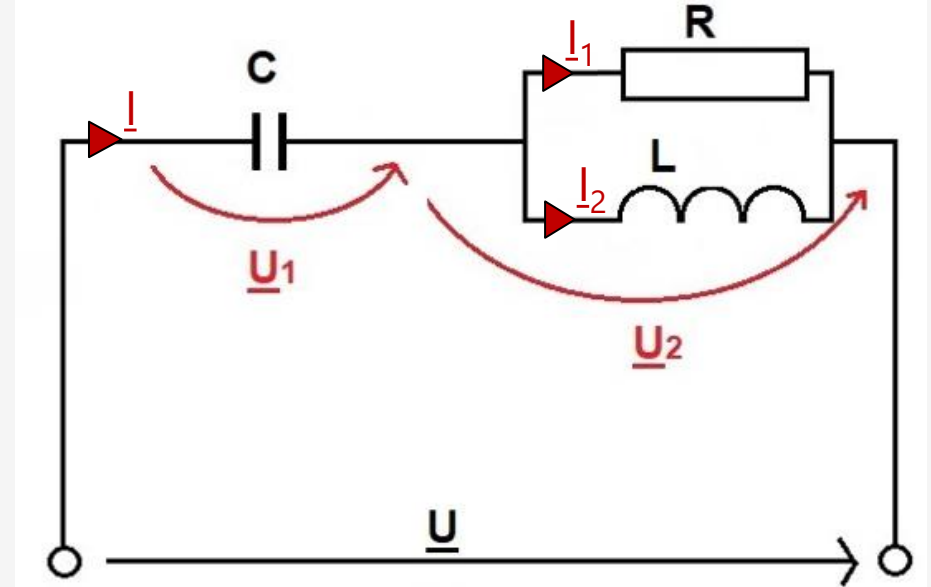
$$\Rightarrow \boxed{\omega = 314, \left[\frac{rad}{s} \right]}$$




- we calculate the **impedances of each component** of the circuit:

$$\left. \begin{array}{l} \underline{Z}_R = R \\ R = 60 [\Omega] \end{array} \right\} \Rightarrow \boxed{\underline{Z}_R = 60, [\Omega]}$$

$$\left. \begin{array}{l} \underline{Z}_L = j \cdot \omega \cdot L \\ L = 0.2 [\text{H}] \\ \omega = 314 \left[\frac{\text{rad}}{\text{s}} \right] \end{array} \right\} \Rightarrow \underline{Z}_L = j \cdot 314 \cdot 0,2 \Rightarrow \boxed{\underline{Z}_L = 62,8 \cdot j, [\Omega]}$$

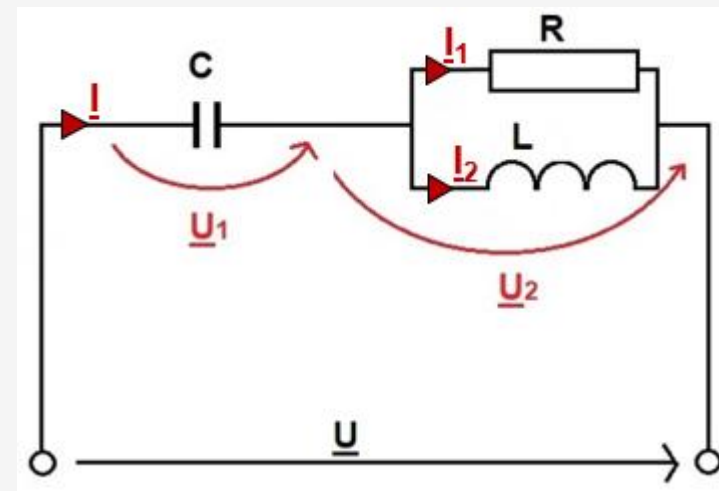
$$\left. \begin{array}{l} \underline{Z}_C = \frac{1}{j \cdot \omega \cdot C} \\ C = 60 [\mu\text{F}] \\ \omega = 314 \left[\frac{\text{rad}}{\text{s}} \right] \end{array} \right\} \Rightarrow \underline{Z}_C = -j \cdot \frac{1}{\omega \cdot C} \Rightarrow \underline{Z}_C = -j \cdot \frac{1}{314 \cdot 60 \cdot 10^{-6}} \Rightarrow \boxed{\underline{Z}_C = -53,08 \cdot j, [\Omega]}$$



- we calculate the **equivalent impedance** of the circuit:

$$\left. \begin{aligned} \underline{Z}_e &= \underline{Z}_C + \frac{\underline{Z}_R \cdot \underline{Z}_L}{\underline{Z}_R + \underline{Z}_L} \\ \underline{Z}_R &= 60 [\Omega] \\ \underline{Z}_L &= 62,8 \cdot j [\Omega] \\ \underline{Z}_C &= -53,08 \cdot j [\Omega] \end{aligned} \right\} \Rightarrow \underline{Z}_e = -53,08 \cdot j + \frac{60 \cdot 62,8 \cdot j}{60 + 62,8 \cdot j}$$
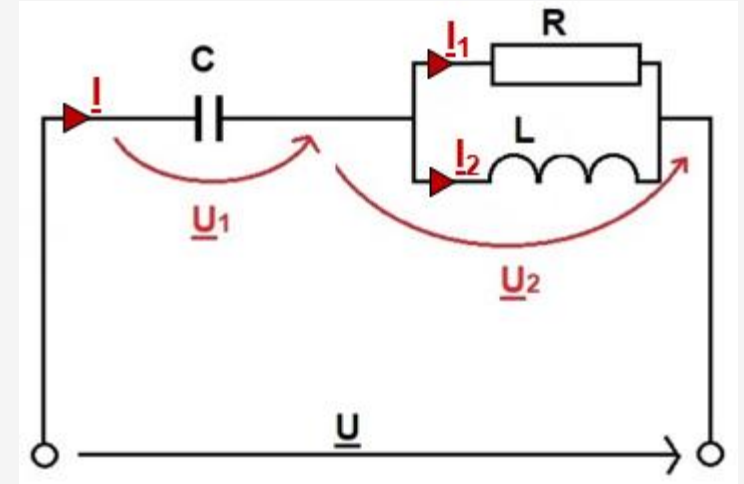
$$\Rightarrow \underline{Z}_e = 31,37 - 23,11 \cdot j, [\Omega]$$



- we calculate the effective value (module) of this complex equivalent impedance:

$$Z_e = \sqrt{31,37^2 + 23,11^2} = 38,96$$

- we calculate the phase angle:

$$\varphi = \arctg \left(-\frac{23,11}{31,37} \right) = -36^\circ 24'$$

$$\Rightarrow \underline{Z}_e = 38,96 \angle -36^\circ 24', [\Omega]$$

■ we calculate the **total current** from the circuit:

• Ohm's Law: $\underline{U} = \underline{Z}_e \underline{I} \Rightarrow \underline{I} = \frac{\underline{U}}{\underline{Z}_e}$

$$\Rightarrow \underline{I} = \frac{220 \angle 0^\circ}{38,96 \angle -36^\circ 24'}$$

○ the effective values are divided, and the phase angles are subtracted:

$$\Rightarrow \underline{I} = 5,65 \angle (0^\circ - (-36^\circ 24')) \Rightarrow \boxed{\underline{I} = 5,65 \angle 36^\circ 24', [A]}$$


• or:

$$\underline{I} = \frac{220}{31,37 - 23,11 \cdot j} \Rightarrow \boxed{\underline{I} = 4,55 + 3,35 \cdot j, [A]}$$

$$I = \sqrt{4,55^2 + 3,35^2} = 5,65$$

$$\gamma_i = \arctg \frac{3,35}{4,55} = 36^\circ 24'$$

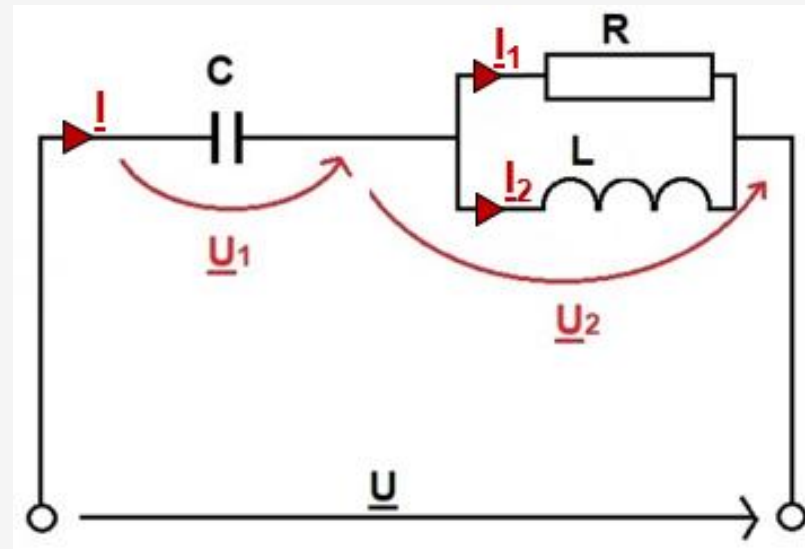
$$\Rightarrow i(t) = 5,65\sqrt{2} \sin(314 \cdot t + 36^\circ 24') [A]$$



- one of the currents is found with the **Current Divider Theorem**:

$$\left. \begin{aligned} \underline{I}_2 &= \frac{\underline{Z}_R}{\underline{Z}_R + \underline{Z}_L} \cdot \underline{I} \\ \underline{Z}_R &= 60 [\Omega] \\ \underline{Z}_L &= 62,8 \cdot j [\Omega] \\ \underline{I} &= 4,55 + 3,35 \cdot j [A] \end{aligned} \right\} \Rightarrow \underline{I}_2 = \frac{60}{60 + 62,8 \cdot j} \cdot (4,55 + 3,35 \cdot j)$$
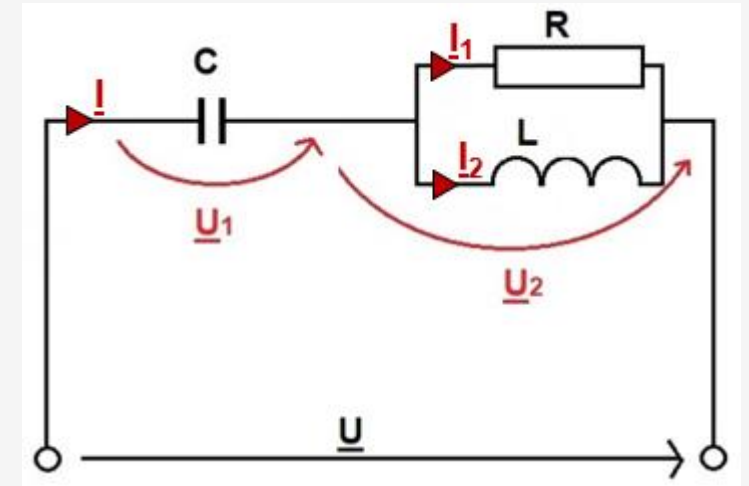
$$\Rightarrow \boxed{\underline{I}_2 = 3,84 - 0,67 \cdot j, [A]}$$



$$\left. \begin{aligned} I_2 &= \sqrt{3,84^2 + 0,67^2} = 3,9 \\ \gamma_{i_2} &= \arctg\left(-\frac{0,67}{3,84}\right) = -9^\circ 53' \end{aligned} \right\} \Rightarrow \boxed{\underline{I}_2 = 3,9 \angle -9^\circ 53', [A]}$$

$$\Rightarrow i_2(t) = 3,9\sqrt{2} \sin(314 \cdot t - 9^\circ 53') [A]$$

- \underline{I}_1 is the **difference** between \underline{I} and \underline{I}_2 :

$$\underline{I}_1 = \underline{I} - \underline{I}_2 \Rightarrow \underline{I}_1 = 4,55 + 3,35 \cdot j - 3,84 + 0,67 \cdot j$$

$$\Rightarrow \boxed{\underline{I}_1 = 0,71 + 4,02 \cdot j, [A]}$$

$$\Rightarrow \underline{I}_1 = 0,71 + 4,02 \cdot j, [A]$$

$$\left. \begin{aligned} I_1 &= \sqrt{0,71^2 + 4,02^2} = 4,08 \\ \gamma_{i_1} &= \arctg \frac{4,02}{0,71} = 80^\circ 7' \end{aligned} \right\} \Rightarrow \underline{I}_1 = 4,08 \angle 80^\circ 7', [A]$$

$$\Rightarrow i_1(t) = 4,08\sqrt{2} \sin(314 \cdot t + 80^\circ 7') [A]$$


■ we calculate the **voltages**, using Ohm's Law:

$$\left. \begin{aligned} \underline{U}_1 &= \underline{Z}_c \cdot \underline{I} \\ \underline{Z}_c &= -53,08 \cdot j [\Omega] \\ \underline{I} &= 4,55 + 3,35 \cdot j [A] \end{aligned} \right\} \Rightarrow \underline{U}_1 = (-53,08 \cdot j) \cdot (4,55 + 3,35 \cdot j)$$

$$\Rightarrow \underline{U}_1 = 177 - 241 \cdot j, [V]$$


$$\left. \begin{aligned} U_1 &= \sqrt{241^2 + 177^2} = 300 \\ \gamma_{u_1} &= \arctg \left(-\frac{241}{177} \right) = -53^\circ 36' \end{aligned} \right\} \Rightarrow \underline{U}_1 = 300 \angle -53^\circ 36', [V]$$
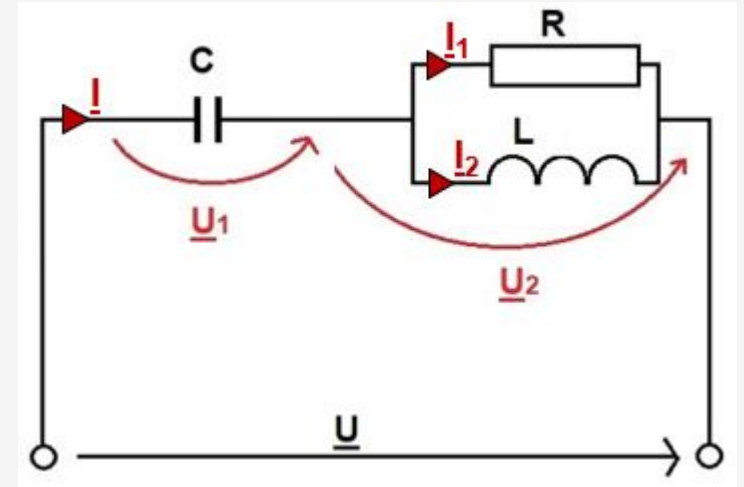
$$\Rightarrow u_1(t) = 300\sqrt{2} \sin(314 \cdot t - 53^\circ 36') [V]$$



$$\left. \begin{array}{l} \underline{U}_2 = \underline{Z}_R \cdot \underline{I}_1 \\ \underline{Z}_R = 60 \, [\Omega] \\ \underline{I}_1 = 0,71 + 4,02 \cdot j \, [A] \end{array} \right\} \Rightarrow \underline{U}_2 = 60 \cdot (0,71 + j \cdot 4,02)$$
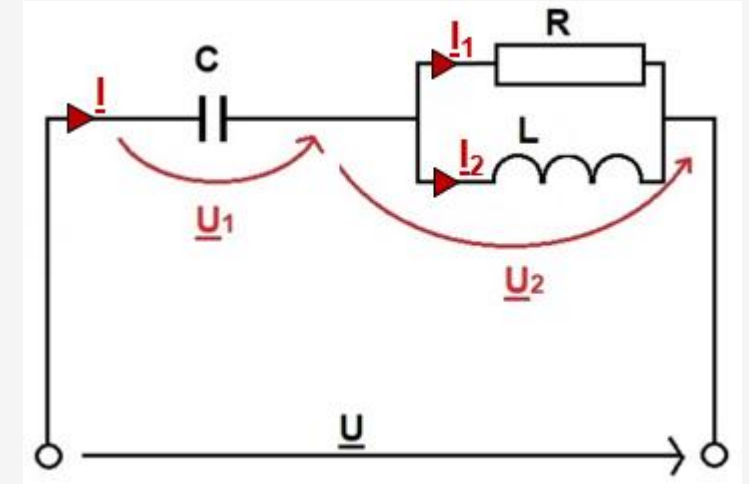
$$\Rightarrow \underline{U}_2 = 43 + 241 \cdot j, [V]$$



$$\left. \begin{array}{l} U_2 = \sqrt{43^2 + 241^2} = 245 \\ \gamma_{u_2} = \arctg \frac{241}{43} = 80^{\circ}7' \end{array} \right\} \Rightarrow \underline{U}_2 = 245 \angle 80^{\circ}7', [V]$$

■ Possible checks:

$$\underline{U}_2 = \underline{Z}_L \cdot \underline{I}_2$$

$$\underline{U}_1 + \underline{U}_2 = \underline{U} \quad \bullet \text{ we must obtain the same value.}$$

$$\Rightarrow u_2(t) = 245\sqrt{2} \sin(314 \cdot t + 80^{\circ}07') [V]$$

We note that $\underline{U}_1 + \underline{U}_2 = \underline{U}$ (complex values) although $U_1 > U$ (effective values) and $U_2 > U$ (effective values).

Also $\underline{I}_1 + \underline{I}_2 = \underline{I}$ $I_1 + I_2 = 7,98 \, A \Rightarrow I_1 + I_2 > I$ (as effective values).

We compute the powers

Complex power received to the terminals can be found in two different ways:


$$\underline{S} = \left\{ \begin{array}{l} \underline{U} \cdot \underline{I}^* = 220 \cdot (4,55 - j \cdot 3,35) \\ \underline{Z}_e \cdot I^2 = (31,37 - j \cdot 23,11) \cdot 5,65^2 \end{array} \right\} \Rightarrow \underline{S} = 1001 - j \cdot 738 \text{ VA}$$

We know that:

$$\underline{S} = P + j \cdot Q = 1001 - j \cdot 738 \text{ VA} \Rightarrow$$

$$\Rightarrow P = 1001 \text{ W}$$

$$Q = -738 \text{ VAR}$$

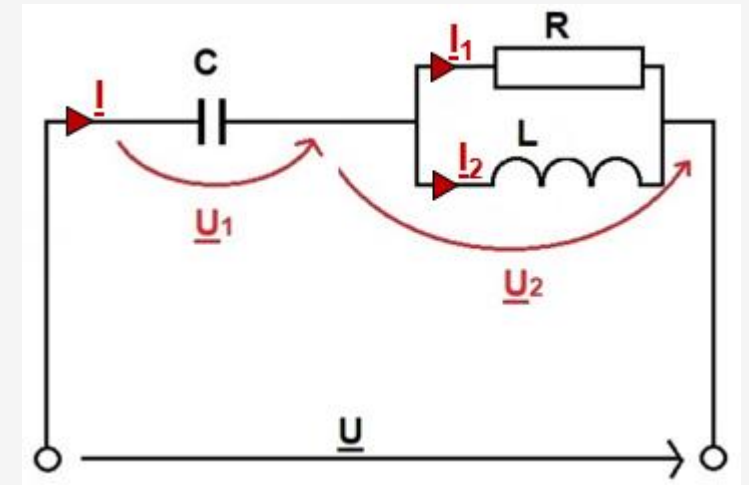

We check now the active power and the reactive power using the other formulas:


$$P = \left\{ \begin{array}{l} R \cdot I_1^2 = 60 \cdot 4,08^2 \\ U \cdot I \cdot \cos \varphi = 220 \cdot 5,65 \cdot \cos(-36^\circ 24') \end{array} \right\} = 1001 \text{ W}$$

$$\Rightarrow P_{\text{generated}} = P_{\text{consummated}}$$

We check also the reactive power:

$$Q = \begin{cases} X \cdot I^2 = X_L \cdot I_L^2 + X_C \cdot I_C^2 \\ U \cdot I \cdot \sin \varphi \end{cases}$$
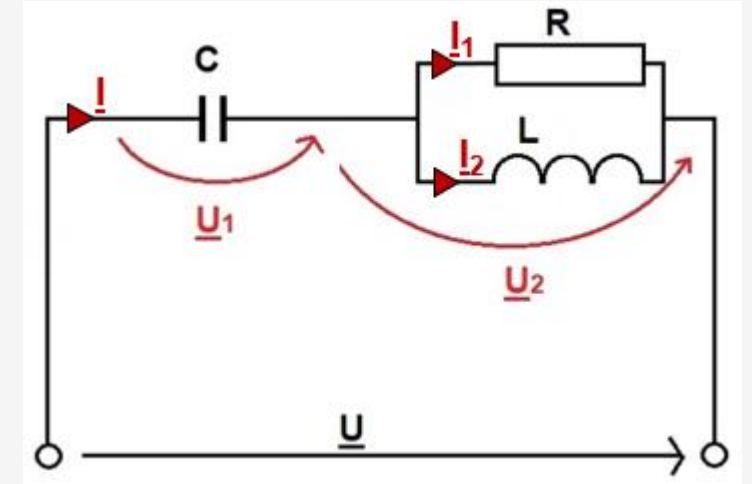
$$Q = \begin{cases} \omega \cdot L \cdot I_2^2 - \frac{1}{\omega \cdot C} \cdot I^2 = 955 - 1693 \\ U \cdot I \cdot \sin \varphi = 220 \cdot 5,65 \cdot \sin(-36^\circ 24') \end{cases} = -738 \text{ VAr}$$



- We note that the inductor consumes 955 VAr, but the capacitor „produces“ 1693 VAr, covering the inductor consumption
- The excess of reactive power 738 VAr, it is ceded to the terminals, the circuit having a capacitive behavior

The phasors diagrams is a simple draw in the complex coordinate system of the three currents phasors at a convenient scale mm/A. The three voltages phasors have their scale mm/V.

$$\underline{U} = 220 \angle 0^\circ \text{ V};$$



$$\underline{U}_1 = 300 \angle -53^\circ 36' \text{ V};$$

$$\underline{U}_2 = 245 \angle 80^\circ 7' \text{ V};$$

$$\underline{I} = 5,65 \angle 36^\circ 24' \text{ A};$$

$$\underline{I}_1 = 4,08 \angle 80^\circ 7' \text{ A};$$
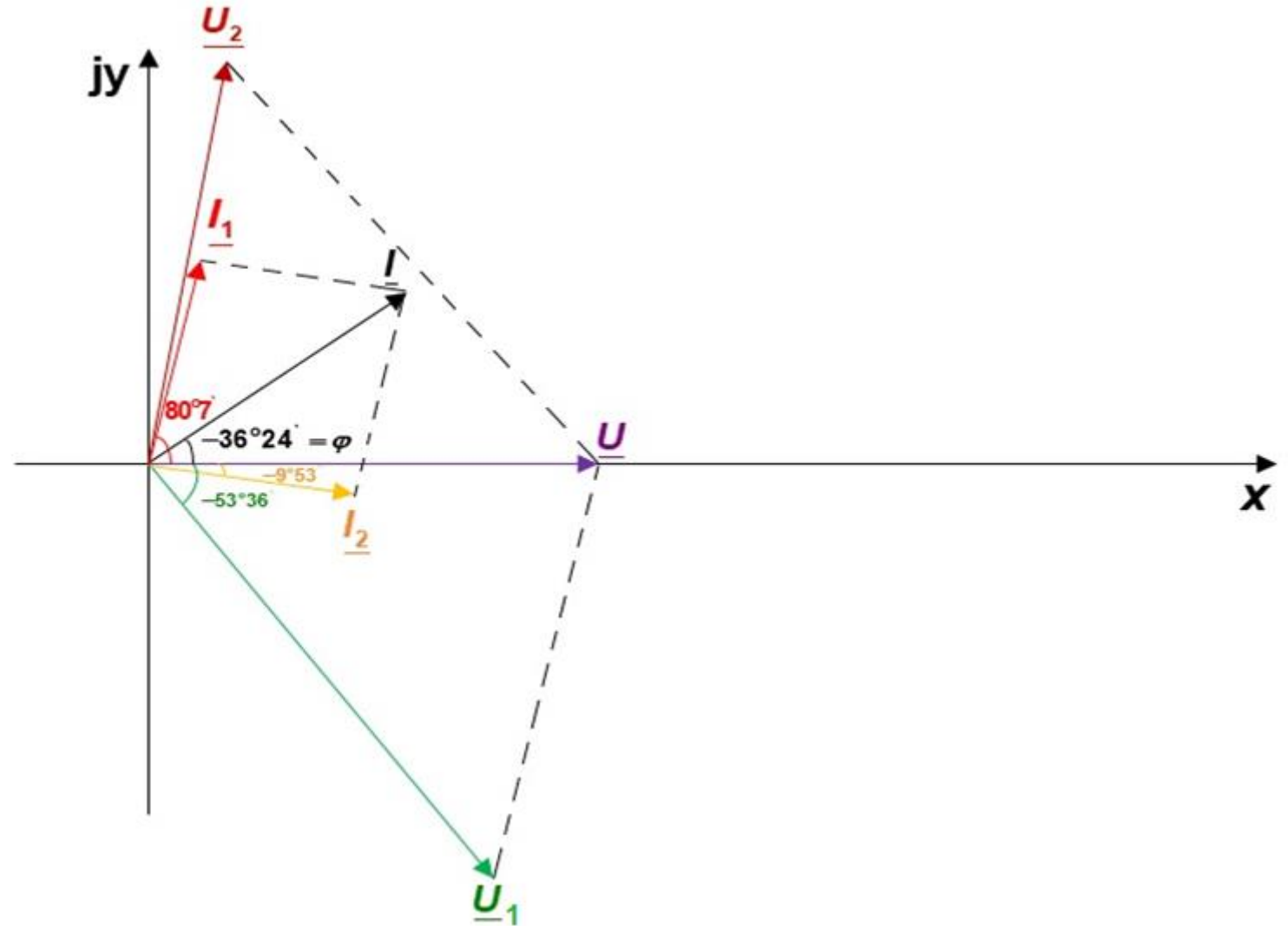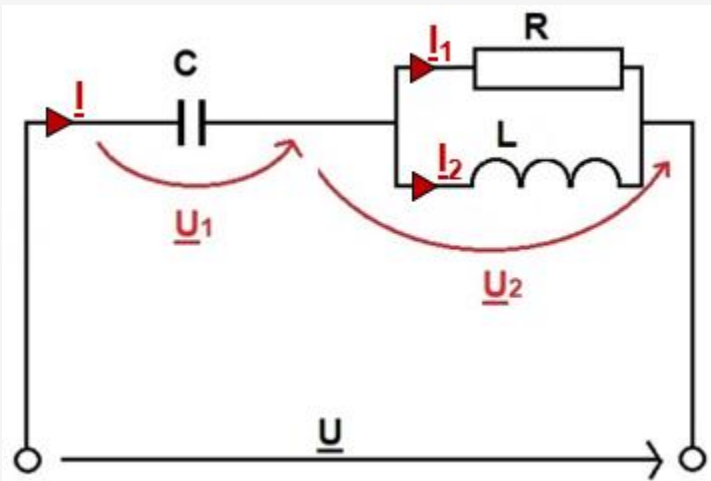
$$\underline{I}_2 = 3,9 \angle -9^\circ 53' \text{ A};$$



Homework

Find the currents, voltages and powers and draw the phasors diagram for the circuit, knowing that:

$$u(t) = 220\sqrt{2} \sin(\omega \cdot t + 0^\circ) [V];$$


$$f = 50 [\text{Hz}];$$

$$R = 60 [\Omega];$$

$$L = 0.2 [\text{H}];$$

$$C = 60 [\mu\text{F}].$$

Solution:

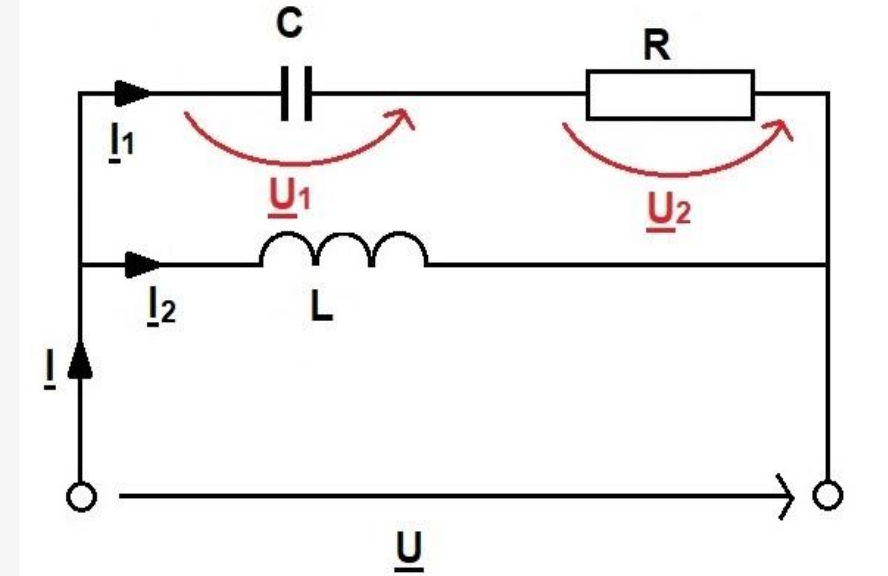

$$\underline{I}_1 = 2,06 + j \cdot 1,82 = 2,75 \angle 41^\circ 30' \text{ A};$$

$$\underline{I}_2 = -j \cdot 3,5 = 3,5 \angle -90^\circ \text{ A};$$

$$\underline{I} = 2,06 + j \cdot 1,68 = 2,66 \angle -39^\circ 20' \text{ A};$$


$$\underline{U}_1 = 145,7 \angle -48^\circ 30' = 96,6 - j \cdot 109,34 \text{ V};$$

$$\underline{U}_2 = 123,6 + j \cdot 109,2 = 164,8 \angle 41^\circ 30' \text{ V};$$

$$\underline{S} = 452 + j \cdot 370 \text{ VA};$$

$$P = 452 \text{ W};$$

$$Q = 370 \text{ VAR}.$$

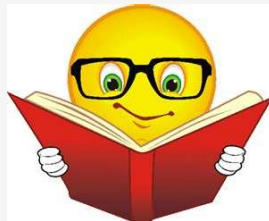



Thank you for your
attention!!!



Questions???