

Op-amp Hysteresis Voltage Comparators


Comparators with positive feedback

Hysteresis = phenomenon according to which the actual value of a quantity (material) also depends on previous values of quantities determining it.

= property of a system such that an output value is not a strict function of the corresponding input, but also incorporates some lag, delay, or history dependence, and in particular **the response for a decrease in the input variable is different from the response for an increase in the input variable.**

Simple comparators have two drawbacks:

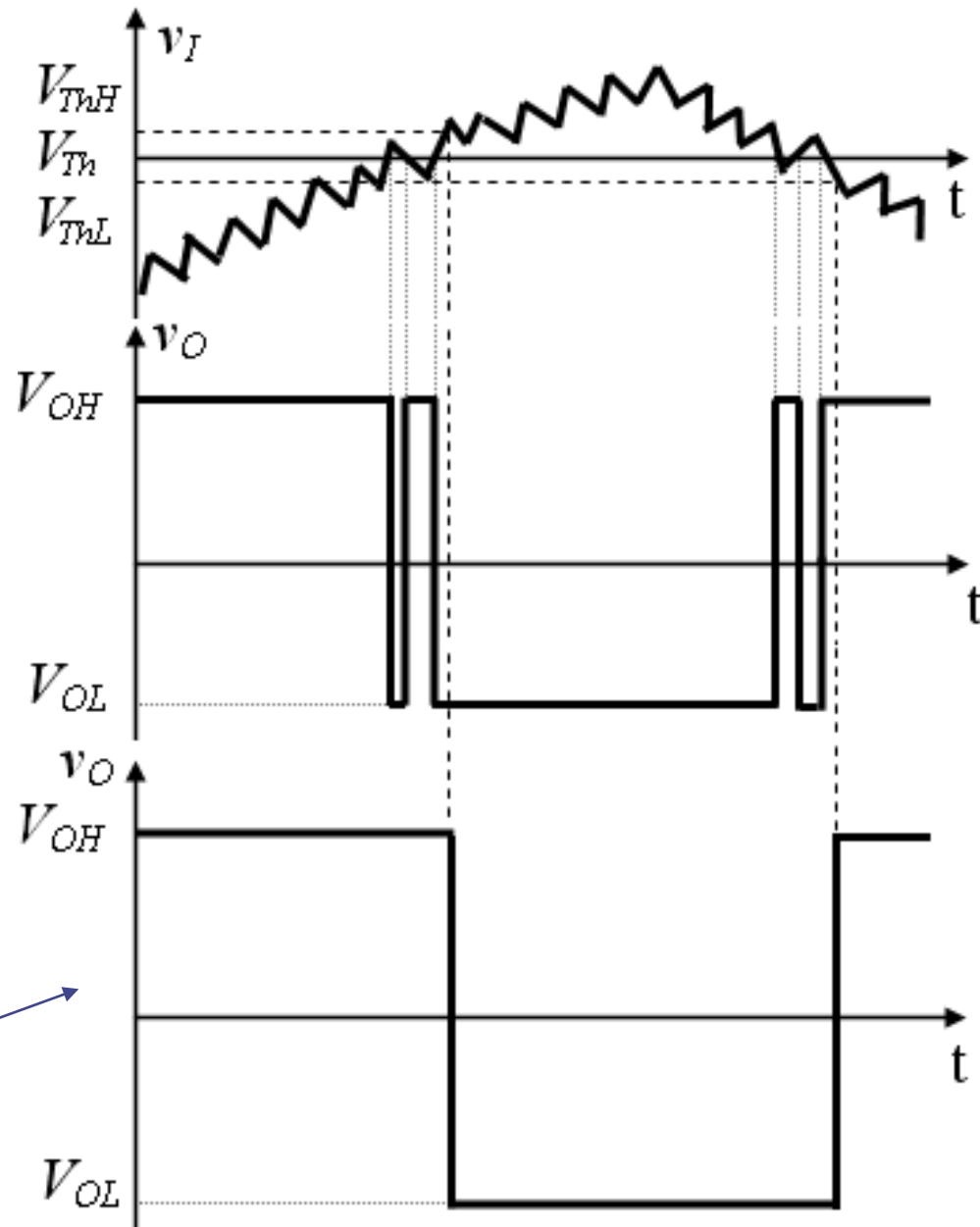- For a very slowly varying input, output switching can be rather slow.
- For a noisy input signal the output may present several unwanted (parasitic) transitions (commutations) as the input passes through the threshold voltage value (trigger point)




no more unwanted transition

*How can one implement
this time response ?*

Solution

- Two different threshold values V_{ThH} and V_{ThL}
 - Two distinct output values: V_{OH} and V_{OL}
 - The commutation takes place at
 - V_{ThH} only if $v_O = V_{OH}$
 - V_{ThL} only if $v_O = V_{OL}$
- ⇒ The threshold values should depend on the output value →
The output voltage should be brought back to the input to
contribute to the threshold values: ***positive feedback***
(intensifies the effect)
- **Feeding back one fraction of the output voltage to the non-inverting input by means of a resistive divider**


How does VTC look like?

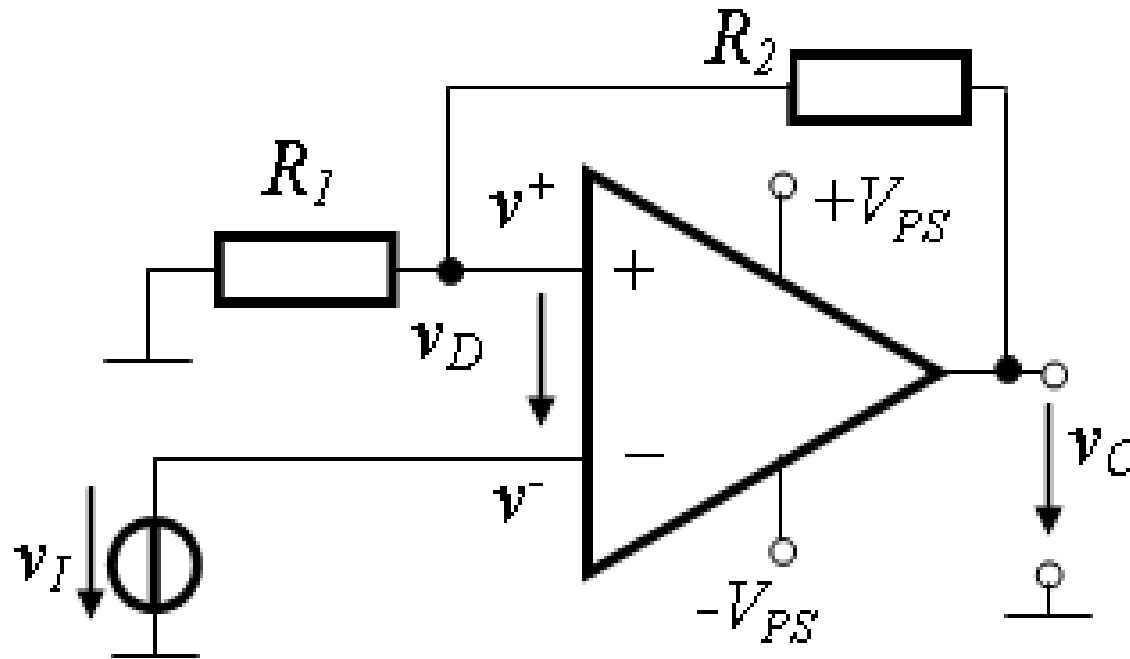

R_1, R_2 – assure positive feedback (PF)

A fraction of the output voltage is fed back to the noninverting input

Inverting hysteresis comparator

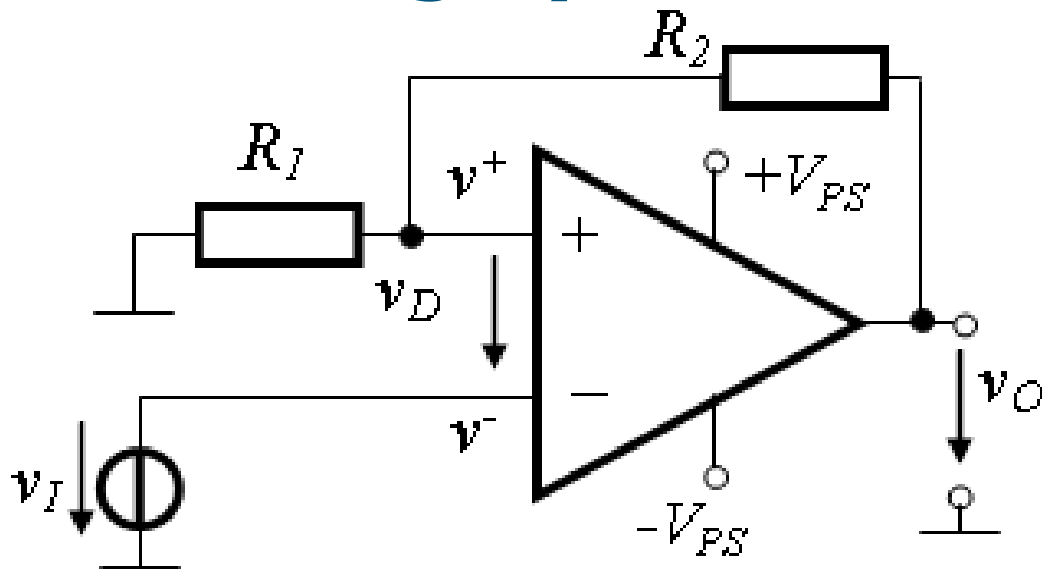

$$v^+ = \frac{R_1}{R_1 + R_2} v_O$$

$$v^- = v_I$$



$$v_D = \frac{R_1}{R_1 + R_2} v_O - v_I$$

$$\text{For } v_D = 0, v_I \rightarrow V_{Th}$$

$$V_{ThH} = \frac{R_1}{R_1 + R_2} V_{OH}$$

$$V_{ThL} = \frac{R_1}{R_1 + R_2} V_{OL}$$

Inverting hysteresis comparator

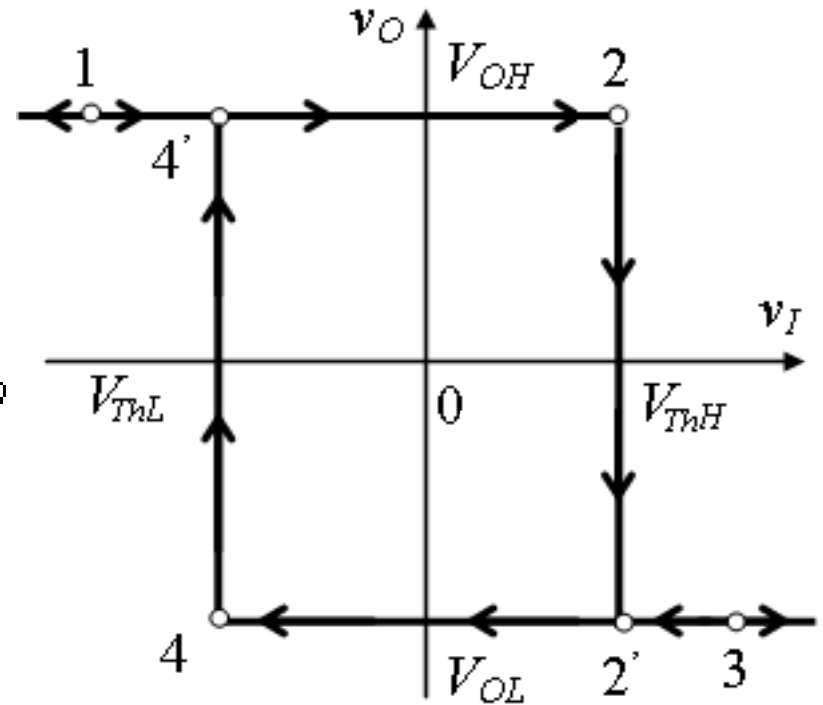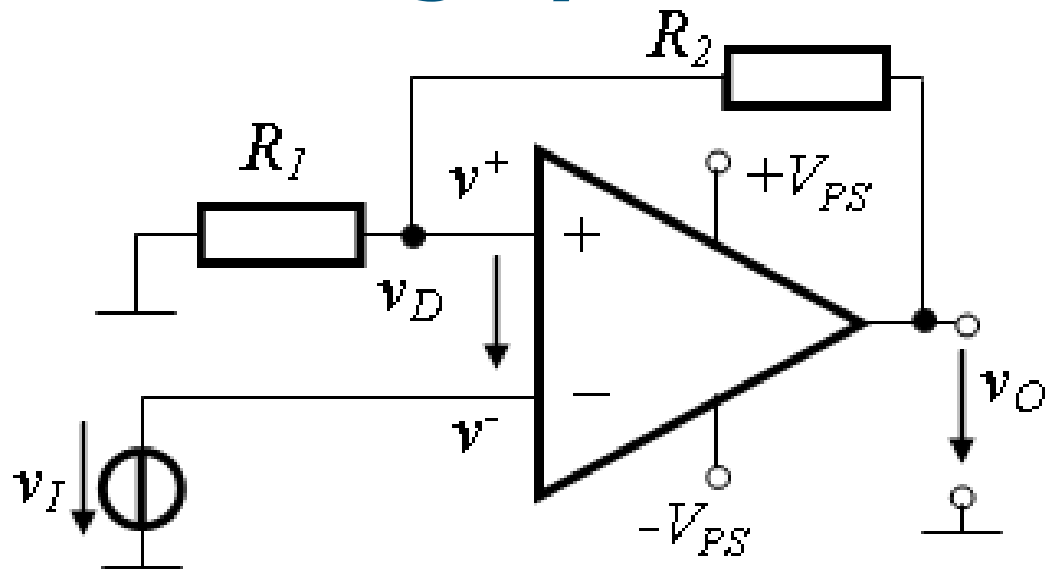

$$v^+ = \frac{R_1}{R_1 + R_2} v_O$$

$$v^- = v_I$$

$$v_D = \frac{R_1}{R_1 + R_2} v_O - v_I$$

$$\text{For } v_D = 0, v_I \rightarrow V_{Th}$$






$$V_{ThH} = \frac{R_1}{R_1 + R_2} V_{OH}$$

$$V_{ThL} = \frac{R_1}{R_1 + R_2} V_{OL}$$


Features

- moving direction on the hysteresis
- at a certain moment only one threshold is “active”
- the input signal triggers the switching of the output, the switching process being then sustained by the PF
- let's suppose $v_O = V_{OL}$, $v_I > V_{ThL}$,
 $v_I \downarrow$, when v_I passes through V_{ThL} $v_D \uparrow$, $v_O \uparrow$, $v^+ \uparrow$, $v_D \uparrow$, $v_O \uparrow$
- once the v_O starts to change its value **the transition is sustained by the circuit itself due to its PF**
 \Rightarrow fast (accelerated) switching
- Bistable circuit or Schmidt triggers

Example

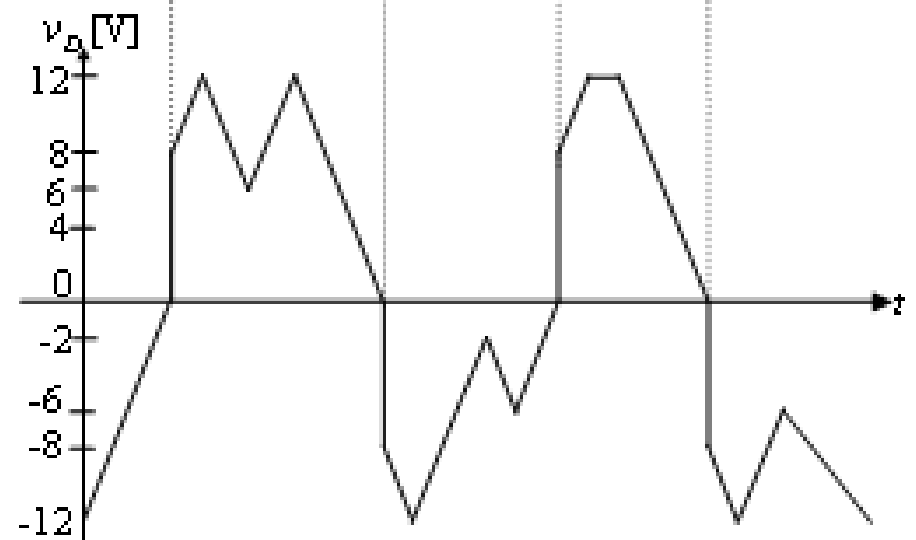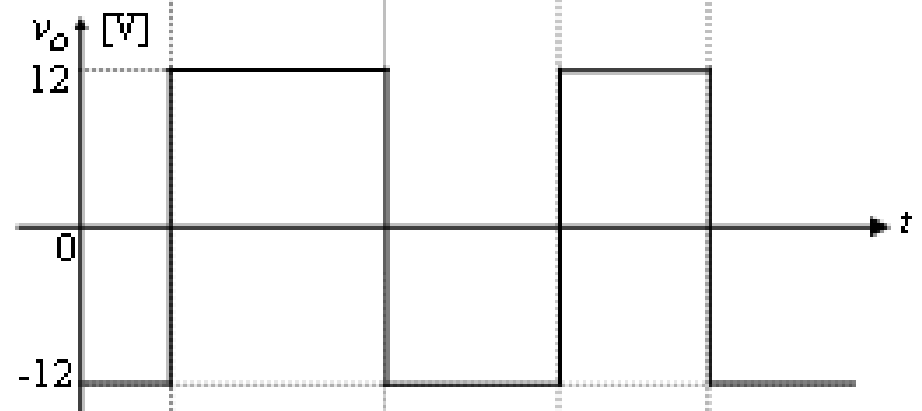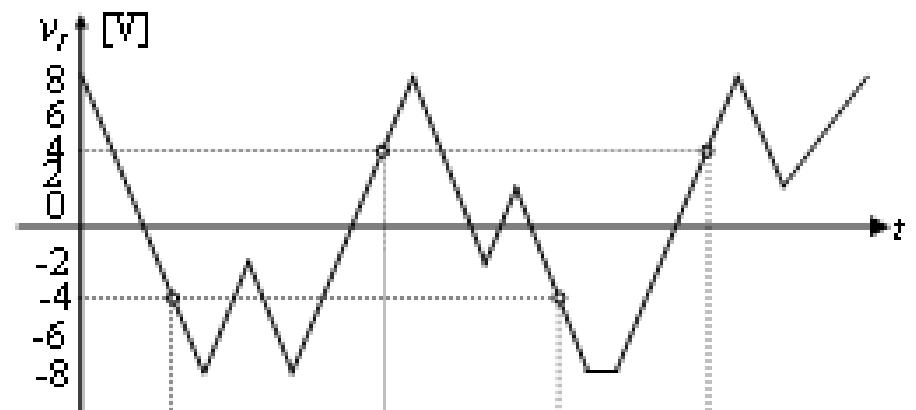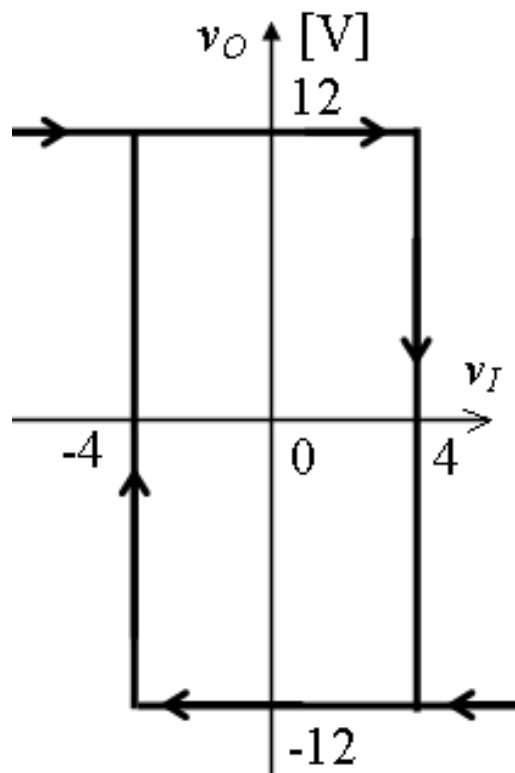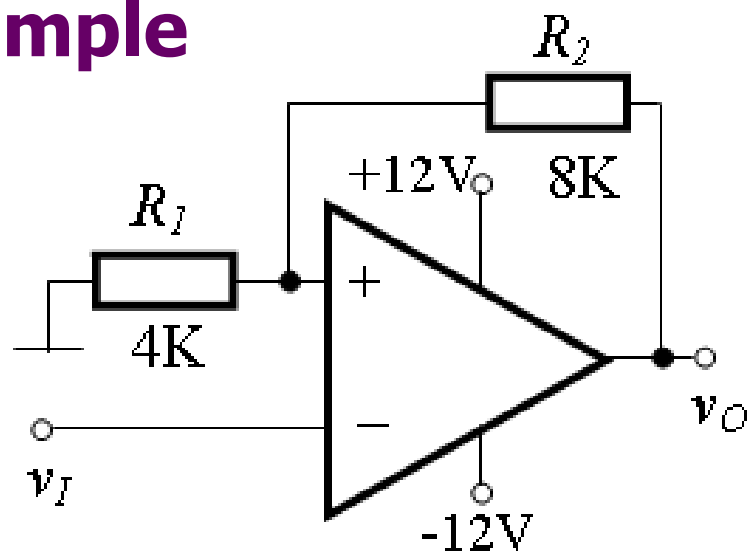

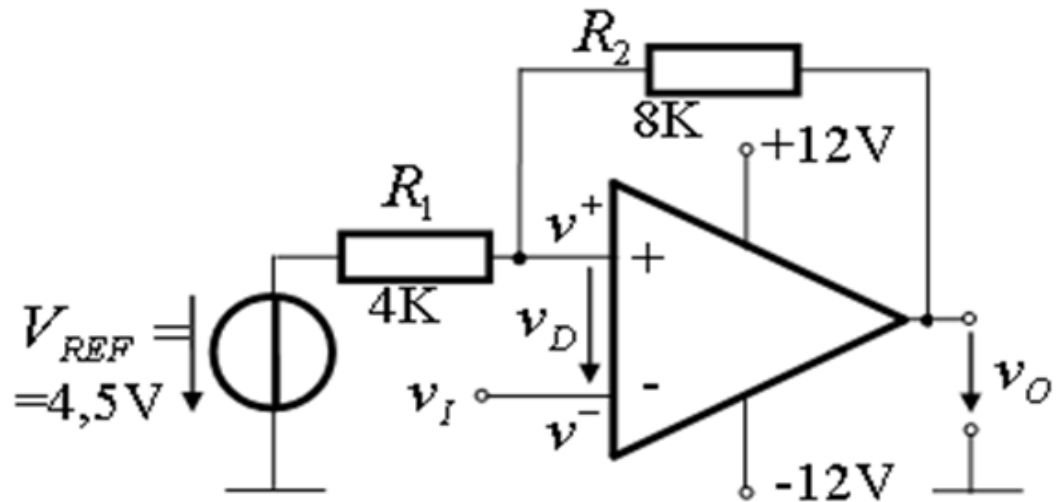Inverting comparator with asymmetric thresholds




$$v^+ = \frac{R_1}{R_1 + R_2} v_O + \frac{R_2}{R_1 + R_2} V_{REF}$$

$$v_D = v^+ - v^- = \frac{R_1}{R_1 + R_2} v_O + \frac{R_2}{R_1 + R_2} V_{REF} - v_I$$



For $v_D = 0$, $v_I \rightarrow V_{Th}$

$$V_{ThL} = \frac{R_1}{R_1 + R_2} V_{OL} + \frac{R_2}{R_1 + R_2} V_{REF}$$
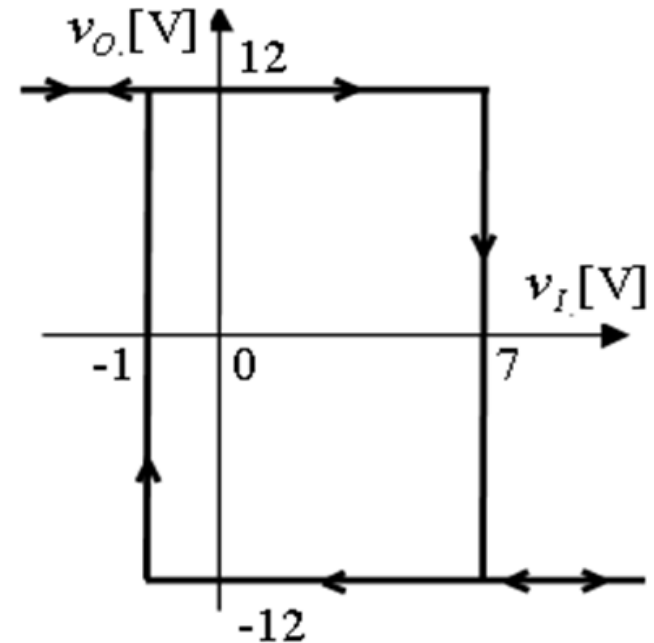
$$V_{ThH} = \frac{R_1}{R_1 + R_2} V_{OH} + \frac{R_2}{R_1 + R_2} V_{REF}$$



Non-inverting hysteresis comparators

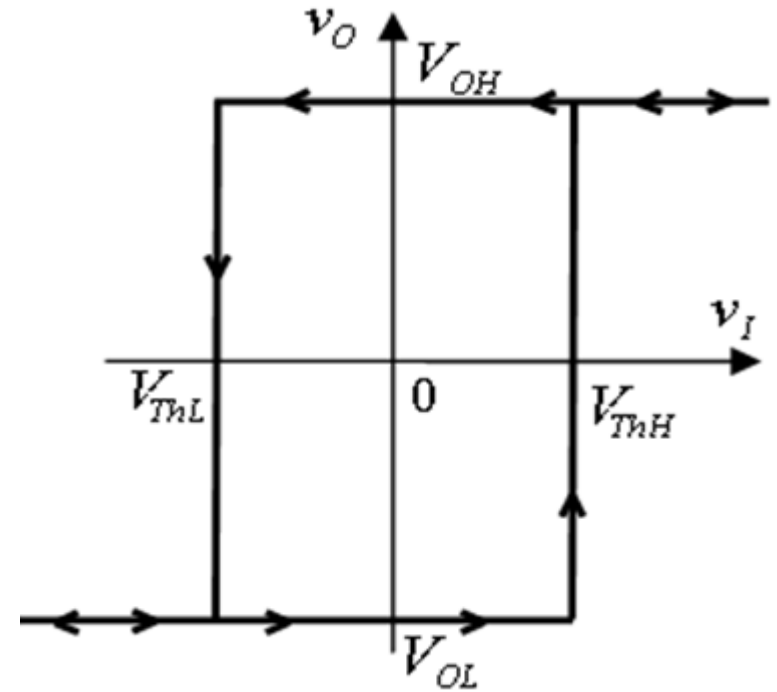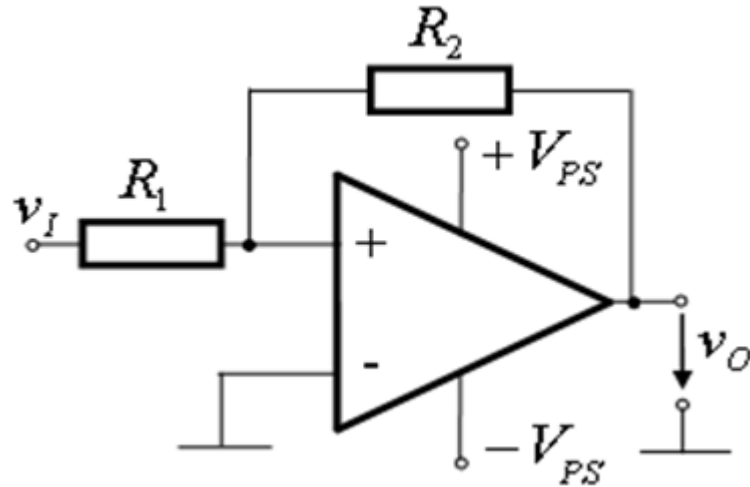

$$v_D = v^+ - v^- = \frac{R_1}{R_1 + R_2} v_O + \frac{R_2}{R_1 + R_2} v_I - 0$$

For $v_D = 0$, $v_I \rightarrow V_{Th}$



$$\frac{R_1}{R_1 + R_2} v_O + \frac{R_2}{R_1 + R_2} V_{Th} = 0$$

$$V_{Th} = -\frac{R_1}{R_2} v_O$$

$$V_{ThL} = -\frac{R_1}{R_2} V_{OH}$$

$$V_{ThH} = -\frac{R_1}{R_2} V_{OL}$$

Illustration

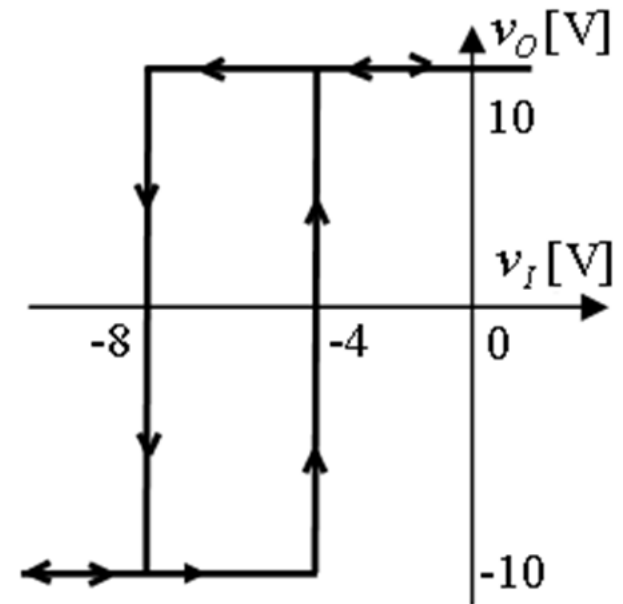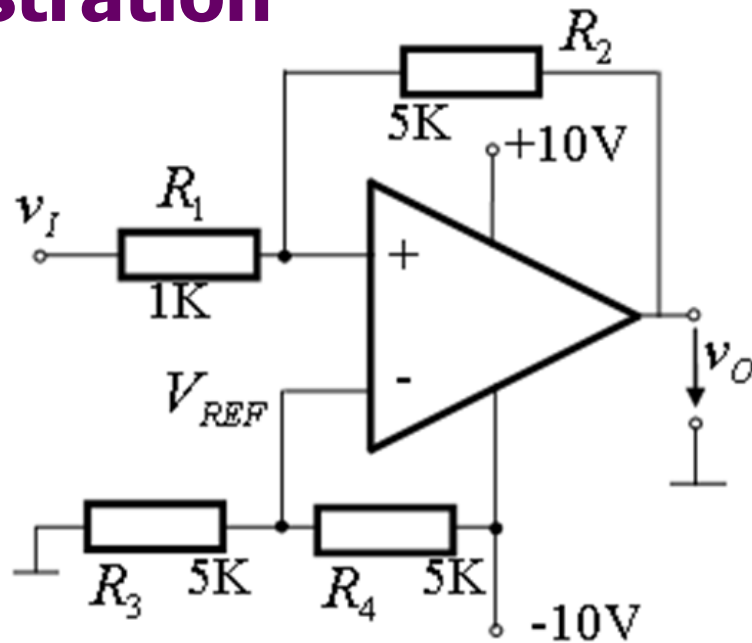

$$v_D = v^+ - v^- = \frac{R_1}{R_1 + R_2} v_O + \frac{R_2}{R_1 + R_2} v_I - V_{REF}$$


$$v_{ThH} = -\frac{R_1}{R_2} V_{OL} + \left(1 + \frac{R_1}{R_2}\right) V_{REF} = -\frac{1}{5}(-10) + \left(1 + \frac{1}{5}\right)(-5) = -4\text{V}$$

$$v_{ThL} = -\frac{R_1}{R_2} V_{OH} + \left(1 + \frac{R_1}{R_2}\right) V_{REF} = -\frac{1}{5}(10) + \left(1 + \frac{1}{5}\right)(-5) = -8\text{V}$$

Applications of hysteresis comparators

- Solution for one-threshold comparator in a noisy environment (the hysteresis width $>$ noise magnitude (peak-to-peak))
- In control system for “on-off control”
-example

Thermostat

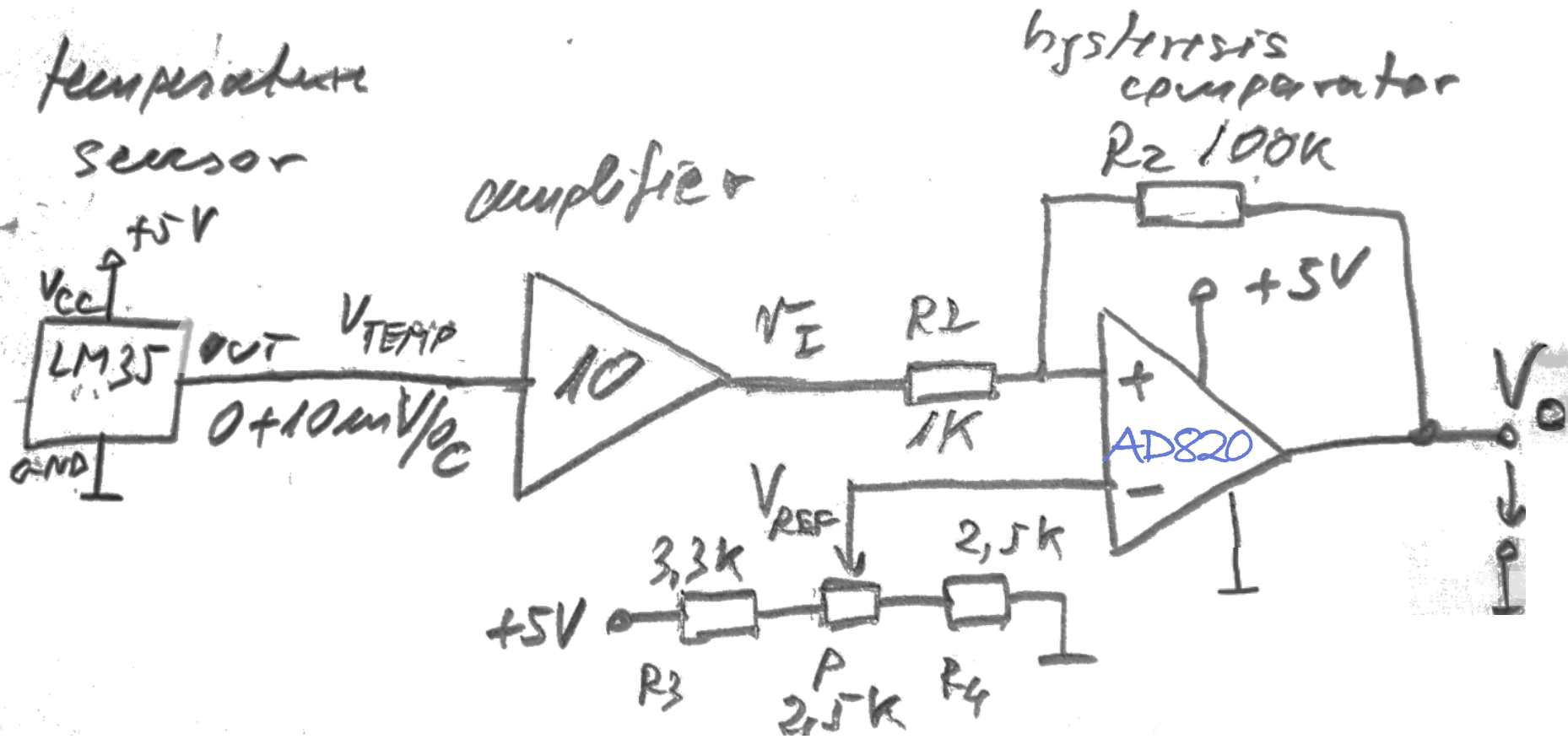


LM35

<http://www.ti.com/product/LM35>

AD 820
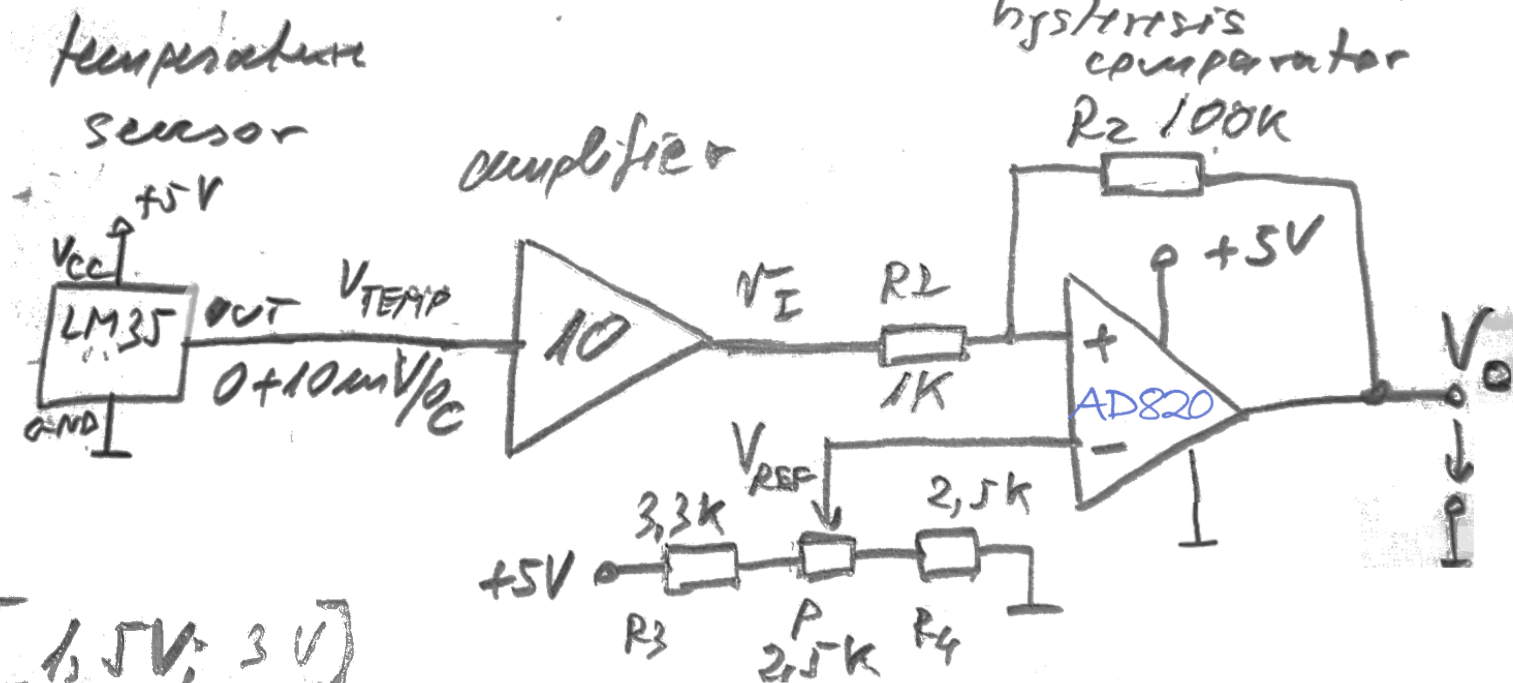
<https://www.analog.com/media/en/technical-documentation/data-sheets/ad820.pdf>



$$V_{REF} \in [1.5V; 3V]$$

$$V_{TH} = -\frac{R_1}{R_2} V_O + \left(1 + \frac{R_1}{R_2}\right) V_{REF}$$

$$\underline{V_{REF} = 1.98V \quad (\approx 2V)}$$

$$V_{THL} = 1.95V ; V_{THH} = 2.05V$$

$$\downarrow$$

$$V_{TEMP} = 195mV$$

$$\downarrow$$



$$temp = 19.5^\circ C$$

$$\downarrow$$


$$V_{TEMP} = 205mV$$

$$\downarrow$$

$$temp = 20.5^\circ C$$

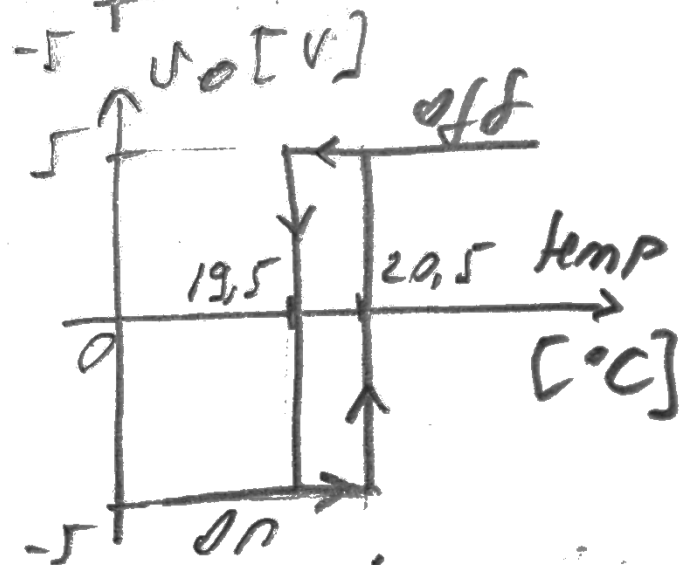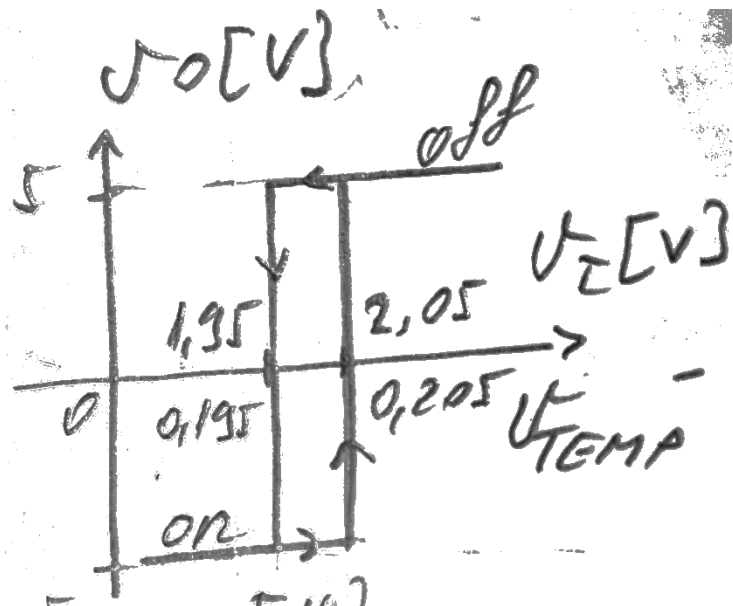

set point: 20°C
Temperature 20°C

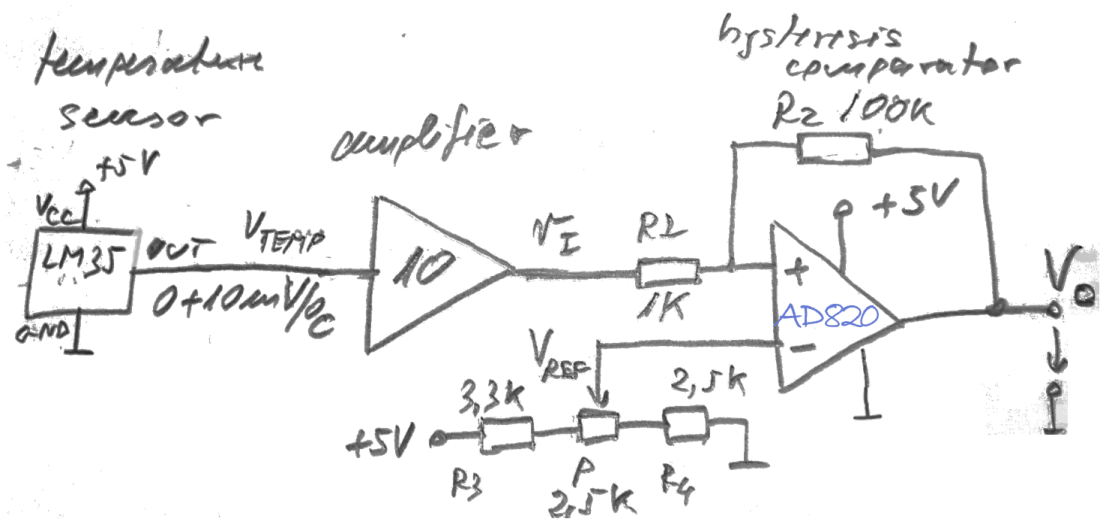

$$V_{REF} \in [1.5V; 3V]$$

$$V_{TH} = -\frac{R_1}{R_2} V_O + \left(1 + \frac{R_1}{R_2}\right) V_{REF}$$

$$V_{REF} = 1.98V \quad (\approx 2V)$$

$$V_{THL} = 1.95V; \quad V_{THH} = 2.05V$$

$$\downarrow$$

$$V_{TEMP} = 195mV$$

$$\downarrow$$

$$temp = 19.5^{\circ}C$$

$$\downarrow$$

$$V_{TEMP} = 205mV$$

$$\downarrow$$

$$temp = 20.5^{\circ}C$$