

Capitolul 1

Sisteme de numerație binare

$$[2^{N-1} - 2^{N-1} - 1]$$

$$[0 - 2^N - 2^M]$$

$$[-2^{(N-1)} - 2^{(N-1)} - 2^{-M}]$$

$$[0 - 2^{(N-1)}]$$

$$[-2^{(N-1)} - 1 - 2^{(N-1)} - 1]$$

$$[-2^{(N-1)} - 2^{(N-1)} - 1]$$

$$[-2^{(N-1)} - 1 - 1 - 2^{(N-1)} - 1]$$

$$(1) [0 - 2^N - 1]$$

- întregi fără semn → nu poate stoca nr. neg.
- complementul față de 2 → necesita 1 bit în plus.
- fractionare fără semn → nu poate stoca nr. negative
- fractionare cu semn în Complement față de 2
- cod. Gray
- Mărimi și Semn
- Complement față de 2 desprins
- Complement față de 1
- Virgula mobilă

Codurile binare

- ponderate → BCD (§ 4.2)
- neponderate → Excess 3
GRAY

Probleme

① cel mai mare ·
cel mai mic

fără semn ⇒ cel mai mic = 0
mare = $2^{12} - 1$

cu semn ⇒ cel mai mic = $-2^{11} - 1$
mare = $2^{11} - 1$

② $(68BE)_{16} \longrightarrow ()_2 \longrightarrow ()_8$

$$68 \text{ BE} \longrightarrow \begin{array}{r} 0110 \\ 8421 \end{array} \quad \begin{array}{r} 1000 \\ 8421 \end{array} \quad \begin{array}{r} 1011 \\ 8421 \end{array}$$

A - 10
B - 11
C - 12
D - 13
E - 14
F - 15

$$(011010001011110)_2 \quad \begin{array}{r} 1110 \\ 8421 \end{array}$$

$$\begin{array}{ccccccccc} 0 & 0 & 0 & 1 & 1 & 0 & 1 & 0 & 0 \\ \hline 0 & 6 & 4 & 2 & 7 & 6 & & & \end{array} \quad \begin{array}{c} 4 \\ 2 \\ 1 \end{array}$$

$$(64276)_8$$

$$\textcircled{3} \quad (34,4375)_{10}$$

$$34 \quad \begin{array}{r} 0 \\ 128 \\ 64 \\ 32 \\ 16 \\ 8 \\ 4 \\ 2 \\ 1 \end{array} \quad \begin{array}{r} 4375 \\ 2 \\ 875 \\ 0 \\ 2 \\ 175 \\ 0 \\ 0 \end{array}$$

$$\begin{array}{l} 0,4375 * 2 = 0,8750 + 0 \\ 0,8750 * 2 = 0,7500 + 1 \\ 0,75 * 2 = 0,5 + 1 \\ 0,5 * 2 = 0 + 1 \end{array} \quad \downarrow$$

$$\begin{array}{r} 0,75 \\ 2 \\ \hline 1,5000 \\ 17500 \end{array}$$

$$(100010,0111)_2$$

$$\begin{array}{r} 00100010,0111 \\ \hline (22,7)_{16} \end{array}$$

$$\frac{1}{4} \cdot \frac{1}{4}$$

$$\textcircled{4} \quad (10110,0101)_2 \quad \begin{array}{r} 1:4=0,25 \\ 0,0625 \\ 25 \\ \hline 3125 \end{array}$$

$$\begin{aligned} & 2^4 \cdot 1 + 2^2 \cdot 1 + 2^1 \cdot 1 + 2^{-2} + 2^{-4} = \frac{25}{3125} \\ & = 16 + 4 + 2 + \frac{1}{4} + \frac{1}{16} = (22,3125)_{10} \end{aligned}$$

$$(16, 5)_{16}$$

$$\begin{array}{r} 5 \cdot 16 = 0, 31 \\ \hline 58 \\ \hline 56 \\ 20 \end{array}$$

$$16^0 \cdot 1 + 6 \cdot 16^0 + 5 \cdot 16^{-1} = 16 + 6 + \frac{5}{16} \\ = (22, 3125)_{10}$$

$$N_3 = (26, 24)_8$$

$$64 : 3 = 1$$

$$6 \cdot 8^0 + 2 \cdot 8^1 + 2 \cdot 8^{-1} + 4 \cdot 8^{-2} \\ = 6 + 16 + \frac{2}{8} + \frac{4}{64} = 22 + \frac{1}{4} + \frac{1}{16} = \\ \frac{16}{16} = 22,0 + 0,25 + \dots \\ = (22, 3125)_{10}$$

⑤

$\begin{array}{r} 1011 \\ \hline 10 \\ \hline 10000 \end{array}$	$\begin{array}{r} 1011 \\ \hline 101 \\ \hline 1011 \\ \hline 0000 \\ \hline 1011 \\ \hline 110111 \end{array}$
--	---

⑥ One's complement \rightarrow Inverting
 Two's complement \rightarrow Inverting + 1

$$N_1 = 11101010$$

$$1's = 00010101$$

$$2's = 00010101 + \overbrace{}^1$$

$$b) N_2 = 01111110$$

$$2's = 10000001$$

$$1's \text{ complement } 10000001 \quad \overbrace{-10000010}^1$$

$$c) N_3 = 00000000$$

$$1's = 11111111$$

$$2's = \begin{array}{r} 11111111 \\ + \\ \hline 1 \end{array}$$

$\textcircled{1} 00000000 \Rightarrow$ igorii transportul
și va fi

$$00000000$$

Complementul lui 1 pt 0 poate fi scris { $\begin{array}{r} 00000000 \\ (0+) \end{array}$

$$\begin{array}{r} 11111111 \\ (-0) \end{array}$$

(7)

$$a) 27_{10} = (00011011)_2$$

$$\begin{array}{r} 0 \\ 64 \\ \hline 0 \\ 32 \\ \hline 1 \\ 16 \\ \hline 1 \\ 8 \\ \hline 0 \\ 4 \\ \hline 1 \\ 2 \\ \hline 1 \\ 1 \\ \hline \end{array}$$

$$61_{10} = (00111101)_2$$

$$\begin{array}{r} 0 \\ 64 \\ \hline 1 \\ 32 \\ \hline 1 \\ 16 \\ \hline 1 \\ 8 \\ \hline 1 \\ 4 \\ \hline 0 \\ 2 \\ \hline 1 \\ 1 \\ \hline \end{array}$$

$$1's \text{ complement} = 1000010+$$

$$2's \text{ complement} = \overline{1000011}$$

$$27 + (-61) = \begin{array}{r} 10000\ddot{1}1+ \\ 0011011 \\ \hline 1011110 \end{array}$$

$$\begin{array}{r} 61- \\ 27 \\ -34 \end{array}$$

$$-34 \text{ tot pe } 7 \quad 34 = \begin{array}{r} 0 \\ 64 \\ \hline 1 \\ 32 \\ \hline 0 \\ 16 \\ \hline 0 \\ 8 \\ \hline 0 \\ 4 \\ \hline 1 \\ 2 \\ \hline 0 \\ 1 \\ \hline \end{array}$$

$$1's \text{ comp: } 1011101+$$

$$2's \text{ comp: } \overline{1011110}$$

b)

-27

$$27_{10} = (0011011)_2$$

$$\begin{array}{r}
 1100100+ \\
 \hline
 1100101 \\
 -1100101 \\
 -0111101 \\
 \hline
 10100010
 \end{array}$$

2^1 's

ignorat

$61_{10} = (00111101)_2$

pag 22 - overflow, BCD

$$\begin{array}{rcl}
 2 & \rightarrow & 8 \\
 8 & \rightarrow & 2
 \end{array}$$

$$\textcircled{3} \quad (1476503)_8 \rightarrow$$

$$\rightarrow (001100111100101000011)_2$$

$$\textcircled{2} \quad (\underline{\underline{11010100}})_4 \rightarrow (\quad)_2$$

$$(\underline{\underline{1010001000010000}})_2 \rightarrow (\quad)_8$$

$$(50420)_8$$

$$\textcircled{7} \quad (10011100010101)_4 \rightarrow (?)_{16}$$

$$(\underbrace{010000010101000000100010001}_{4\ 1\ 5\ 0\ 1\ 1\ 1})_2$$

$$(4150111)_{16}$$

$$\begin{array}{r} 256 \\ 260 \\ -4 \\ \hline 256 \\ 32 \\ \hline 288 \\ 288 \\ \hline 0 \\ \hline 3 \\ 81 \\ \hline 292 \end{array}$$

$$\begin{aligned} 4^4 &= 4^2 \cdot 4^2 \\ &= 16 \cdot 16 \\ &= 256 \end{aligned}$$

$$\textcircled{8} \quad \text{a)} \quad (100)_4$$

$$4 \cdot 1 = (16)_{10}$$

$$4^4 = 4^2 \cdot 4^2$$

$$\text{b)} \quad (12041)_4 = 4 \cdot 4^0 + 4^1 \cdot 0 + 4^2 \cdot 2 + 4^4$$

$$\begin{aligned} &= 4 + 16 \cdot 2 + 256 \\ &= (292)_{10} \end{aligned}$$

\textcircled{1}

$$\begin{array}{c|ccccc} & 6 & 3 & 1 & -1 \\ \hline 0 & 0 & 0 & 1 & 1 \\ 1 & 0 & 0 & 1 & 0 \\ 2 & 0 & 1 & 0 & 1 \\ 3 & 0 & 1 & 0 & 0 \\ 4 & 0 & 1 & 1 & 0 \\ 5 & 1 & 0 & 0 & 1 \\ 6 & 1 & 0 & 0 & 0 \\ 7 & 1 & 0 & 1 & 0 \\ 8 & 1 & 1 & 0 & 1 \\ 9 & 1 & 1 & 0 & 0 \end{array}$$


\textcircled{4}

$$\begin{array}{c|ccccc} & 7 & 3 & 1 & -1 \\ \hline 0 & 0 & 0 & 0 & 0 & ? \\ 1 & 0 & 0 & 1 & 0 \\ 2 & 0 & 1 & 1 & 1 \\ 3 & 0 & 1 & 0 & 0 \\ 4 & 0 & 1 & 1 & 0 \\ 5 & 1 & 0 & 0 & 1 \\ 6 & 1 & 0 & 1 & 1 \\ 7 & 1 & 0 & 0 & 0 \\ 8 & 1 & 1 & 0 & 1 \\ 9 & 1 & 1 & 1 & 1 \end{array}$$

⑤

	5	4	-2	-1
?	0	0	0	0
1	0	1	1	1
2	0	1	1	0
3	0	1	0	1
4	0	1	0	0
5	1	0	0	0
6	1	1	1	1
7	1	1	1	0
8	1	1	0	1
9	1	1	0	0

1) NOT
 $f = \bar{a}$

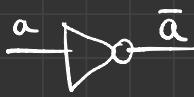


$a \mid f = \bar{a}$

0	1
1	0


2) AND

$$f = a \cdot b$$

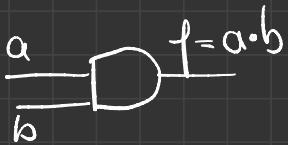


a	b	$a \cdot b$
0	0	0
0	1	0
1	0	0
1	1	1

3) OR $f = a + b$

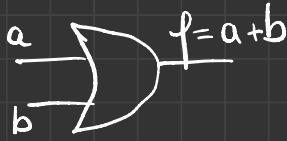


a	b	$a + b$
0	0	0
0	1	1
1	0	1
1	1	1

4) NAND

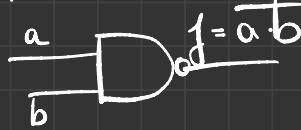

a	b	$\overline{a \cdot b}$
0	0	1
0	1	1
1	0	1
1	1	0

5) NOR

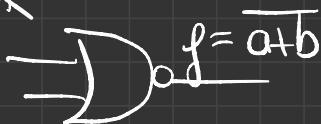

a	b	$\overline{a + b}$
0	0	1
0	1	0
1	0	0
1	1	0


6) XOR



$$f = a \oplus b = \bar{a}b + \bar{b}a$$

a	b	\bar{a}	\bar{b}	$\bar{a}b$	$\bar{b}a$	f
0	0	1	1	0	0	0
0	1	1	0	1	0	1
1	0	0	1	0	1	1
1	1	0	0	0	0	0

7) NXOR

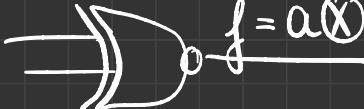

$$f = a \otimes b$$

a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

FORMA CANONICĂ DISJUNCTIVĂ

mintermeni = 1

$$f(\dots) = \sum (1, 2, 3)$$

$$f(\dots) = P_1 + P_2 + P_3$$

FORMA CANONICĂ CONJUNCTIVĂ

maxtermeni = 0

$$f(\dots) = \prod (2, 4, 6)$$

$$f(\dots) = S_2 \cdot S_4 \cdot S_6$$

Kuime-McCluskey minimization Technique

1. Prime Implicant (groups of 1)
2. Essential Prime Implicant

Ex $Y(A, B, C, D) = \sum_m (0, 1, 3, 7, 8, 9, 11, 15)$

Step 1: fa tabel după mre de 1

A B C D	
0 - 0 0 0	$\Rightarrow 0$
1 - 0 0 0	$\Rightarrow 1$
3 - 0 0 1	$\Rightarrow 2$
7 - 0 1 1	$\Rightarrow 3$
8 - 1 0 0 0	$\Rightarrow 1$
9 - 1 0 0 1	$\Rightarrow 2$
11 - 1 0 1 1	$\Rightarrow 3$
15 - 1 1 1 1	$\Rightarrow 4$

Group	Minterm	A	B	C	D
0	m_0	0	0	0	0
1	m_1	0	0	0	1
	m_8	1	0	0	0
2	m_3	0	0	1	1
	m_9	1	0	0	1
3	m_7	0	1	1	1
	m_{11}	1	0	1	1
4	m_{15}	1	1	1	1

Step 2: Matched pairs

Group	Matched pairs	A	B	C	D
0	$m_0 - m_1$	0	0	0	-
	$m_0 - m_8$	-	0	0	0

1	$m_1 - m_3$	0 0 - 1	$\begin{pmatrix} 1 & 0 & 0 \\ 0 & 1 & 1 \\ 0 & 0 & 1 \end{pmatrix}$
	$m_1 - m_9$	- 0 0 1	
	$m_8 - m_9$	1 0 0 -	$\begin{pmatrix} 0 & 0 & 1 \\ 0 & 1 & 1 \end{pmatrix}$
2	$m_3 - m_7$	0 - 1 1	$\begin{pmatrix} 1 & 0 & 0 \\ 0 & 1 & 1 \\ 0 & 0 & 1 \end{pmatrix}$
	$m_3 - m_{11}$	- 0 1 1	
	$m_9 - m_{11}$	1 0 - 1	
3	$m_7 - m_{15}$	- 1 1 1	
	$m_{11} - m_{15}$	1 - 1 1	

acelasi pasca si la 2

Step 3 Group Match.P. A B C D

0	$m_0 - m_1 - m_8 - g$ (0, 8, 11, g)	- 0 0 -	$\{ \overline{BC} }$
1	(1, 3, 9, 11)	- 0 - 1	$\{ \overline{BD} }$
	(1, 9, 3, 11)	- 0 - 1	
2	(3, 7, 11, 15)	- - 1 1	$\{ \overline{CD} }$
	(3, 11, 7, 15)	- - 1 1	

Step 4 = Prime Implicant table - minimize

PI	Minterms	0	1	3	7	8	9	11	15
\overline{BC}	0, 1, 8, 9	*	*			*			

\overline{BD}	$ 1, 3, 9, 11 $	$ * *$	$ * *$
cD	$ 3, 7, 11, 15 $	$ * $	$ * *$



$$Y = \overline{BC} + cD$$

Pensare Sanguine

De aici am inceput eu


$$a) \quad x \cdot (y + z)$$



x	y	z	$y + z$	$x \cdot (y + z)$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

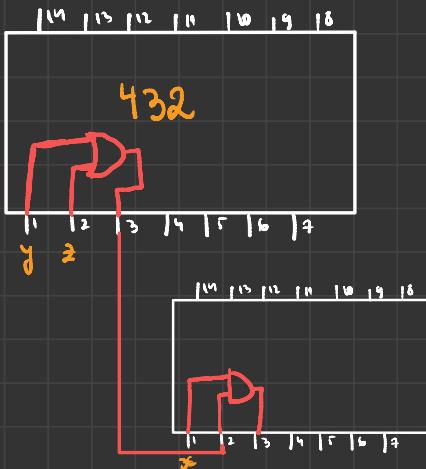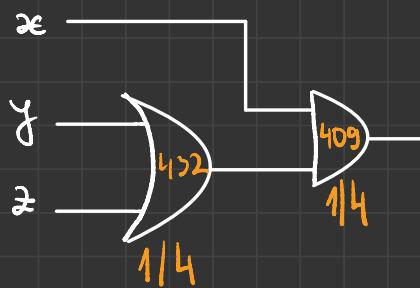

$$d) \bar{x} + \bar{y} \cdot \bar{z}$$

\bar{x}	\bar{y}	\bar{z}	\bar{x}	\bar{y}	\bar{z}	$\bar{y} \cdot \bar{z}$	$\bar{x} + \bar{y} \cdot \bar{z}$
0	0	0	1	1	1	0	1
0	0	1	1	1	0	0	1
1	0	0	0	0	0	0	1
1	0	1	0	1	0	0	1
1	1	0	0	1	1	0	0
1	1	1	0	0	1	0	0
1	1	1	0	0	0	0	0

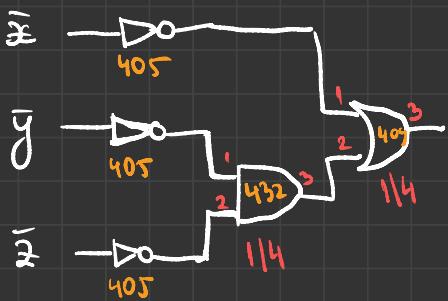


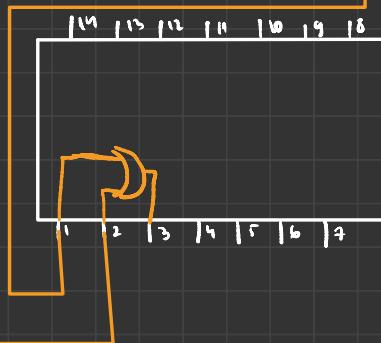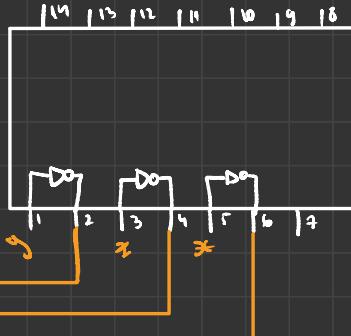

$$e) W \cdot (\bar{x} + y \cdot z)$$

W				AND	OR	AND	$W \cdot (\bar{x} + y \cdot z)$
	x	y	z	$y \cdot z$	$\bar{x} + y \cdot z$		
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	1	0	0
0	0	1	1	1	1	1	0
0	1	0	0	0	0	1	0
0	1	0	1	0	1	1	0
0	1	1	0	0	0	1	0
0	1	1	1	1	1	1	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	0	0	0	1
1	1	0	0	0	0	0	0

1	1	0	0	0	1	1	1
1	1	0	1	0	1	1	1
1	1	1	0	0	1	1	1
1	1	1	1	1	1	1	1

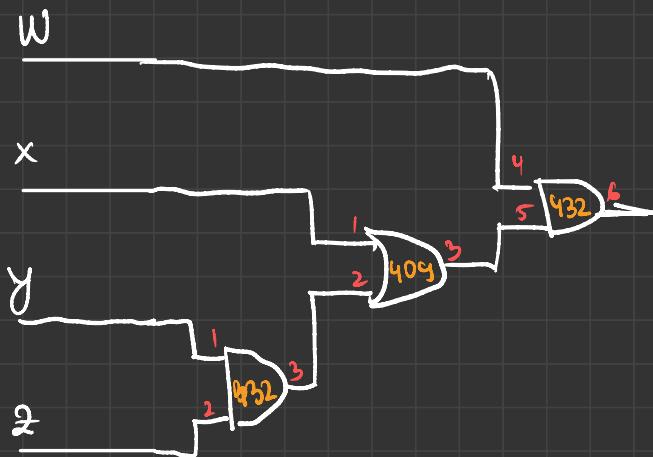



$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

$$\begin{aligned}
 f &= \overline{(x+y)} + \overline{(x+z)} = \overline{(x \cdot y)} + \overline{(x \cdot z)} = \overline{(x \cdot y)} + \overline{(x \cdot z)} \\
 &= \overline{(x \cdot y)} \cdot \overline{(x \cdot z)} = (x \cdot y) \cdot (x \cdot z) = 0
 \end{aligned}$$

$$f = \overline{\overline{x} + (\overline{y+z})} = \overline{\overline{x}} \cdot (\overline{\overline{y+z}}) = x \cdot (y+z)$$

<i>a</i>	<i>b</i>	<i>c</i>	\bar{a}	\bar{b}	$\bar{a} + \bar{b}$	$\bar{a} + \bar{c}$	$\bar{a} + \bar{b} + \bar{a} + \bar{c}$
0	0	0	1	1	1	1	1
0	0	1	1	1	1	0	1
0	1	0	1	0	1	1	1
0	1	1	1	0	1	0	1
1	0	0	0	1	1	0	1
1	0	1	0	1	1	0	1
1	1	0	0	0	0	0	0
1	1	1	0	0	0	0	0

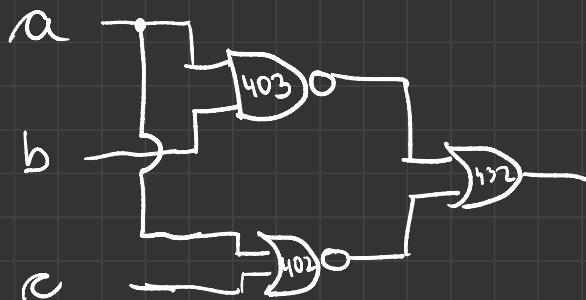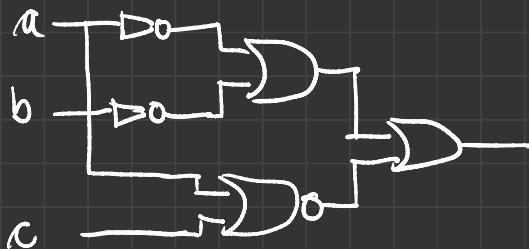

Algebra booleană

$$2) \overline{\bar{a} \cdot \bar{b}} + \overline{a+b+c+d}$$

$$\overline{\overline{a+b}} + \overline{a+b} \cdot \overline{c+d}$$

$$\overline{a \cdot b} = \overline{\overline{a+b}}$$

$$\overline{\bar{a}+\bar{b}} = \overline{a \cdot b}$$

$$A + A\bar{B} = A$$

$$\overline{a+b}$$

$$3) a+b \cdot \bar{c} + \bar{a} \cdot b \cdot \bar{c} \cdot (a \cdot d + b)$$

$$a+b\bar{c} + \overbrace{\bar{a}\bar{b}\bar{c}ad}^{\substack{\bar{a}\bar{b}\bar{c}ad \\ \bar{a} \cdot a = 0}} + \bar{a}\bar{b}\bar{c}b$$

$$a+b\bar{c} + \bar{a}\bar{b}\bar{c}$$

$$a+b\bar{c} + \bar{a} \cdot \bar{c} \cdot b$$

$$a + b(\bar{c} + \bar{a}\bar{c})$$

$$a + b\bar{c}$$

$$\left. \begin{array}{l} \bar{a}\bar{b}\bar{c}ad \\ \bar{a} \cdot a = 0 \\ \bar{a}\bar{b}\bar{c}b \\ b \cdot b = b \end{array} \right\} = \bar{a}\bar{b}\bar{c}$$

$$\begin{array}{l} \bar{c} = A \\ \bar{a} = B \end{array}$$

$$A + A \cdot B = A$$

$$1) a) x_1 + \bar{x}_1 x_2 = x_1 + x_2$$

$$(x_1 + \bar{x}_1) \cdot (x_1 + x_2) = 1 \cdot x_1 + x_2 = x_1 + x_2$$

$$b) x_1 \cdot (\bar{x}_1 + x_2) = x_1 \cdot x_2$$

$$x_1 \cdot \bar{x}_1 + x_1 \cdot x_2 = 0 + x_1 \cdot x_2 = x_1 \cdot x_2$$

$$2) 1) \overline{\overline{A} + \overline{B}} + \overline{\overline{A} + \overline{B}} = A \cdot B$$

$$(A \cdot B) + (A \cdot B) = A \cdot B$$

$$2) A \cdot B + A \cdot C + B \cdot \overline{C} = A \cdot C + B \cdot \overline{C}$$

$$AB + AC + B\overline{C} =$$

$$A(B + C) + B\overline{C} =$$

AND

A	B	C	\overline{C}	$A \cdot B$	$A \cdot C$	$B \cdot \overline{C}$	$AB + AC$	$-BC + B\overline{C}$
0	0	0	1	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	1	0	0	1	0	1
0	1	1	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0
1	0	1	0	0	1	0	1	1
1	1	0	1	1	0	1	1	1
1	1	1	0	1	1	0	1	1

$$C) A \cdot B + \overline{B} \cdot \overline{C} + A \cdot \overline{C} = A \cdot B + \overline{B} \cdot \overline{C}$$

$$AB + \overline{B}\overline{C} + A\overline{C} =$$

$$AB + \overline{B+C} + A\overline{C}$$

$$A(B + \overline{C}) + \overline{B+C} =$$

			AND					
A	B	C	\bar{B}	\bar{C}	A · B	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot \bar{C}$	⊕
0	0	0	1	1	0	0	0	0
0	0	1	1	0	0	0	0	0
0	1	0	0	1	0	0	0	0
0	1	1	0	0	0	0	0	0
1	0	0	1	1	0	1	0	1
1	0	1	1	0	0	0	1	1
1	1	0	0	0	1	0	0	1
1	1	1	0	0	1	1	1	1

$$A \oplus B = \overline{A \oplus \bar{B}} = \overline{\bar{A} \oplus B}$$

$$a \oplus b = a \cdot \bar{b} + \bar{a} \cdot b$$

$$\begin{aligned}
 \widehat{A \oplus B} &= \overline{A \cdot \bar{B} + \bar{A} \cdot B} = \overline{A \cdot \bar{B} + \bar{A} \cdot B} = \overline{A \bar{B}} \cdot \overline{\bar{A} B} \\
 &= (\bar{A} + \bar{B}) \cdot (\overline{\bar{A} B}) \\
 &= (\bar{A} + \bar{B}) \cdot (A + B) \\
 &= \bar{A} A + \bar{A} B + A \bar{B} + B \bar{B} \\
 &= A \oplus B
 \end{aligned}$$

10) Minimizabilă funcția $f: \Sigma(0, 2, 8, 10)$

		C				
		00	01	11	10	
A		00	1	0	0	1
B		01	0	0	0	0
C		11	0	0	0	0
D		10	1	0	0	1

$$f = \overline{x_3}x_2 \cdot x_0 + \overline{x_3}x_2 x_1 +$$

		00	01	11	10
		$x_3 x_2$	$x_3 \bar{x}_2$	$\bar{x}_3 x_2$	$\bar{x}_3 \bar{x}_2$
00		0	1	X	1
01		X	0	1	0
11		1	1	1	0
10		1	1	0	0

$$f: \overline{x_3}x_2 \cdot x_0 + \overline{x_3}x_2 x_1 + \\ x_1 x_0 \cdot x_2 + x_3 \cdot \overline{x_1}$$


$$5) \quad f(x_1, y_1, z) = \sum (1, 3, 7)$$

xy

	00	01	11	10
0	0	1	1	0
1	0	0	1	0

$$f: (\bar{x}+y) \cdot (\bar{z}+x) \cdot (\bar{x}+y)$$

$$1) \quad f = \sum (1, 7, 9, 13, 15)$$

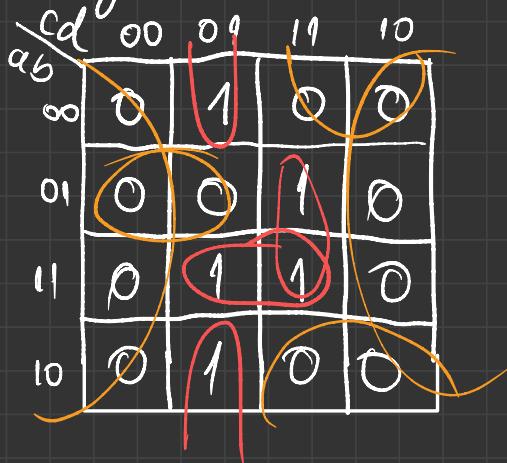

0001	1
0111	7
1101	13
1001	9
1111	15

$$f: \bar{c}d\bar{b} + cd\bar{b} + ab\bar{d}$$

$$f = \sum (1, 3, 5, 6, 7)$$

$ab \backslash cd$	00	01	11	10
00	0	1	1	0
01	0	1	1	1
11	0	0	0	0
10	0	0	0	0

$$f: \bar{a}d + \bar{a}b\bar{c}$$

4) $f: \sum (1, 4, 5, 6, 7, 9, 14, 15)$

$ab \backslash cd$	00	01	11	10
00	1			
01	1	1	1	1
11			1	1
10	1			

$$f: bc + \bar{a}b + \bar{c}d\bar{b}$$

2) 1) $f: \sum (2, 3, 10, 11, 14, 15) + \sum_0 (0, 1, 8, 9)$

$ab \backslash cd$	00	01	11	10
00	X	X	1	1
01				
11			1	1
10	X	X	1	1

$$f: ac + \bar{b}$$

$$2) \sum (0, 1, 3, 15, 14) + \sum_0 (8, 15)$$

$ab\backslash cd$	00	01	11	10
00	1 ₀	1 ₁	1 ₂	2
01	4	1 ₃	7	6
11	1 ₂	1 ₃	X ₅	1 ₄
10	X ₈	9	11	10

$$f: \bar{c}\bar{d}\bar{b} + abc + \bar{c}d\bar{a}$$

$$+ \bar{a}\bar{b}d$$

$$3) f = \sum (1, 5, 9, 14, 15) + \sum_0 (11)$$

$ab\backslash cd$	00	01	11	10
00	0	1 ₁	3	2
01	4	1 ₃	7	6
11	1 ₂	1 ₃	1 ₅	1 ₄
10	1 ₈	9	X ₁₁	10

$$f: \bar{c}d\bar{a} + d\bar{c}\bar{b} + abc$$

$$4) f: \sum (3, 5, 6, 7, 13) + \sum_0 (1, 2, 4, 12, 15)$$

cd	00	01	11	10
ab	00	X ₁	1 ₃	X ₂
ab	01	X ₁ ₁	1 ₅	1 ₆
ab	11	X ₁ ₂	X ₅	1 ₄
ab	10	8	9	11

$$f: \overline{bc} + \overline{a}c$$

3. 1) $f = \sum (1, 3, 4, 5, 6, 7, 9, 11)$

cd	00	01	11	10
ab	00	1 ₀	1 ₃	1 ₂
ab	01	1 ₄	1 ₅	1 ₆
ab	11	1 ₁	1 ₇	1 ₄
ab	10	1 ₈	1 ₉	1 ₆

$$f: \overline{ab} + \overline{b}d$$

$$f: (\overline{a} + \overline{b}) \cdot (b + d)$$

2) $f: \sum (2, 3, 10, 11, 14, 15) + \sum_0 (8, 9)$

a_5	a_4	c	d	00	01	11	10
00	0	0	0	00	01	11	10
01	1	1	1	00	01	11	10
11	12	13	14	11	15	11	11
10	X	X	X	11	11	11	11

$$f = ac + c\bar{b}$$

$$f = (a+b) \cdot c$$

4. $f = \sum (1, 3, 5, 6, 7, 9, 11, 15)$

a_5	a_4	c	d	00	01	11	10
00	0	0	0	00	01	11	10
01	1	1	1	00	01	11	10
11	12	13	14	11	15	11	11
10	8	5	1	11	11	11	11

$$f = \bar{a}d + \bar{b}d + cd \\ + \bar{a}bc$$

$$\overline{a \cdot b} = \text{NAND}$$

$$f = \bar{a} \cdot d + \bar{b} \cdot d + c \cdot d + \bar{a} \cdot b \cdot c$$

$$f = \overline{\bar{a} \cdot d} \cdot \overline{\bar{b} \cdot d} \cdot \overline{c \cdot d} \cdot \overline{\bar{a} \cdot b \cdot c}$$

$$f = \overline{a \cdot a \cdot d} \cdot \overline{b \cdot b \cdot d} \cdot \overline{c \cdot d} \cdot \overline{a \cdot a \cdot b \cdot c}$$

\sum - forma dijunctiva normală

$f(\dots)$ - sumă de produse

	00	01	11	10
00	0 ₀	0 ₁	0 ₃	0 ₂
01	0 ₄	1 ₅	0 ₇	0 ₆
11	0 ₁₂	0 ₈	0 ₁₅	1 ₁₄
10	1 ₈	0 ₉	0 ₁₁	0 ₁₀

Circuite MSI:


- 1) 1 bit Comparator
- 2) 2 — " —
- 3) MUX — " —
- 4) DMUX 2:1, 4:1, 8:1, 16:1
- 5) Parity detector
- 6) Encoder
- 7) 1 bit Full-Adder
- 8) Decoder

1 Si, SAV, NU au (NAND)

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

$\neg D \circ D$ (AND) din NAND + NOT
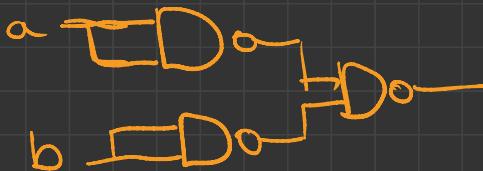
$$f = a+b = \overline{\overline{a}+\overline{b}} = \overline{\overline{a} \cdot \overline{b}} = \overline{\overline{a} \cdot a + \overline{b} \cdot b}$$



OR din NAND

2.


NOR

A	B	y
0	0	1
0	1	0
1	0	0
1	1	0



OR from NOR
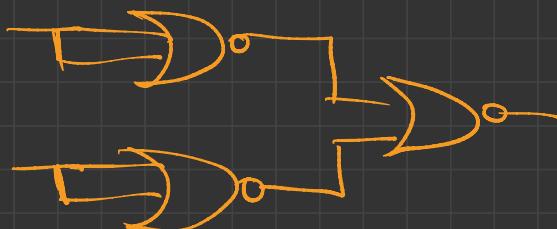
$$f : a \cdot b = \overline{\overline{a} \cdot \overline{b}} = \overline{\overline{a} + \overline{b}} = \overline{\overline{\overline{a+a}} + \overline{\overline{b+b}}}$$




AND from NOR

$$3) f = \overline{\underline{a \cdot b} + \underline{\overline{a} \cdot \overline{b} \cdot c} + \underline{\overline{b} \cdot (a+c)}}$$

$$f = \overline{\overline{\overline{a+a}} + \overline{\overline{b+b}}} + \overline{a+b} + \overline{\overline{c+c}} + \overline{b + (\overline{a+c})}$$

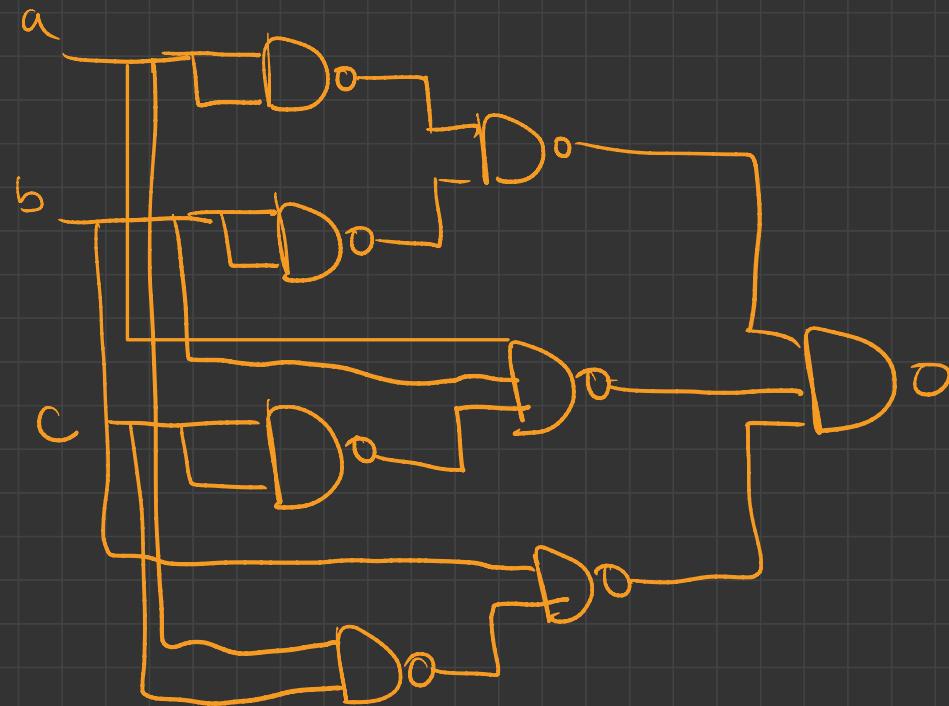
$$\overline{b \cdot (a+c)} = \overline{b} \cdot \overline{(a+c)} = \overline{b + (\overline{a+c})}$$



$$5) f = \bar{a} \cdot b \cdot \bar{d} + \bar{a} \cdot b \cdot \bar{c} \cdot d + a \cdot b \cdot c \cdot \bar{d}$$

0 1 0 0 1 0 1 1 1 1 0
 2 5 14

$$f = \sum (2, 5, 14)$$

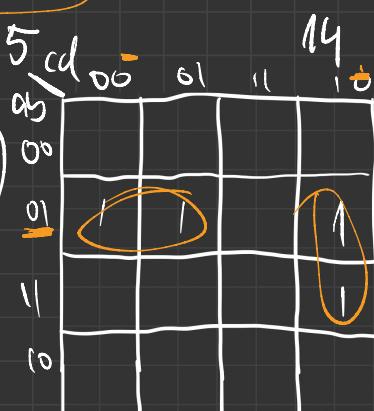

$$\bar{a}\bar{b}\bar{c} + \bar{c}\bar{d}\bar{b}$$

$$f = \sum (1, 4, 5, 7, 8, 9, 11, 14, 15)$$

	a	b	c	d	f
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	1

maxterm



minterm

ab\cd	00	01	11	10
00	0	1	0	0
01	1	1	1	0
11	0	0	1	1
10	1	1	1	0

$$f_d = \bar{a}\bar{b}\bar{c}d + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}\bar{d} + \bar{a}\bar{b}\bar{c}d + ab\bar{c}d + ab\bar{c}\bar{d} + a\bar{b}\bar{c}\bar{d} + a\bar{b}\bar{c}d + a\bar{b}cd$$

$$f_C = (a+b+c+d) \cdot (\bar{a}+\bar{b}+\bar{c}+\bar{d}) \cdot (\bar{a}+b+\bar{c}+d)$$

$$\begin{aligned} & \bullet (\bar{a}+\bar{b}+\bar{c}+d) \cdot (\bar{a}+\bar{b}+c+d) \cdot (\bar{a}+\bar{b}+c+\bar{d}) \\ & \bullet (\bar{a}+b+\bar{c}+d) \end{aligned}$$

7) $f = \sum (1, 3, 5, 6, 7, 13) + \sum_0 (2, 4, 12, 15)$


	a	b	c	d	f
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	X
3	0	0	1	1	1
4	0	1	0	0	X
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	X
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	1

$$f_{\text{cu}} = (\bar{a}+b+c+d) \cdot (\bar{a}+b+c+d) \cdot (\bar{a}+b+c+\bar{d}) \cdot (\bar{a}+b+\bar{c}+\bar{d})$$

ab\cd	00	01	11	10
00	0	1	1	X
01	X	1	1	1
11	X	1	X	0
10	0	0	0	0

$$f: (\bar{a}+\bar{c}) \cdot (c+d) \cdot (\bar{a}+b)$$
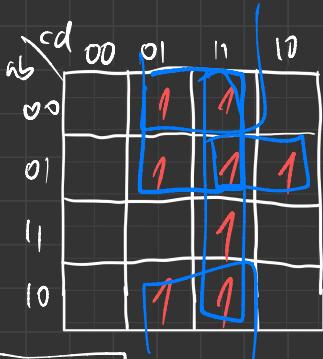
$$4) f = \sum (1, 3, 5, 6, 7, 9, 10, 15)$$




$$\boxed{\overline{a} \cdot \overline{d}}$$

$$f = \overline{a} \cdot \overline{d} + \overline{b} \cdot \overline{d} + c \cdot \overline{d} + \overline{a} \cdot b \cdot c$$


$$f = \overline{\overline{a} \cdot \overline{d}} \cdot \overline{\overline{b} \cdot \overline{d}} + \overline{c \cdot \overline{d}} \cdot \overline{\overline{a} \cdot b \cdot c}$$

$$f = \overline{\overline{\overline{a} \cdot \overline{a} \cdot \overline{d}}} \cdot \overline{\overline{\overline{b} \cdot \overline{b} \cdot \overline{d}}} \cdot \overline{c \cdot \overline{d}} \cdot \overline{\overline{\overline{a} \cdot \overline{a} \cdot b \cdot c}}$$


2) DECODER

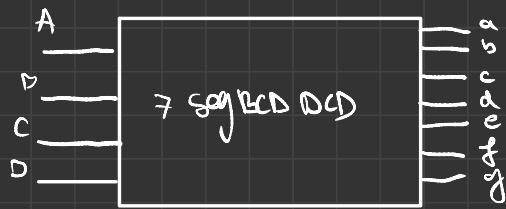

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X
1	1	1	1	Y	X	X	X	X	X	X

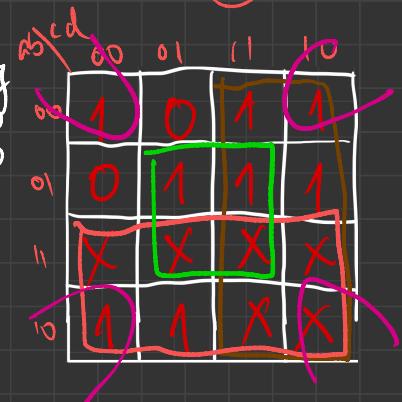

$$f: a + c + \overline{b}d - bd$$

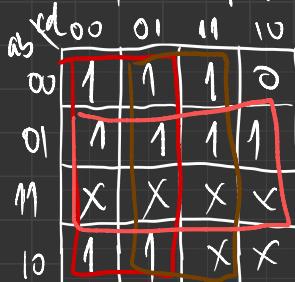

$$j: \overline{c} + d + b$$

(C)

ab	cd	00	01	11	10
00	0	0	1	1	
01	1	1	0	1	
11	X	X	X	X	
10	1	1	X	X	

(G)

$$f: a + b\bar{c} + \bar{c}\bar{d} + \bar{b}\bar{c}$$

A	B	C	D	E ₁	E ₂	E ₃	E ₄	
0	0	0	0	0	0	1	1	
0	0	0	1	0	1	0	0	
0	0	1	0	0	1	0	-1	
0	0	1	1	0	1	-1	0	
0	1	0	0	0	1	1	1	
0	1	0	1	1	0	0	0	
0	1	1	0	1	0	0	1	
0	1	1	1	1	0	1	0	
1	0	0	0	1	0	1	1	
1	0	0	1	1	1	0	0	
1	0	1	0	1	1	0	-1	
1	0	1	1	1	1	1	0	
1	1	0	0	1	1	1	1	
1	1	0	1	0	0	0	0	
1	1	1	0	0	0	0	1	
1	1	1	1	0	0	1	0	

ab	cd	00	01	11	10
00	1	0	1	0	
01	1	0	1	0	
11	1	0	1	0	
10	1	0	1	0	

F3

ab	cd	00	01	11	10
00	1	0	0	1	
01	1	0	0	1	
11	1	0	0	1	
10	1	0	0	1	

(E4)

$$f: \bar{d}$$

(51)


ab	cd	00	01	11	10
00	0	0	0	0	0
01	0	1	1	1	1
11	1	0	0	0	0
10	1	1	1	1	1

$$f: \bar{c}\bar{d}a + \bar{a}\bar{b} + \bar{a}bd + \bar{a}bc$$

(E2)

ab	cd	00	01	11	10
00	0	0	1	1	1
01	1	0	0	0	0
11	1	0	0	0	0
10	0	1	1	1	1

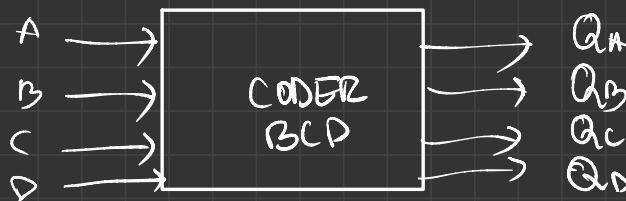
$$f: \bar{b}c + \bar{b}d + \bar{c}\bar{d}b$$



$$a) F(x,y,z) = \sum (1,3,7) \\ = \pi (0,2,4,5,6)$$


Circuite CLC

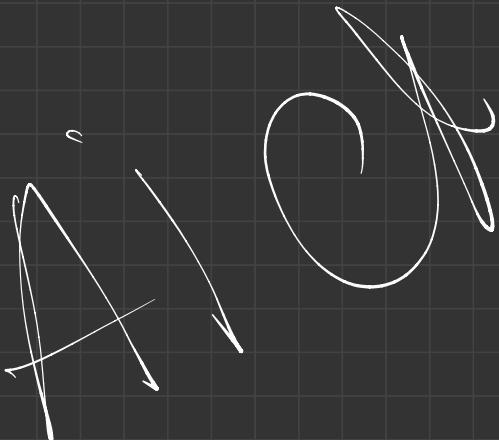1. Code converter
2. Priority encoder
3. Decoder , $n \leq 2^m$, m-intări , 4:10 , 3:8 , 4:16
n-iesiri
4. Multiplexor
5. Demultiplexor




$$1) f = \sum(1, 3, 9, 12)$$

b) MUX 16:1

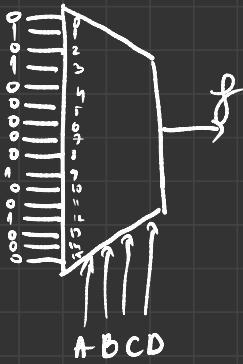

1001
0001

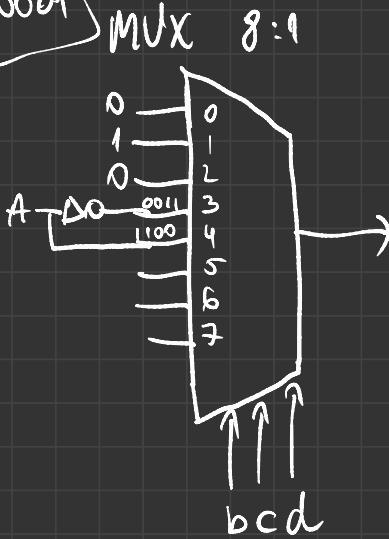

MUX 8:1

ab	cd	00	01	11	10
00		0	1	1	0
01		0	0	0	0
11		1	0	0	0
10		0	1	0	0


1011

0011


1001

$$\begin{array}{r} A \\ \overline{0} = \overline{A} \\ \overline{1} = A \\ \hline \overline{0100} = 12 \\ \overline{1100} \end{array}$$


$$f = \sum(0, 1, 2, 3, 11, 12, 14, 15)$$

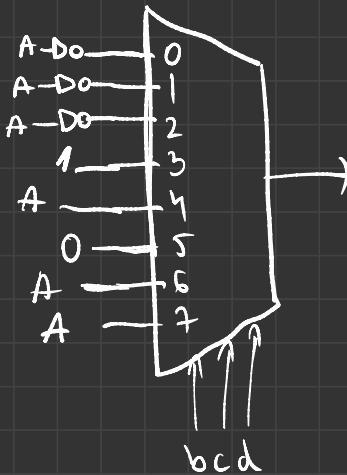

a	b	00	01	11	10
00	00	1	1	1	1
01	01	0	0	0	0
11	11	1	0	1	1
10	10	0	0	1	0

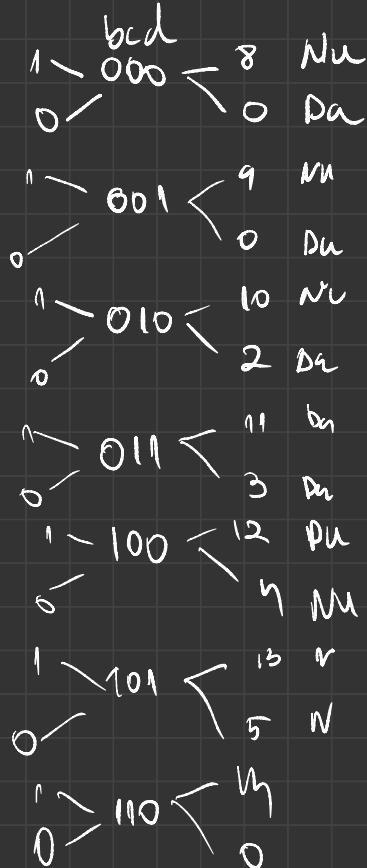


$$f = \sum (1, 3, 9, 12)$$

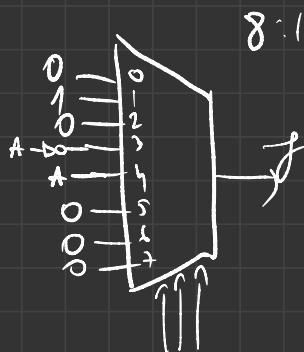

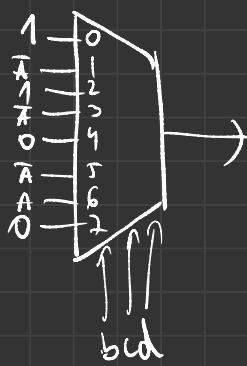8:1

$$f = \overline{P} (0, 1, 2, 3, 5) \quad (8, 10, 14)$$



0, 0, 0
0, 1
1, 0, 1
1, 1, 0

$A=1$ bcd 8 DA = 1
 $\bar{A}=0$ 000 0 DA



$A=1$ bcd 9
 $\bar{A}=0$ 001 1 \bar{A}

1 > 010 0
0 > 010 2

1 > 011 1
0 > 011 3

> 110
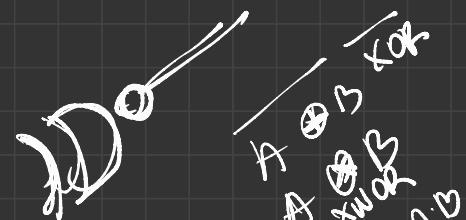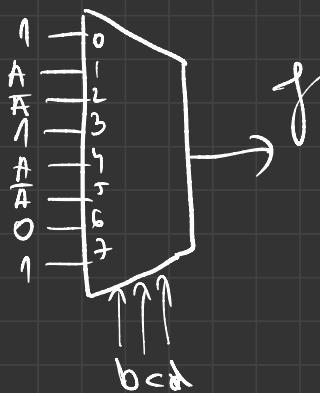
$$f = \sum (0, 1, 2, 3, 5, 7, 8, 9, 11, 12, 15)$$



$$f = \sum (0, 1, 2, 3, 11, 12, 14, 15) \quad c, d$$

cd
00
01
10
11

	00	01	10	11
00	1	0	1	0
01	0	1	0	1
10	1	1	0	0
11	0	0	1	1

$$\begin{array}{r} 00 \\ \hline AB + A \cdot B \end{array}$$

$$\begin{array}{r} 0000=0 \\ 1100=14 \end{array}$$

$$A \otimes B$$

$$0 = \overrightarrow{A \oplus B}$$

1, eq

$$\begin{array}{r} 0001 = 1 \\ 0101 = 5 \\ 1101 = 13 \\ 1001 = 9 \end{array}$$


$$1 = \bar{A} \cdot \bar{B}$$

$$\begin{array}{rcl}
 0011 & = 3 \\
 0111 & = 7 \\
 1111 & = 15 \\
 1011 & = 11
 \end{array}$$

$$\begin{array}{l}
 \overline{A} \cdot \overline{B} + A \cdot B + A \cdot \overline{B} \\
 \hline
 \overline{A \oplus B} + A \cdot \overline{B}
 \end{array}$$

$$\begin{array}{rcl}
 0010 & = 2 \\
 0110 & = 6 \\
 1110 & = 14 \\
 1010 & = 10
 \end{array}$$
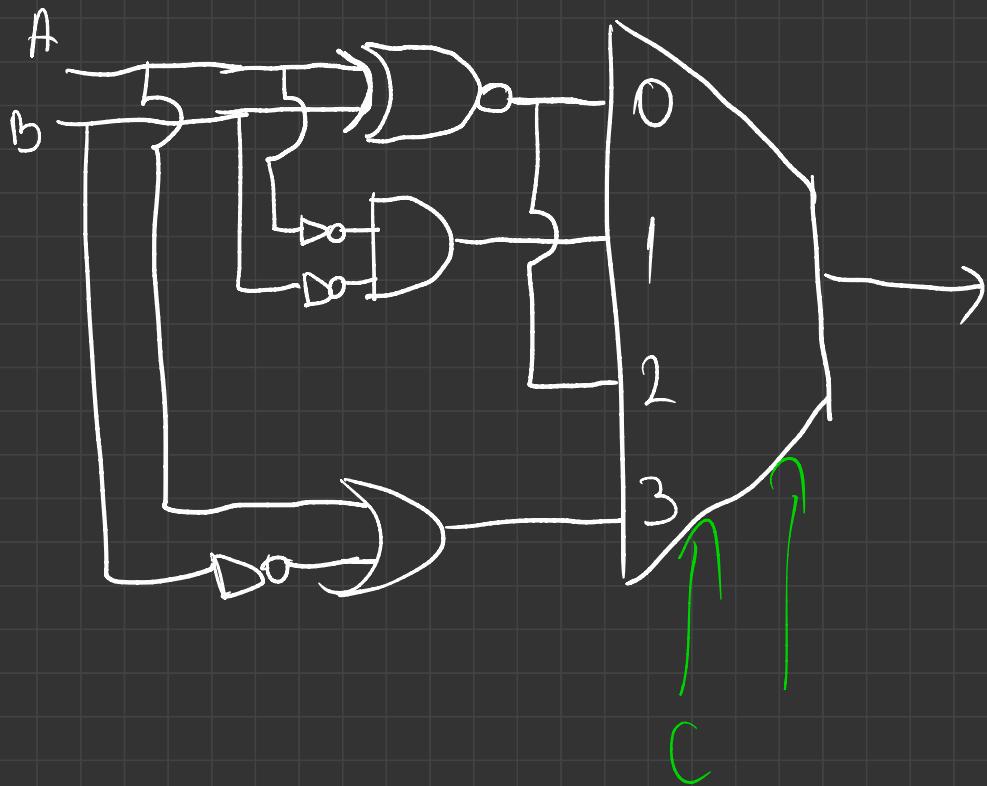
$$\begin{array}{l}
 \overline{A} \cdot \overline{B} + A \cdot B \\
 \hline
 \overline{A \oplus B}
 \end{array}$$



$$f = \sum (0, 2, 3, 5, 7, 8, 9, 11, 12, 15)$$

MUX 4:1


ab/cd	00	01	11	10
8	1	0	1	1
01	0	1	1	0
11	1	0	1	0
10	1	1	1	0

$$0 - b\bar{c}\bar{d} + a\bar{c}\bar{d} = a+b$$

$$1 - ab + \bar{a}b = a \oplus b$$

$$2 - \bar{a}b$$


$$3. - 1$$

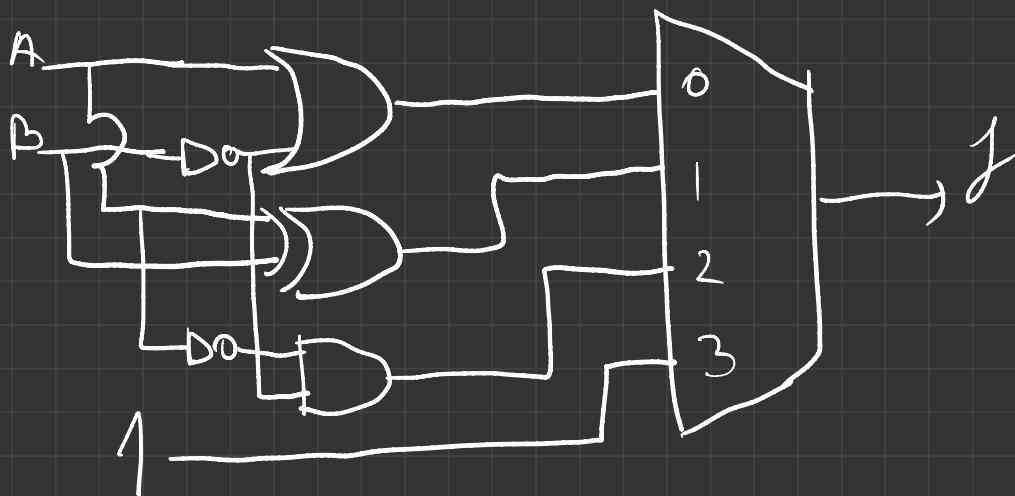

$$f = \sum(1, 3, 9, 12)$$

ab\cd	00	01	11	10
00	1	1	0	
01	0	0	0	0
11	1	0	0	0
10	0	1	0	0
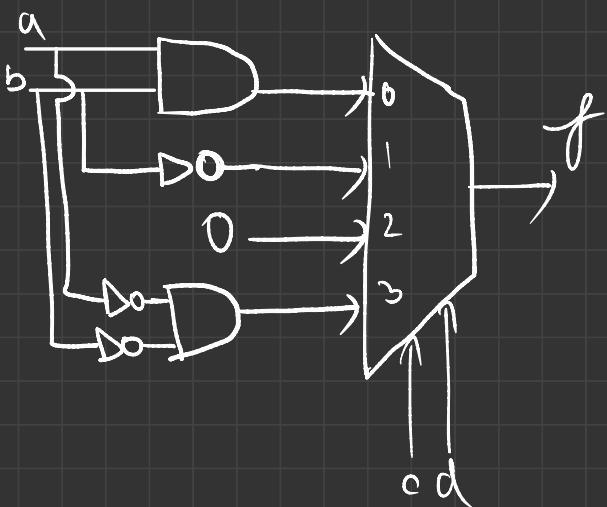
$$\begin{aligned}
 0 - & ab \\
 1 - & \overline{b} \\
 3 - & \overline{a} \cdot \overline{b} \\
 2 - & 0
 \end{aligned}$$



$$f = \sum(1, 3, 9, 12)$$

$a\bar{b}$	$c\bar{d}$	00	01	11	10
$\bar{a}b$	00	0	1	1	0
$a\bar{b}$	01	0	0	0	0
$\bar{a}b$	11	1	0	0	0
$\bar{a}b$	10	0	1	0	0

$$D = 0$$


$a\bar{b}$	c	00	01
$\bar{a}b$	00	0	0
$a\bar{b}$	01	0	0
$\bar{a}b$	11	1	0
$\bar{a}b$	10	0	0

$$f = ab\bar{c}$$

$$D = 1$$

$a\bar{b}$	c	01
$\bar{a}b$	00	1
$a\bar{b}$	01	0
$\bar{a}b$	11	0
$\bar{a}b$	10	1

$$f = \bar{a}\bar{b} + \bar{b}\bar{c}$$

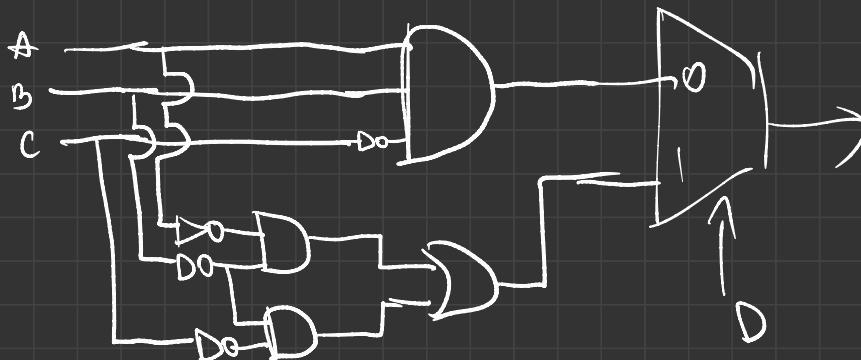


Decoder:

$$f = \sum (0, 2, 3, 4, 7, 8, 9) + \sum_0 (6, 10, 11, 12, 13, 14, 15)$$

$ab\backslash cd$	00	01	11	10
00	1	0	1	1
01	1	0	1	x
11	x	x	x	x
10	1	1	x	x

$$f: a + c + d$$

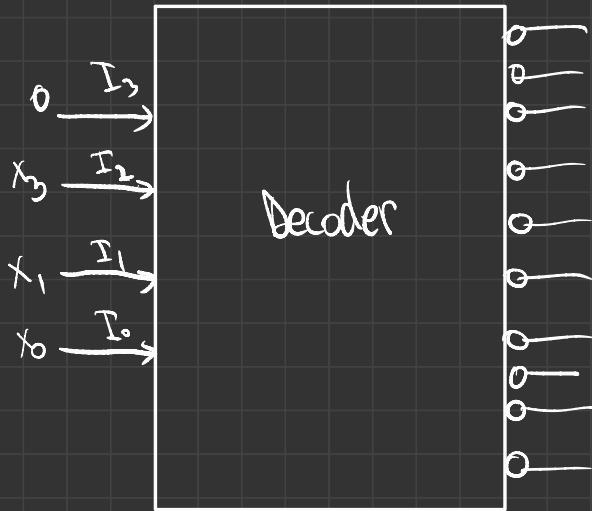

$$f = \overline{x_3} \ x_1 \ \overline{x_0}$$

(0) | (1) $\Rightarrow 0_5$